

# SKP Engineering College

Tiruvannamalai – 606611

A Course Material

on

Linear Integrated Circuits



By

**A.Vigneswaran**

**Assistant Professor**

**Electronics and Communication Engineering Department**

### Quality Certificate

This is to Certify that the Electronic Study Material

Subject Code: EC6404

Subject Name: Linear Integrated Circuits

Year/Sem: II /IV

Being prepared by me and it meets the knowledge requirement of the University curriculum.

Signature of the Author

Name: A.Vigneswaran

Designation: Assistant Professor

This is to certify that the course material being prepared by Mr.A.Vigneswaran is of the adequate quality. He has referred more than five books and one among them is from abroad author.

Signature of HD

Name:

Seal:

Signature of the Principal

Name: Dr.V.Subramania Bharathi

Seal:

**EC6404 LINEAR INTEGRATED CIRCUITS****L T P C****3 0 0 3****OBJECTIVES:**

- To introduce the basic building blocks of linear integrated circuits.
- To learn the linear and non-linear applications of operational amplifiers.
- To introduce the theory and applications of analog multipliers and PLL.
- To learn the theory of ADC and DAC.
- To introduce the concepts of waveform generation and introduce some special function ICs.

**UNIT I BASICS OF OPERATIONAL AMPLIFIERS****9**

Current mirror and current sources, Current sources as active loads, Voltage sources, Voltage References, BJT Differential amplifier with active loads, Basic information about op-amps – Ideal Operational Amplifier - General operational amplifier stages -and internal circuit diagrams of IC 741, DC and AC performance characteristics, slew rate, Open and closed loop configurations.

**UNIT II APPLICATIONS OF OPERATIONAL AMPLIFIERS****9**

Sign Changer, Scale Changer, Phase Shift Circuits, Voltage Follower, V-to-I and I-to-V converters, adder, subtractor, Instrumentation amplifier, Integrator, Differentiator, Logarithmic amplifier, Antilogarithmic amplifier, Comparators, Schmitt trigger, Precision rectifier, peak detector, clipper and clamper, Low-pass, high-pass and band-pass Butterworth filters.

**UNIT III ANALOG MULTIPLIER AND PLL****9**

Analog Multiplier using Emitter Coupled Transistor Pair - Gilbert Multiplier cell – Variable transconductance technique, analog multiplier ICs and their applications, Operation of the basic PLL, Closed loop analysis, Voltage controlled oscillator, Monolithic PLL IC 565, application of PLL for AM detection, FM detection, FSK modulation and demodulation and Frequency synthesizing.

**UNIT IV ANALOG TO DIGITAL AND DIGITAL TO ANALOG CONVERTERS 9**

Analog and Digital Data Conversions, D/A converter – specifications - weighted resistor type, R-2R Ladder type, Voltage Mode and Current-Mode  $R \square 2R$  Ladder types - switches for D/A converters, high speed sample-and-hold circuits, A/D Converters – specifications - Flash type – Successive Approximation type - Single Slope type – Dual Slope type - A/D Converter using Voltage-to-Time Conversion - Over-sampling A/D Converters.

**UNIT V WAVEFORM GENERATORS AND SPECIAL FUNCTION ICs 9**

Sine-wave generators, Multivibrators and Triangular wave generator, Saw-tooth wave generator, ICL8038 function generator, Timer IC 555, IC Voltage regulators – Three terminal fixed and adjustable voltage regulators - IC 723 general purpose regulator - Monolithic switching regulator, Switched capacitor filter IC MF10, Frequency to Voltage and Voltage to Frequency converters, Audio Power amplifier, Video Amplifier, Isolation Amplifier, Opto-couplers and fibre optic IC.

**TOTAL: 45 PERIODS**

**OUTCOMES:**

**Upon Completion of the course, the students will be able to:**

- Design linear and non linear applications of op– amps.
- Design applications using analog multiplier and PLL.
- Design ADC and DAC using op – amps.
- Generate waveforms using op – amp circuits.
- Analyze special function ICs.

**CONTENTS**

<b>S.No</b>	<b>Particulars</b>	<b>Page</b>
1	Unit – I	6
2	Unit – II	26
3	Unit – III	77
4	Unit – IV	99
5	Unit – V	132

**Unit – I****Basics Of Operational Amplifiers****Part – A**

1. **A differential amplifier has a differential voltage gain of 2000 and a common mode gain of 0.2. Determine the CMRR in dB. [CO1-H1-April/May 2015]**

$$\text{CMRR} = \frac{A_{DM}}{A_{CM}} = \frac{2000}{0.2} = 10000$$

$$\text{CMRR}_{\text{dB}} = 20 \log_{10} 10000 = 80\text{dB}$$

2. **Define Slew rate and what causes slew rate? [CO1-L1-April/May 2015]**

Slew rate is defined as the maximum rate of change of output voltage realized by a step input voltage and it is usually specified in units of V/ $\mu$ s. The slew rate of the op-amp is related to its frequency response.

**Causes of Slew rate:**

The slew rate is determined by a number of factors such as the amplifier gain, compensating capacitors and the change in polarity of output voltage. It is also a function of temperature and the slew rate generally reduced due to rise in temperature.

3. **Mention two advantages of active load over passive load in an operational amplifier.[CO1-L1-Nov/Dec 2015]**

To achieve high voltage gain without requiring large power supply voltage active load is used in an operational amplifier.

4. **Define input bias current and input offset current of an operational amplifier. [CO1-L1-Nov/Dec 2015]**

**Input Bias Current** : The average of the currents entering into the (-) input and (+) input terminals of an op-amp is called input bias current. Its value is 500nA for 741C.

**Input Offset Current** : The algebraic difference between the currents into the (-) input and (+) input is referred to as the input offset current. It is 200nA maximum for 741C.

5. **Find the maximum frequency for sine wave output voltage 10 V peak to peak with an op-amp whose slew rate is 1 V/ $\mu$ S. [CO1-H1-April/May 2016]**

To find maximum frequency :  $f_{max} = \text{Slew rate} / 2\pi m$   
 $= 1V/\mu s / 2\pi \times 10$

6. **Define CMRR of an op-amp. [CO1-L1]**

CMRR is defined as the ratio of the differential voltage gain to common mode voltage gain. It is expressed in decibels.  $CMRR = A_d/A_c$

7. **Differentiate the ideal and practical characteristics of an op-amp. [CO1-H1-May/June 2016]**

**Ideal Characteristics**

Open loop voltage gain,  $A_{OL} = \infty$

Input impedance,  $R_i = \infty$

Output impedance,  $R_o = 0$

Bandwidth,  $BW = \infty$

Zero offset, i.e.  $V_o = 0$  when  $V_1 = V_2 = 0$


**Practical Characteristics**

Open loop voltage gain,  $A_{OL} \neq \text{Infinity}$


Input impedance,  $R_i \neq \text{Infinity}$

Output impedance,  $R_o \neq 0$

 8. **Draw the block diagram of a general opamp. [CO1-L1-Nov/Dec 2016]**



 9. Draw the circuit diagram of a symmetrical emitter coupled differential amplifier. [CO1-L1- Nov/Dec 2016]



10. State the advantages of IC over discrete components [CO1-L1]

- Miniature in size and hence increased equipment density
- Improved performance
- Low cost due to batch processing
- High reliability and ruggedness
- Low power consumption
- Less vulnerability to parameter variations
- Increased operating speeds

11. Define Unity gain bandwidth of an op-amp. [CO1-L1]



The unity gain bandwidth is the bandwidth of the op-amp when the voltage gain is unity. The other terms are Closed-loop bandwidth, Gain-bandwidth product and Small-signal bandwidth.

For general purpose op-amps, the gain-bandwidth product is in the range of 1 to 20 MHz. For an op-amp with a single break frequency  $f_1$ , the gain-bandwidth product is constant and it can be written as Unity Gain Bandwidth  $UGB = A_o f_1$

**12. Mention the characteristics of an operational-amplifier. [CO1-L1]**

***a.c characteristics***

- i) Frequency response
- ii) Bandwidth
- iii) Slew rate.

***d.c characteristics***

- i) Input bias current
- ii) Input offset current
- iii) Input offset voltage
- iv) Thermal drift

**13. What are the applications of current sources? [CO1-L3]**

Transistor current sources are widely used in analog ICs both as biasing elements and as load devices for amplifier stages.

**14. Justify the reasons for using current sources in integrated circuits. [CO1-H2]**

Superior insensitivity of circuit performance to power supply variations and temperature.

More economical than resistors in terms of die area required providing bias currents of small value.

•When used as load element, the high incremental resistances of current source results in high voltage gain at low supply voltages.


**15. Why current mirror is used as a active load? [CO1-L1]**

A Current mirror can be used as an active load because it has high ac resistance.

**16. Explain the meaning of open loop and closed loop operation of an op-amp. [CO1-L1]**

In open loop mode, the output of the op-amp is at positive or negative saturation level. It does not operate linearly in this mode.

 **17. What is a practical op-amp? Draw its equivalent circuit. [CO1-L1]**



**18. What is a current mirror and why it is called so? [CO1-L2]**

A current mirror is a circuit block which functions to produce a copy of the current in one active device by replicating the current in second active device. An important feature of the current mirror is a relatively high output resistance which helps to keep the output current constant regardless of load conditions. Another feature of the current mirror is a relatively low input resistance which helps to keep the input current constant regardless of drive conditions. The current being 'copied' can be, and often is, a varying signal current.

**19. Define virtual ground property of Op-amp. [CO1-L1]**

Concept of virtual ground says that the two input terminals of the Op-amp are always at same potential. Thus if one terminal is grounded the other can be assumed to be at ground potential, which is called virtual ground.

**20. What are the frequency compensation techniques used in practice? [CO1-L3]**

Two methods of compensation techniques are used in practice :

- (1) External frequency compensation
- (2) Internal frequency compensation


The commonly used external compensation methods are :

- (i) Dominant-pole compensation (ii) Pole-zero(lag) compensation

### Part B
 
#### 1. Explain the significance of virtual ground in an opamp. [CO1-L1-Nov/Dec 2016]

The concept of a virtual ground is based on an ideal op-amp. When an op-amp is ideal, it has infinite open-loop voltage gain and infinite input resistance. Because of this, we can deduce the following ideal properties for the inverting amplifier : (1) Since  $R_{in}$  is infinite,  $i_2$  is zero. (2) Since  $A_{OL}$  is infinite,  $V_2$  is zero.



The Virtual ground shown in the figure means that the inverting input acts like a ground for voltage but an open for current. Virtual ground is very unusual. It is like half of a ground because it is a short for voltage but an open for current. In the figure, dashed line is shown between the inverting input and ground. The dashed line means that no current can flow to ground. Although virtual ground is an ideal approximation, it gives very accurate answers when used with very heavy negative feedback.

#### 2. Explain the operation of a current mirror circuit. [CO1- L1-Nov/Dec 2016]

A current mirror is a circuit block which functions to produce a copy of the current in one active device by replicating the current in second active device. An important feature of the current mirror is a relatively high output resistance which helps to keep the output current constant regardless of load conditions. Another feature of the current mirror is a relatively low input resistance which helps to

keep the input current constant regardless of drive conditions. The current being 'copied' can be, and often is, a varying signal current.

 


Fig. Basic Current Mirror circuit

### Features

- Generate an output current equal to input current multiplied by desired current gain factor
- Current gain is independent of input frequency.
- Output current independent of output voltage to common node.
- Provide bias current to circuits like differential amplifiers, transconductance amplifiers.
- Takes advantage of matching transistors on a chip.

### Operation

The figure shows the simplest form of current mirror circuit. Here, the transistors Q1 and Q2 are assumed identical.  $V_{BE1} = V_{BE2}$

The transistor Q1 is diode connected transistor, with its collector shorted to base, such that  $V_{CB} = 0$ . Q1 is operating in the active region.

Since the voltages  $V_{BE1}$  and  $V_{BE2}$  are equal, Q2 will also be in the active region and the collector currents  $I_{C1}$  and  $I_{C2}$  are equal.

Hence, this circuit is a current mirror. i.e., the current flowing through the left part of the circuit produces a mirror image of current in the right side. This principle forms the basis of most of the current source circuits and the active loads using current source circuits.

- 3. Draw the circuit of basic current mirror and explain its operation. Also discuss about, how current ratio can be improved in the basic current mirror. Sketch the improved circuit and explain. [CO1-L3]**

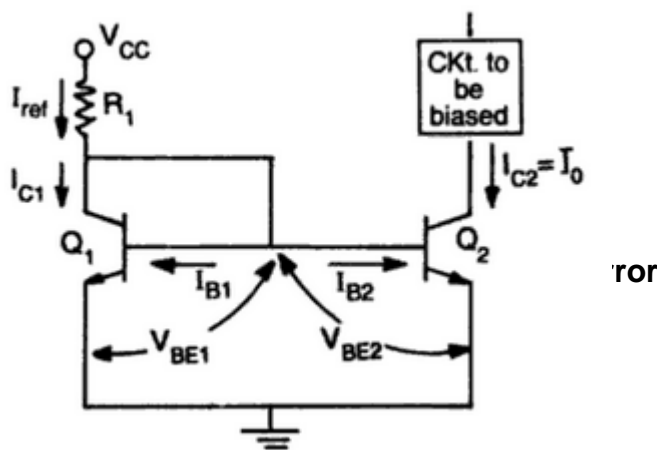


Fig. Basic Current Mirror circuit

A constant current source makes use of the fact that for a transistor in the active mode of operation, the collector current is relatively independent of the collector voltage. In the basic circuit shown in Fig. transistors Q1 and Q2 are matched as the circuit is fabricated using IC technology. It may be noted that bases and emitter of Q1 and Q2 are tied together and thus have the same  $V_{BE}$ . In addition, transistor Q1 is connected as a diode by shorting its collector to base.

The input current  $I_{ref}$  flows through the diode-connected transistor Q1 and thus establishes a voltage across Q1. This voltage in turn appears between the base and emitter of Q2. Since Q2 is identical to Q1, the emitter current of Q2 will be equal to emitter current of Q1 which is approximately equal to  $I_{ref}$ . Thus, we can say that as

long as Q2 is maintained in the active region, its collector current  $I_{c2} = I_o$  will be approximately equal to  $I_{ref}$ . Since the output current  $I_o$  is a reflection or mirror of the reference current  $I_{ref}$ , the circuit is often referred to as a current mirror.

This minor effect is however, valid only for large values of  $\beta$ . To study the effect of  $\beta$  on the operation of the current mirror circuit, we analyze it further.

### Analysis

The collector currents in and  $k2$  for transistors Q1 and Q2 can be approximately expressed as

$$I_{c1} = \alpha_F I_{ES} e^{V_{BE1}/V_T} \text{----- (1.1)}$$

$$I_{c2} = \alpha_F I_{ES} e^{V_{BE2}/V_T} \text{----- (1.2)}$$

From equations (1.1) and (1.2), we may write

$$\frac{I_{c2}}{I_{c1}} = e^{(V_{BE2} - V_{BE1})/V_T} \text{----- (1.3)}$$

since

$V_{BE1} = V_{BE2}$ , we obtain

$$I_{c2} = I_{c1} = I_o$$

Also since both the transistors are identical,  $\beta_1 = \beta_2 = \beta$

KCL at the collector of Q1, gives

$$I_{ref} = I_{c1} + I_{c2} + I_{B2} \text{----- (1.4)}$$

$$= I_{c1} + \frac{I_{c1}}{\beta_1} + \frac{I_{c2}}{\beta_2} = I_c \left(1 + \frac{2}{\beta}\right) \text{----- (1.5)}$$


Solving Equn (1.5),  $I_c$  may be expressed as

$$I_c = \frac{\beta}{\beta+2} I_{ref} \text{----- (1.6)}$$

Where  $I_{ref}$  from figure can be seen to be

$$I_{ref} = \frac{V_{CC} - V_{BE}}{R_1} = \frac{V_{CC}}{R_1} \text{ (as } V_{BE} = 0.7 \text{ is small) ----- (1.7)}$$


From equation (1.6), for  $\beta \gg 1$ ,  $\beta/(\beta+2)$  is almost unity and the output current  $I_o$  is equal to the reference current,  $I_{ref}$  which for a given  $R_1$  is constant. Typically  $I_o$  varies by about 3 % for  $50 \leq \beta \leq 200$ .

 

**Fig. Volt-ampere characteristics for transistor  $Q_2$**

**Improved Current Mirror**

However if  $\beta$  is small, then  $I_2$  cannot be equal to  $I_{C3}$ . In such case modified current mirror circuit is used. The improved current mirror circuit is shown in Fig.

 

**Fig.Improved Current Mirror Circuit**

### Analysis

Applying KCL at node 'n', we get,

$$I_1 = I_{C1} + I_{B3}$$

The two transistors  $Q_1$  and  $Q_2$  are identical

$$I_{B1} = I_{B2} = I_B$$

Hence the emitter current  $I_{E3}$  of transistor  $Q_3$  gets divided equally.

$$\text{Therefore, } I_{E3} = 2I_B$$

$$\text{Now, } I_{E3} = (1+\beta) I_{B3}$$

$$2I_B = (1+\beta) I_{B3}$$

$$\text{Now } I_{C1} = I_{E1} = \beta I_B$$

$$\text{and } I_{C2} = I_{E2} = \beta I_B$$

Substituting,

$$I_1 = \beta I_B + \frac{2I_B}{(1 + \beta)}$$

$$I_2 = I_B \left( \frac{\beta(1 + \beta) + 2}{(1 + \beta)} \right)$$

And

$$I_{C2} = \beta \left[ \frac{I_1(1 + \beta)}{\beta(1 + \beta) + 2} \right]$$

$$I_{C2} = I_{C1} = I_2 = \frac{I_1\beta(1 + \beta)}{\beta(1 + \beta) + 2}$$



**4. Briefly explain about constant current source. [CO1-L1-April/May 2015]**

A constant current source makes use of the fact that for a transistor in the active mode of operation, the collector current is relatively independent of the collector voltage. In the basic circuit shown in figure transistors Q1 and Q2 are matched as the circuit is fabricated using IC technology. It may be noted that bases and emitter of Q1 and Q2 are tied together and thus have the same  $V_{BE}$ . In addition, transistor Q1 is connected as a diode by shorting its collector to base. The input current  $I_{ref}$  flows through the diode-connected transistor Q1 and thus establishes a voltage across Q1. This voltage in turn appears between the base and emitter of Q2. Since Q2 is identical to Q1, the emitter current of Q2 will be equal to emitter current of Q1 which is approximately equal to  $I_{ref}$ . Thus, we can say that as long as Q2 is maintained in the active region, its collector current  $I_{c2} = I_o$  will be approximately equal to  $I_{ref}$ . Since the output current  $I_o$  is a reflection or mirror of the reference current  $I_{ref}$ , the circuit is often referred to as a current mirror.

**5. With a schematic diagram, explain the effect of  $R_E$  on CMRR in differential amplifier. [CO1-H1-May/June 2016]**

To improve the CMRR, the common mode gain  $A_c$  must be reduced. The common mode gain  $A_c$  approaches zero as  $R_E$  tends to infinity. This is because  $R_E$  introduces a negative feedback in the common mode operation which reduces the common mode gain  $A_c$ . Thus higher the value of  $R_E$ , lesser is the value of  $A_c$  and higher is the value of CMRR. The differential gain  $A_d$  is not dependent on  $R_E$ . But practically  $R_E$  can not be selected very high due to certain limitations such as,

1. Large  $R_E$  needs higher biasing voltage to set the operating Q point of the transistors.
2. This increases the overall chip area. Hence practically instead of increasing  $R_E$  various other methods are used which provide effect of increased  $R_E$  without any

limitations. Such two methods are -1. Constant current bias method. 2. Use of current mirror circuit.

The other method used to increase  $A_d$  to improve CMRR is called use of an active load.

**6. Explain with a circuit diagram, the working of BJT-emitter coupled differential amplifier, also explain the concept of Active load and sketch the relevant circuit diagram. [CO1-L2]**

The main purpose of the difference amplifier stage is to provide high gain to the difference-mode signal and cancel the common-mode signal. The relative sensitivity of an op-amp to a difference signal as compared to common-mode signal is called common-mode rejection ratio (CMRR) and gives the figure of merit of the differential amplifier. The higher the value of CMRR, better is the op-amp. Another requisite of a good op-amp is that it should have high input impedance. A cascaded dc amplifier can provide high gain down to zero frequency as it has no coupling capacitor. However, such an amplifier suffers from the major problem of drift of the operating point due to temperature dependency of  $\beta$ ,  $V_{BE}$  and  $I_{CBO}$  of the transistor. This problem can be eliminated by using a balanced or differential amplifier as shown in Fig. .

It may be seen that it is essentially an emitter-coupled differential amplifier. This circuit has low drift on account of symmetrical construction. It can be designed to give high input resistance. It has two input terminals and it may be seen easily that terminal B2 is the inverting input terminal since transistor Q2 provides a phase shift of  $180^\circ$  for the output taken at the collector of Q2. Obviously, B1 is the non-inverting input terminal. A differential amplifier of the type shown in Fig. can be used in four different configurations depending upon the number of input signals used and the way output is taken. These four configurations are:

(i) Differential-input, differential-output or Dual-input balanced-output (ii) Differential-input, single ended-output (iii) Single-input, differential output (iv) Single-

input, single ended-output If signal is applied to both the inputs, then it is differential input or Dual input and the difference of signals applied to the two inputs gets amplified. In many applications a single input is only used as we shall see later. Similarly, if output voltage is measured between two collectors then it is a differential output. This is also referred to as a balanced output, as both collectors are at the same d.c. potential w.r.t. ground.

 


Fig. Basic differential amplifier

 


Fig. Differential pair with common mode input signal  $V_{CM}$

 


Fig. Differential pair with 'large' differential input signal

**7. Define CMRR. Draw the circuit of an Op-amp differential amplifier and give the expression for CMRR. [CO1- L1]**

The Common Mode Rejection Ratio (CMRR) is defined as the ratio of the differential voltage gain  $A_{dm}$  to common voltage gain  $A_{cm}$  and is generally expressed in decibels.

$$\text{CMRR in decibels (dB)} = 20 \log_{10} \left( \frac{A_D}{A_C} \right)$$

8. Compare the features of ideal and practical opamp circuit. [CO1-H1- Nov/Dec 2016]

Ideal Op-amp Characteristics	Practical Op-amp Characteristics
Open loop voltage gain, $A_{OL} = \infty$	Open loop voltage gain, $A_{OL} \neq \text{Infinity}$
Input impedance, $R_i = \infty$	Input impedance, $R_i \neq \text{Infinity}$
Output impedance, $R_o = 0$	Output impedance, $R_o \neq 0$
Bandwidth, $BW = \infty$	
Zero offset, i.e. $V_o = 0$ when $V_1 = V_2 = 0$	

9. With a neat block diagram, explain the general stages of an OP-AMP IC. [CO1-L1]

 


Fig. Internal block schematic of op-amp

### Input stage

The input stage requires high input impedance to avoid loading on the sources. It requires two input terminals. It also requires low output impedance. All such requirements are achieved by using the dual input, balanced output differential amplifier as the input stage. The function of a differential amplifier is to amplify the difference

between the two input signals. The differential amplifier has high input impedance. This stage provides most of the voltage gain of the amplifier.

### **Intermediate Stage**

The output of the input stage drives the next stage which is an intermediate stage. This is another differential amplifier with dual input, unbalanced i.e. single ended output. The overall gain requirement of the op-amp is very high. The input stage alone cannot provide such a high gain. The main function of the intermediate stage is to provide an additional voltage gain required. Practically, the intermediate stage is not a single amplifier but the chain of cascaded amplifiers called multistage amplifiers.

### **Level Shifting Stage**


All the stages are directly coupled to each other. As the op-amp amplifies d.c. signals also, the coupling capacitors are not used to cascade the stages. Hence the d.c. quiescent voltage level of previous stage gets applied as the input to the next stage. Hence stage by stage d.c. level increases well above ground potential. Such a high d.c. voltage level may drive the transistors into saturation. This further may cause distortion in the output due to clipping. This may limit the maximum a.c. output voltage swing without any distortion. Hence before the output stage, it is necessary to bring such a high d.c. voltage level to zero volts with respect to ground.

The level shifter stage brings the d.c. level down to ground potential, when no signal is applied at the input terminals. Then the signal is given to the last stage which is the output stage. The buffer: is usually an emitter follower whose input impedance is very high. This prevents loading of the high gain stage.
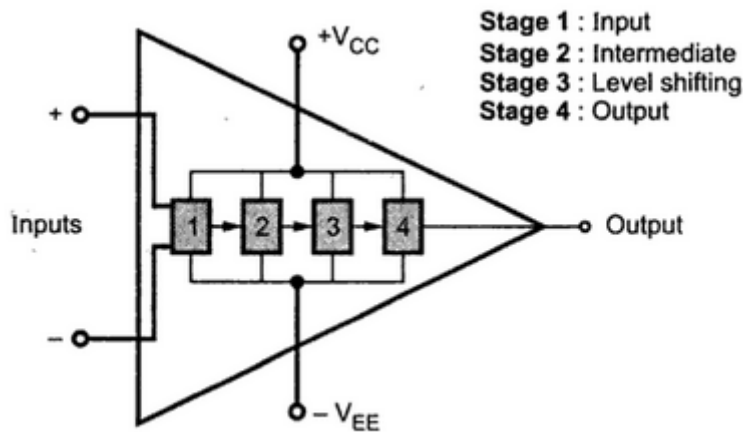
### **Output Stage**

The basic requirements of an output stage are low output impedance, large a.c. output voltage swing and high current sourcing and sinking capability. The push-pull complementary amplifier meets all these requirements and hence used as an output

stage. This stage increases the output voltage swing and keeps the voltage swing symmetrical with respect to ground. The stage raises the current supplying capability of the op-amp. In short, the overall block diagram can be shown as in the Fig below.



**10. Assuming a slew rate for 741 IC is 0.5 v/μs. What is the maximum undistorted sinewave that can be obtained for 12 V peak. [CO1-H3-Nov/Dec 2016]**

Solution :

The given slew rate for 741 is 0.5 v/μs.

For the sine wave of 12V peak,

$$F_{\max} = \text{Slew rate} / 2\pi V_m$$

$$= 0.5 \text{ v}/\mu\text{s} / 2\pi \times 12 \text{ V}$$

$$= 6.63 \text{ kHz}$$

**11. What is the need for frequency compensation in an OPAMP? Briefly explain the techniques used for frequency compensation. [CO1-L3-April/May 2015]**

Concept of frequency compensation : In applications where one desires large bandwidth and lower closed loop gain suitable compensation techniques are used.

Two used compensation techniques are used : External compensation and Internal compensation.

External frequency compensation : Two methods are used in external compensation. They are : Dominant pole compensation and Pole-zero (lag) compensation.

**Dominant pole compensation** : The dominant pole means the pole with magnitude much smaller than the existing poles. And hence the break frequency of the compensating network is the smallest compared to the existing frequencies.


 


Fig. Dominant pole compensation

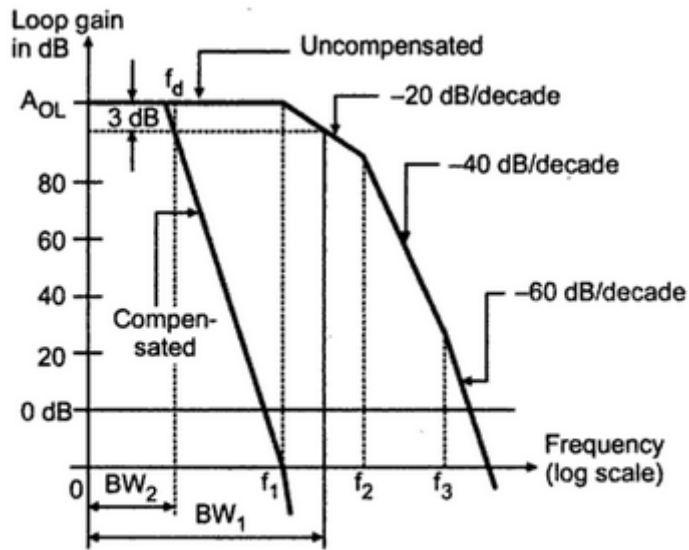



**Fig. Dominant pole compensation**

It can be observed from the plot that 3 dB down bandwidth for noncompensated system is  $BW_1$  while for compensated it becomes  $BW_2$ . There is drastic reduction in the bandwidth.

**Advantages :** i) As the noise frequency components are outside the smaller bandwidth, the noise immunity of the system improves. ii) Adjusting value of  $f_d$ , adequate phase margin and the stability of the system is assured.

**Disadvantage :** i) The only disadvantage of the method is that the bandwidth reduces drastically.

### **Pole zero compensation**

In this method the transfer function  $A$  is modified by adding a pole and a zero with the help of compensating network. The zero is added at higher frequency and the pole is added at a lower frequency.

 


Fig.Pole zero compensation.

**12.How do the open loop gain and the closed loop gain of an op-amp differ?**  
**[CO1-L2-April/May 2015]**

### Open loop configuration

Open loop gain of op-amp is very large, very small input voltage drives the op-amp voltage to the saturation level. Thus in open loop configuration, the output is at its positive saturation voltage ( $+V_{sat}$ ) or negative saturation voltage ( $-V_{sat}$ ) depending on which input  $V_1$ , or  $V_2$  is more than the other. For a.c. input voltages, output may switch between positive and negative saturation voltages. The Fig. shows the voltage transfer curve which indicates that in open loop mode, the input range of op-amp is very very small in AV or mV, for which op-amp behaves linearly. This range is indicated as a-b in the Fig.

**Closed Loop Operation of Op-amp :** The op-amp cannot operate linearly in open loop mode. But the utility of an op-amp can be considerably increased by operating it in closed loop mode. The closed loop operation is possible with the help of feedback. The feedback allows to feed some part of the output back to the input terminals. In the linear applications, the op-amp is always used with negative feedback. The negative feedback helps in controlling gain.

 


Fig. Op-amp with negative feedback

The advantages of negative feedback are :

i) It reduces the gain and makes it controllable. ii) It reduces the possibility of distortion. iii) It increases the bandwidth i.e. frequency range. iv) It increases the input resistance of the op-amp. v) It decreases the output resistance of the op-amp. vi) It reduces the effects of temperature, power supply on the gain of the circuit. The countless simple circuits using one or more op-amps can be designed with the help of negative feedback. Such op-amp applications are classified as linear and nonlinear type. In linear applications, output voltage varies linearly with respect to the input voltage. Some of the linear applications are inverting amplifier, noninverting amplifier, voltage follower, summing amplifier, difference amplifier etc. The concept of virtual ground plays an important role in analysing the various application circuits.

## Unit - II

### Applications of Operational Amplifiers

#### Part A

#### 1. What is hysteresis and mention the purpose of hysteresis in a comparator? [CO2-L1-April/May 2015]

[CO2-L1-April/May 2015]


The regenerative comparator or Schmitt trigger exhibits hysteresis, a deadband condition. It means, when the input of the circuit exceeds  $V_{ut}$  (upper threshold),  $V_o$  switches from  $+V_{sat}$  to  $-V_{sat}$  and comeback to original state  $+V_{sat}$  when the input reaches  $V_{it}$  (Lower threshold). The hysteresis voltage is equal to the difference between upper threshold voltage and lower threshold voltage.

#### 2. What is the difference between normal rectifier and precision rectifier? [CO2-L1-April/May 2015]

[CO2-L1-April/May 2015]

In a normal rectifier ordinary diodes are used for rectification purpose which offers cut-in voltage at higher order range whereas in the case of precision rectifier precision diodes are used for rectification purpose in order to operate them for cut-in voltages in the order of micro volts.

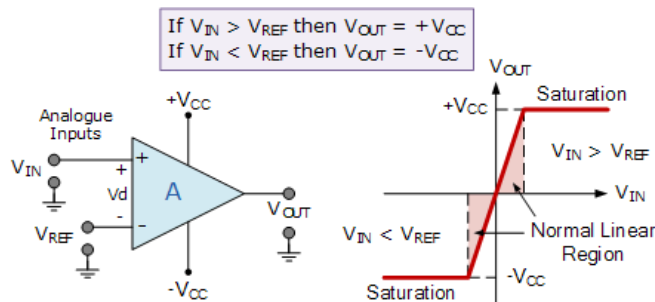
#### 3. Draw the circuit diagram of a comparator. Mention its applications. [CO-L2-May/June 2016]



### Applications of Comparator

- Zero crossing detector
- Window detector
- Phase detector
- Timing marker generator

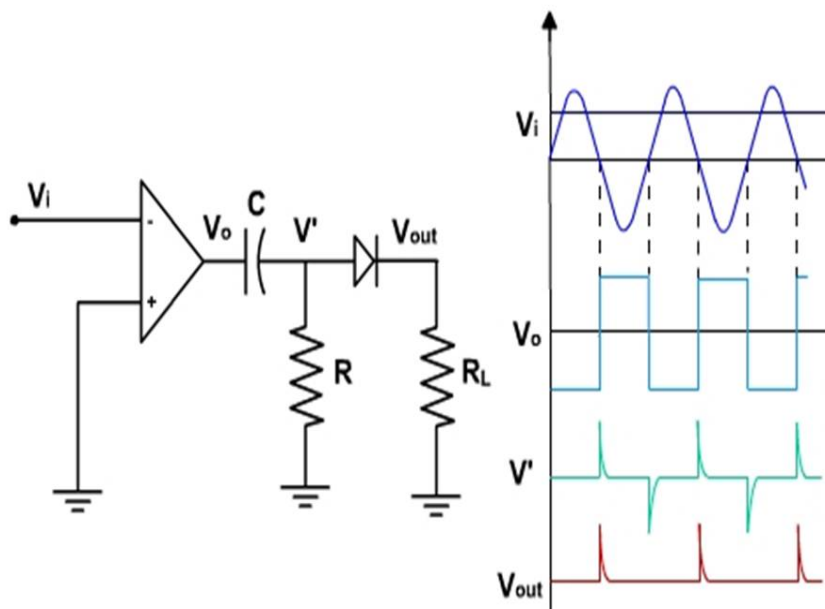**4. Draw the circuit diagram of a peak detector with waveforms. . [CO2—H1-  
Nov/Dec2016]**



**5. Mention some of the linear applications of op – amps. [CO2-L1]**

Adder, subtractor, voltage –to- current converter, current –to- voltage converters, instrumentation amplifier, analog computation, power amplifier, etc are some of the linear opamp circuits.

**6. Mention some of the non – linear applications of op-amps.[CO2—H1-Nov/Dec2016]**

Rectifier, peak detector, clipper, clamper, sample and hold circuit, log amplifier, anti – logamplifier, multiplier are some of the non – linear op-amp circuits.

**7.What is the need for an instrumentation amplifier? [CO2-L1]**

In a number of industrial and consumer applications, the measurement of physical quantities is usually done with the help of transducers. The output of transducer has to be amplified So that it can drive the indicator or display system. This function is performed by an instrumentation amplifier.

**8 List the features of instrumentation amplifier. [CO2-L1]**

- High gain accuracy
- High CMRR
- High gain stability with low temperature co-efficient
- Low dc offset
- Low output impedance

**9. What are the applications of V-I converter? [CO2-L1]**

- Low voltage dc and ac voltmeter
- L E D
- Zener diode tester

**10. What do you mean by a precision diode? [CO2-L1]**

The major limitation of ordinary diode is that it cannot rectify voltages below the cut – in voltage of the diode. A circuit designed by placing a diode in the feedback loop of an

op – amp is called the precision diode and it is capable of rectifying input signals of the order of millivolt.

**11. Write down the applications of precision diode. [CO2-L2]**

- Half - wave rectifier
- Full - Wave rectifier
- Peak – value detector
- Clipper
- Clamper

**12. List the applications of Log amplifiers. [CO2-L2]**

- Analog computation may require functions such as  $\ln x$ ,  $\log x$ ,  $\sin hx$  etc. These functions can be performed by log amplifiers
- Log amplifier can perform direct dB display on digital voltmeter and spectrum analyzer
- Log amplifier can be used to compress the dynamic range of a signal

**13. What are the limitations of the basic differentiator circuit? [CO2-L2]**

At high frequency, a differentiator may become unstable and break into oscillations. The input impedance decreases with increase in frequency, thereby making the circuit sensitive to high frequency noise.

**14 Write down the condition for good differentiation. [CO2-L2]**

For good differentiation, the time period of the input signal must be greater than or equal to  $R_f C_1$

$$T > R_f C_1$$

Where,  $R_f$  is the feedback resistance  $C_f$  is the input capacitance

**15.What is a comparator? [CO2-L2]**

A comparator is a circuit which compares a signal voltage applied at one input of an op-amp with a known reference voltage at the other input. It is an open loop op - amp with output  $+V_{sat}$

**16.What are the applications of comparator? [CO2-L2]**

- Zero crossing detectors
- Window detector
- Time marker generator
- Phase detector

**17.What is a Schmitt trigger? [CO2-L2]**

Schmitt trigger is a regenerative comparator. It converts sinusoidal input into a square wave output. The output of Schmitt trigger swings between upper and lower threshold voltages, which are the reference voltages of the input waveform.

**18.What are the requirements for producing sustained oscillations in feedback circuits?**

For sustained oscillations,

- The total phase shift around the loop must be zero at the desired frequency of oscillation,  $f_o$ .
- At  $f_o$ , the magnitude of the loop gain  $|\beta A|$  should be equal to unity

**19.Mention any two audio frequency oscillators. [CO2-L2]**

- RC phase shift oscillator
- Wein bridge oscillator



**20. What is a filter? [CO2-L1]**

Filter is a frequency selective circuit that passes signal of specified band of frequencies and attenuates the signals of frequencies outside the band

**21. What are the demerits of passive filters? [CO2-L1]**

Passive filters work well for high frequencies. But at audio frequencies, the inductors become problematic, as they become large, heavy and expensive. For low frequency applications, more number of turns of wire must be used which in turn adds to the series resistance degrading inductor's performance i.e., low Q, resulting in high power dissipation.

**22. What are the advantages of active filters? [CO2-L1]**

- Active filters use op-amp as the active element and resistors and capacitors as passive elements.
- By enclosing a capacitor in the feedback loop, inductorless active filters can be obtained
- Op-amp used in non-inverting configuration offers high input impedance and low output impedance, thus improving the load drive capacity.

**23. Mention some commonly used active filters. [CO2-L1]**

- Low pass filter
- High pass filter
- Band pass filter
- Band reject filter.

**24. What is frequency scaling? ? [CO2-L1]**

Once the filter is designed, sometimes it is necessary to change the value of cut-off frequency. The method used to change the original cut-off frequency to new cut-off frequency is called frequency scaling.

**25. What is Voltage follower? ? [CO2-L1]**

- A circuit in which the output voltage follows the input voltage is called voltage follower circuit.
- In Op-amp if the inverting input and the output terminals are shorted and if any signal is applied at the non-inverting terminal, it appears at the output without any change.
- It is also called as source follower, unity gain amplifier, buffer amplifier or isolation amplifier.

**26..Define logarithmic and antilogarithmic amplifier. ? [CO2-L1]**

- The Op-amp circuit in which the output is proportional to the logarithmic of the input is called logarithmic amplifier. It employs a diode or a transistor in the negative feedback path.
- The Op-amp circuit in which the output is proportional to the antilogarithmic of the input is called antilogarithmic amplifier. It employs a diode or a transistor in the input stage.

### Part B


**1. With a neat circuit diagram and mathematical expression explain the following operational amplifier applications.[CO2-L1-Nov/Dec2012]**

**(i) Scale changer (ii) Sign changer and (iii)Phase shift circuits**

**SCALE CHANGER( INVERTER)**

In the basic inverting amplifier of Fig. 4.1, if the ratio  $R_f/R_i = K$ . where  $K$  is a real constant, then the closed loop gain  $A_{CL} = -K$ . The circuit thus could be used to multiply by a constant factor if  $R_f$  and  $R_i$  are selected as precision resistors.

For  $R_f = R_i$ ,  $A_{CL} = -1$  and the circuit is called an inverter, i.e., the output is  $180^\circ$  out of phase with respect to input though the magnitudes are same.

 

**Fig.Sign changer**


**SIGN CHANGER(PHASE INVERTER):**

Figure shows the basic inverting amplifier configuration using an op-amp with input impedance  $Z_1$  and feedback impedance  $Z_f$ . If the impedances  $Z_1$  and  $Z_f$  are equal in magnitude and phase, then the closed-loop voltage gain is  $-1$ , and the input signal will undergo a  $180^\circ$  phase shift at the output

Hence, such a circuit is also called phase inverter. If two such amplifiers are in Fig. (Inverting op-amp) with connected in cascade, then the output from voltage shunt feedback the second stage is the same as the input signal without any change of sign.

Hence, the outputs from the two stages are equal in magnitude but opposite in phase and such a system is an excellent paraphase amplifier.

**Fig: Inverting op-amp with voltage shunt feedback**

 

### PHASE SHIFT CIRCUITS

The phase shift circuits produce phase shifts that depend on the frequency and maintain a constant gain. These circuits are also called constant-delay filters or all-pass filters.

Those constant delay refers to the fact that the time difference between input and output remains constant when frequency is changed over a range of operating frequencies.

This is called all-pass because normally a constant gain is maintained for all the frequencies within the operating range. The two types of circuits, for lagging phase angles and leading phase angles are discussed below.

➤ Referring above Fig, if  $Z_1$  and  $Z_f$  are equal in magnitude and differ in angle, then the op-amp shifts the phase of the sinusoidal input voltage. Any phase shift between  $-180^\circ$  and  $+180^\circ$  can be obtained by varying  $Z_1$  and  $Z_f$ .

Example Phase-Lag Circuit

#### Phase-Lag Circuit

Figure . shows the phase-lag circuit constructed using an op-amp, connected in both inverting and non-inverting modes.

To analyze the circuit operation, it is assumed that the input voltage  $v_i$  drives a simple inverting amplifier with inverting input applied at (-) terminal of op-amp and a non-inverting amplifier with a low-pass filter. It is also assumed that inverting gain is -1 and non-inverting gain after the low pass circuit is  $1 + R_f/R_1 = 1 + 1 = 2$ , Since  $R_f = R_1$ .

 


Fig. (a) Phase lag circuit

 


Fig. (b) Bode plot for the phase-lag circuit

For the circuit shown in figure(a), it can be written as

$$V_o = -V_i(j\omega) + 2(1/(1 + j\omega RC)) V_i(j\omega)$$

$$V_o(j\omega) / V_i(j\omega) = (1 - j\omega RC) / (1 + j\omega RC)$$

The relationship is complex as defined by above Eqn. , and it shows that it has both magnitude and phase. Since the numerator and denominator are complex conjugates, their magnitudes are identical and the overall phase angle equals the angle of numerator less the angle of the denominator. The phase angle is then given by

$$\theta = -\tan^{-1}(\omega RC) - \tan^{-1}(\omega RC) = -2 \tan^{-1}(\omega RC)$$

here, when  $\omega=0$ , the phase angle approaches zero, when  $\omega=\infty$ , the phase angle approaches  $-180^\circ$ .

The equation(4) can be written as

$$\theta = -2 \tan^{-1}(f/f_0)$$

When the frequency  $f_0$  is given by

$$f_0 = 1/2\pi RC$$

Here, when  $f = f_0$  in equation 4, the phase angle  $\theta = -90^\circ$ , the bode plot for the phase lag circuit is shown in figure.

## 2. With neat diagram explain the operation of voltage follower with example. [CO2-L1-Nov/Dec 2012]

### Definition:

The output voltage is equal to input voltage, both in magnitude and phase

In the non-inverting amplifier, if  $R_f = 0$  and  $R_1 = \infty$ , we get modified circuit as voltage follower.

$$V_o = V_i$$

 


Fig. Voltage follower

- That is, the output voltage is equal to input voltage, both in magnitude and phase. In other words, we can also say that the output voltage follows the input voltage exactly. Hence, the circuit is called a voltage follower.
- The use of the unity gain circuit lies in the fact that its input impedance is very high (i.e.  $M\Omega$  order) and output impedance is zero. Therefore, it draws negligible current from the source. Thus a voltage follower may be used as buffer for impedance matching, that is, to connect a high impedance source to a low impedance load.

## 3. Explain in detail about I to V converters. [CO2- L2-April/May 2016]

### Current to voltage converter:

#### Definition:

In this type the output voltage is proportional to the input current. It accepts an input current  $I_i$  and yields an output voltage  $V_o$  such that  $V_o = A_i I_i$ , where

A- gain of the circuit and measured in ohms. Because of this I-V converters are also called transresistance amplifiers.

Fig shows the current to voltage converter :

 


Fig. Voltage to Current converter

The node A is virtual ground as node B is grounded. Hence  $V_A=0$


The circuit is also referred as current controlled voltage source (CCVS). If the resistance in the circuit is replaced by the impedance  $Z$ , the circuit is called trans-impedance amplifier.

#### Applications of I/V converter:

- One of the most applications of I/V converters is in connection with current type photo detectors such as photodiodes, photoFETs and photomultipliers.
- Another application of I/V conversion is current output digital to analog converter.

#### Photodiode detector:

Fig shows the connection diagram of widely used photo detectors, photodiode.

 

-Fig. Photo diode as photo detector

-The photodiode produces electrical current in response to incident light. This current flows through R. The voltage across R, the output voltage is proportional to diode current.

### PhotoFET detector:

-Fig shows another photo detector circuit with photoFET:

 


Fig. Photodetector circuit with photoFET

The photo FET is similar to conventional junction FET, the exception of a lens for focusing light onto the gate function. On application of light photons enter the gate area and excite valence electrons into conduction band.

The photon-excited current carries causes a small current  $\Delta I_G$  resulting in large current change  $\Delta I_D$  results change the voltage drop across R and hence output voltage. Thus op-amp circuit acts as I/V converter and gives the indication of light in terms of voltage.

#### 4. Draw and explain the circuit of a voltage to current converter if the load is

(i) Floating            (ii) Grounded.            [CO2- L2-April/May 2016 &Nov/Dec 2015]



In a voltage to current converter the output load current is proportional to the input voltage. **Types of V to I converters**

(i) Floating type and

(ii) Grounded type.

In floating type V to I converter  $R_L$  is not connected to the ground whereas in grounded type one end of  $R_L$  is connected to the ground.

**Voltage to current converter with floating load:**

The fig shows the voltage to current converter in which load resistor  $R_L$  is floating

 


Fig. Floating load V-I converters

-As input current of op-amp is zero

$$I_L = I_i = V_i/R_i$$

$$I_L \propto V_i$$

- Thus the load current is always proportional to input voltage and circuit works as voltage to current converter. If the load is a capacitor, it will charge or discharge at a constant rate. Hence such converter circuits are used to generate the saw tooth or triangular waveforms. -The proportionality constant is  $1/R_f$  hence the circuit is called transconductance amplifier. It is also called as voltage controlled current source (VCCS).

- The expression  $I_L = V_i/R_1$  holds the type of the load. It can be linear or non linear or it can have time- dependent characteristics.

### Voltage to current converter with grounded load:

- When one end of the load is grounded it is no longer possible to place the load within feedback loop of the op-amp .The fig shows a voltage to current converter in which one end of load resistor  $R_L$  is grounded. It is also known as 'Howland Current converter' from the name of inverter.

- The analysis of circuit is first determining the voltage  $V_1$  at the noninverting input terminal and then establishing relation between  $V_1$  and the load current.

 


Fig.V to I converter with grounded load

### Applications of V-I converter:

- Low voltage D.C. Voltmeter
- Low voltage A.C. voltmeter
- Diode tester and match finder
- Zener diode tester

**5. Draw the circuit diagram of an instrumentation amplifier and explain its operation. List few applications. [CO2- H1-May/June 2016]**

The measurement of the physical quantities is carried with the help of a device called as transducer. A transducer is a device which converts one form of energy into another.

For example: A Thermocouple converts the heat energy into an electrical energy, microphone converts the sound energy into an electrical energy, Such a proportional electrical signal output from a transducer can be further used to control or operate the other parts of the system.

But most of the transducer outputs are of very low level signals. Such a low level signals are not sufficient to drive the next stage of system. One more difficulty is the transducer used may be mounted on pieces of equipment which are remote from the control location. Long connecting wires are required to get transducer output to the control room. Such a signal may be very low. Hence before the next stage, it is necessary to amplify the level of such signal rejecting the noise and interference. Hence single ended amplifier like high gain emitter amplifier is not suitable to amplify such signal. For rejection of noise, such amplifiers must have high CMRR. Hence a special amplifier is used to amplify such signals.

The special amplifier which is used for such a low level amplification with high CMRR, high input impedance to avoid loading, low power consumption and some other features is called as instrumentation amplifier.

The instrumentation amplifier is also called data amplifier and is basically a difference amplifier. The expression for its voltage gain is generally of the form,

$$A = \frac{V_o}{V_2 - V_1}$$

where  $V_o$  = Output of the amplifier

$V_2 - V_1$  = Differential input which is to be amplified


**Requirements of a good instrumentation amplifier:**

- Finite, accurate and stable gain :
- Easier gain adjustment
- High input impedance
- Low output impedance
- High CMRR.
- Low power consumption
- Low thermal and time
- High slew rate.
- The amplifier must have differential input so that it can be amplified.

**Instrumentation amplifiers with Two Op-amps:**

- The high input impedance is achieved by using voltage follower circuit. Such a high input impedance along with variable voltage gain can be achieved by using a two op-amp instrumentation amplifier circuit.

-Such an amplifier circuit is shown below:

 


**Fig. Instrumentation amplifier using two op-amps**

**Advantages:**

The advantages of this circuit are:

- The gain variation is easy and precise.
- The CMRR value is completely independent of the setting of resistance  $R_3$ . Hence with the precision ratios for  $R_2 / R_1$  the gain can be changed without degrading the performance of the amplifier.
- The resistance  $R_3$  is separate from accurately matched resistances  $R_1$  and  $R_2$  which are required for symmetric arrangement.
- The main problem is that the resistances  $R_1$  and  $R_2$  must be accurately matched.
- Another limitation of the circuit is that it treats the input asymmetrically. The input  $V_1$  has to propagate through  $A_2$  before reaching to  $A_1$ .
- Due to additional delay common mode components of the two signals will no longer cancel out with each other at high frequencies. This decreases CMRR with frequency.
- The typical set of values of  $R_1$ ,  $R_2$  and  $R_3$  is  $R_1 = 9\text{K}\Omega$   $R_2 = 3\text{K}\Omega$   $R_3 = 0.5\text{K}\Omega$  to  $9\text{K}\Omega$
 
### Three Op-amp Instrumentation Amplifier:



The op-amps  $A_1$  and  $A_2$  are the non inverting amplifiers forming the input or first stage stage of the instrumentation amplifier. The op-amp  $A_3$  is the normal difference amplifier forming an output stage of the amplifier. The block diagram representation of the three op-amp instrumentation amplifier in the figure:

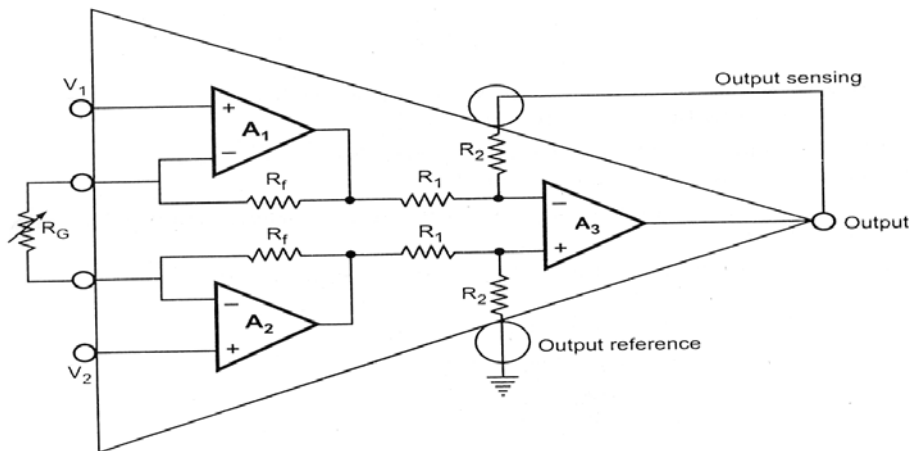


Fig. Block diagram representation.

**Analysis of 3 op amp instrumentation amplifier:**

It can be seen that the output state is a standard basic difference amplifier. So if the output of the op-amp A<sub>1</sub> is V<sub>o1</sub> and the output of the op-amp A<sub>2</sub> is V<sub>o2</sub> we can write

$$V_o = \frac{R_2}{R_1} (V_{o2} - V_{o1})$$

Let us find out the expression for V<sub>o2</sub> and V<sub>o1</sub> in terms of V<sub>1</sub>, V<sub>2</sub>, R<sub>f1</sub> and R<sub>f2</sub> and R<sub>G</sub>. Consider the first stage in the figure:

 


Fig.

The node A potential of op-amp A<sub>1</sub> is V<sub>1</sub>. From the realistic assumption the potential of node B is also V<sub>1</sub>. And hence potential as G is also V<sub>1</sub>. The node D potential of op-amp

$A_2$  is  $V_2$ . From the assumption the potential of node C is also  $V_2$ . And hence potential of H is also  $V_2$ . The input current of op-amp  $A_1$  and  $A_2$  both are zero. Hence current  $I$  remains same through  $R_{f1}$ ,  $R_g$  and  $R_{f2}$ .

### **Advantages:**

The advantages of three op-amp instrumentation amplifier circuit:

- With the help of variable resistance  $R_G$ , The gain can be easily varied, without disturbing the symmetry of the circuit.
- Gain depends on the external resistances and hence can be adjusted accurately and made stable by selecting high quality resistances.
- The input impedance depends on the input impedance of non-inverting amplifiers which is extremely high.
- The output impedance is the output impedance of the op-amp  $A_3$  which is very low. This is an required by any instrumentation amplifier.
- The CMRR of the op-amp  $A_3$  is very high and most of the common mode signal will be rejected.
- By trimming one of the resistances of the output stage, CMRR can be made extremely high as required by a good instrumentation amplifier.
- Thus the circuit satisfies all the requirements of a good instrumentation amplifier and hence very commonly used in practical applications.

### **Applications of Instrumentation Amplifier:**

#### 1. Data acquisition system

The instrumentation amplifier along with the transducer bridge can be used in many applications. The general form of such systems can be called as 'Data Acquisition System' and can be represented in the block diagram form as shown in the figure:

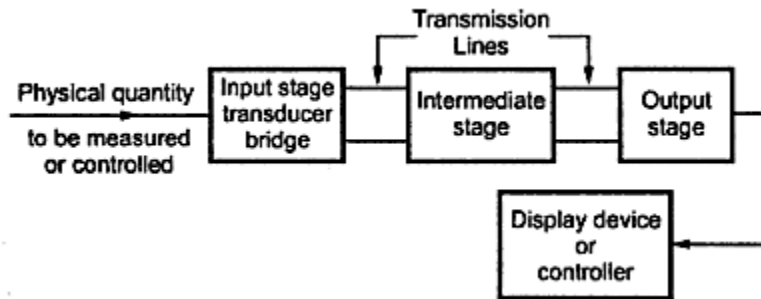


Fig. Data acquisition system


The input stage is a transducer bridge which converts physical quantity to be measured into an electrical signal. The signal is then carried out to an instrumentation amplifier, with help of transmission lines. The output stage consists of display device controller or some type of signal conditioning circuit such as ADC etc.

2. Temperature controller
3. Temperature Indicator
4. Light intensity meter
5. Analog weight scale
 
### 6. Write short notes on : Integrator (6) [CO2- L3- Nov/Dec 2016]

Definition: A circuit in which the output voltage waveform is the integral of the input voltage waveform is the integrator or Integration Amplifier. Such a circuit is obtained by using a basic inverting amplifier configuration if the feedback resistor  $R_F$  is replaced by a capacitor  $C_F$ .





The expression for the output voltage  $V_o$  can be obtained by KVL eqn at node  $V_N$ .

$$I_B = i_1 + i_F \text{ ----- (1)}$$

$$\frac{V_{in} - V_N}{R_1} + C_F \frac{d(V_o - V_N)}{dt} = 0$$

$$\text{sub, } V_N = 0$$

$$\frac{V_{in}}{R_1} + C_F \frac{d(V_o)}{dt} = 0$$


$$C_F \frac{d(V_o)}{dt} = -\frac{V_{in}}{R_1}$$

$$\frac{d(V_o)}{dt} = -\frac{1}{R_1 C_F} \int V_{in} dt \text{ ----- (2)}$$

Eqn (2) indicates that the output is directly proportional to the negative integral of the input volts and inversely proportional to the time constant  $R_1 C_F$ .


Ex: If the input is sine wave -> output is cosine wave.

 If the input is square wave -> output is triangular wave.



These waveform with assumption of  $R_1 C_f = 1$ ,  $V_{out} = 0V$  (i.e)  $C = 0$ .

**Practical Integrator:**

 

Practical Integrator to reduce the error voltage at the output, a resistor  $R_F$  is connected across the feedback capacitor  $C_F$ .

➤ Thus  $R_F$  limits the low frequency gain and hence minimizes the variations in the output voltages. The frequency response of the basic integrator, shown from this fb is the frequency at which the gain is dB and is given by,

$$f_b = \frac{1}{2\pi R_F C_F}$$

Both the stability and low frequency roll-off problems can be corrected by the addition of a resistor  $R_F$  in the practical integrator.

Stability -> refers to a constant gain as frequency of an input signal is varied over a certain range.

Low frequency -> refers to the rate of decrease in gain roll off at lower frequencies.

From the fig of practical Integrators,  $f$  is some relative operating frequency and for frequencies  $f$  to  $f_a$  to gain  $R_F / R_1$  is constant. After  $f_a$  the gain decreases at a rate of 20dB/decade or between  $f_a$  and  $f_b$  the circuit act as an integrator. The gain limiting frequency  $f_a$  is given by

$$f_a = \frac{1}{2\pi R_F C_F}$$

➤ Generally the value of  $f_a$  and in turn  $R_1 C_F$  and  $R_F C_F$  values should be selected such that  $f_a < f_b$ . In fact, the input signal will be integrated properly if the time period  $T$  of the signal is larger than or equal to  $R_F C_F$ , (i.e)

$$T \geq R_F C_F$$

Where

$$R_F C_F = \frac{1}{2\pi f_a}$$

### Uses:

- Most commonly used in analog computers.
- ADC
- Signal wave shaping circuits.


## 7. Explain in detail about difference amplifier(Subtractor). [CO2-L2]

### Definition:

The differential amplifiers amplify the difference between two voltages. This type of operational amplifier circuit is commonly known as a Differential Amplifier configuration and is shown below:
 
### Differential Amplifier

By connecting each input in turn to 0v ground we can use superposition to solve for the output voltage  $V_{out}$ . Then the transfer function for a Differential Amplifier circuit is given as:



$$V_{out} = R3 / R1 (V_2 - V_1)$$

If all the resistors are all of the same ohmic value, that is:  $R1 = R2 = R3 = R4$  then the circuit will become a Unity Gain Differential Amplifier and the voltage gain of the amplifier will be exactly one or unity. Then the output expression would simply be  $V_{out} = V_2 - V_1$ . Also note that if input  $V_1$  is higher than input  $V_2$  the output voltage sum will be negative, and if  $V_2$  is higher than  $V_1$ , the output voltage sum will be positive.

The Differential Amplifier circuit is a very useful op-amp circuit and by adding more resistors in parallel with the input resistors  $R1$  and  $R3$ , the resultant circuit can be made to either "Add" or "Subtract" the voltages applied to their respective inputs. One of the most

common ways of doing this is to connect a “Resistive Bridge” commonly called a *Wheatstone Bridge* to the input of the amplifier .

### Subtractor :

A basic differential amplifier can be used as a subtractor as shown in Fig. 4.3 (a). If all resistors are equal in value, then the output voltage can be derived by using superposition principle. To find the output  $V_{o1}$  due to  $V_1$  alone, make  $V_2 = 0$ . Then the circuit of Fig. 4.3 (a) becomes a non-inverting amplifier having input voltage  $V_1/2$  at the non-inverting input terminal and the output becomes

$$V_{o1} = V_1/2 (1+R/R) = V_1$$

Similarly the output  $V_{o2}$  due to  $V_2$  alone (with  $V_1$  grounded) can be written simply for an inverting amplifier as  $V_{o2} = -V_2$

Thus the output voltage  $V_o$  due to both the inputs can be written as

$$V_o = V_{o1} + V_{o2} = V_1 - V_2$$

 


Fig. Op-amp as subtractor

**8. With the help of circuits and necessary operations, how log and antilog computations are performed using IC741. [CO2- H2-May/June 2016]**

### LOG AND ANTILOG AMPLIFIER

There are several applications of log and antilog amplifiers. Antilog computation may require functions such as  $\ln x$ ,  $\log x$  or  $\sinh x$ . These can be performed continuously with log-amps. One would like to have direct dB display on digital voltmeter and spectrum

analyser. Log-amp can easily perform this function. Log-amp can also be used to compress the dynamic range of a signal.

## Log Amplifier

### Definition:

Output voltage is equal to the logarithm of input voltage.

 


Fig .Logarithmic amplifier

The fundamental log-amp circuit is shown in below Fig.(a) where a grounded base transistor is placed in the feedback path. Since the collector is held at virtual ground and the base is also grounded, the transistor's voltage-current relationship becomes that of a diode and is given by,

The current equation of diode is given as  $I_d = I_{do} * (\exp (V/V_t) - 1)$  where  $I_{do}$  is reverse saturation current,

$V$  is voltage applied across diode;  $V_t$  is the voltage equivalent of temperature. Hence applying KCL at inverting terminal of opamp, we get

$$(0 - V_{in}) / R_1 + I_d = 0 \text{ implies } I_d = V_{in} / R_1$$

Substituting the equation for current in the above equation we get  $I_{do} * (\exp (V/V_t) - 1) = V_{in} / R_1$ . Assuming  $\exp (V/V_t) \gg 1$  i.e.  $V \gg V_t$  and  $V = -V_o$ , we get  $I_{do} * \exp (-V_o / V_t) = V_{in} / R_1$ . Applying Antilog on both sides we get

$$V_o = -V_t * \ln (V_{in}/(R_1 * I_{do})).$$

### Gain of logarithmic amplifier

Gain of amplifier  $K = -V_t$

The output voltage is thus proportional to the logarithm of input voltage. Although the circuit gives natural log (ln), one can find  $\log_{10}X$  by proper scaling

$$\text{Log}_{10} X = 0.4343 \ln X$$

The circuit, however, has one problem. The emitter saturation current  $I_s$  varies from transistor to transistor and with temperature. Thus a stable reference voltage  $V_{ref}$  cannot be obtained. This is eliminated by the circuit given in fig..

The input is applied to one log-amp, while a reference voltage is applied to another log-amp. The two transistors are integrated close together in the same silicon wafer. This provides a close match of saturation currents.

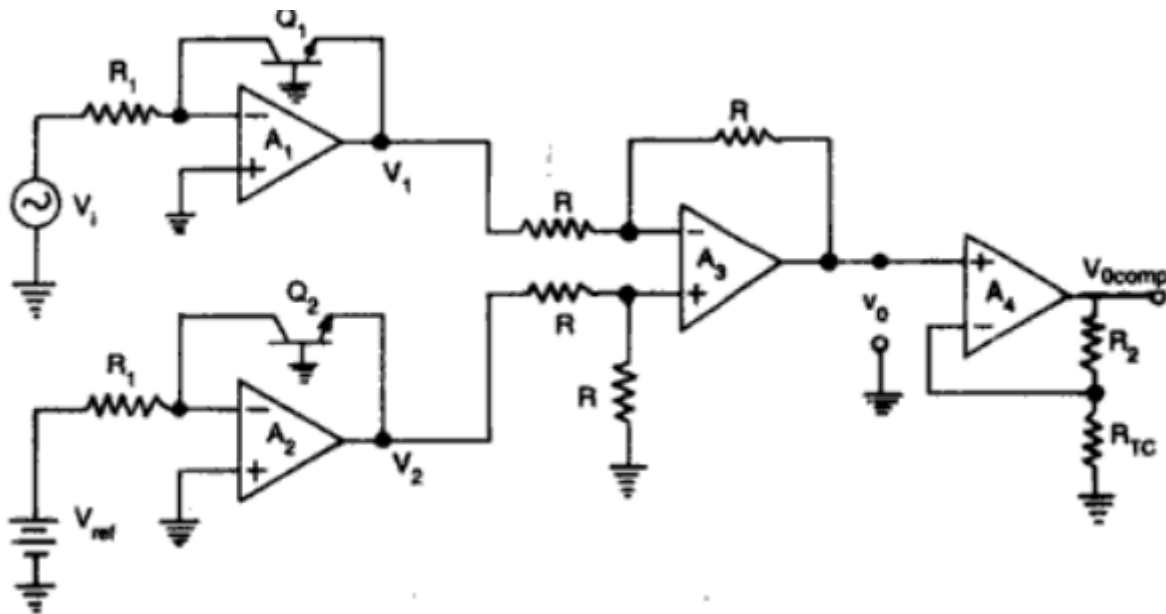


Fig. Log amp with saturation current and temperature compensation

The voltage  $V_o$  is still dependent upon temperature and is directly proportional to  $T$ . This is compensated by the last op-amp stage  $A$ , which provides a non-inverting gain of  $(1 + R_2/R_{TC})$ . Now, the output voltage is,

$$V_{O \text{ comp}} = (1 + R_2/R_{TC}) (kt/q) \ln(V_i/V_{ref})$$

where  $R_{TC}$  is a temperature-sensitive resistance with a positive coefficient of temperature (sensistor) so that the slope of the equation becomes constant as the temperature changes.

 


Fig. Log amp with two Op-amps only

### Antilog amplifier

#### Definition:

Output voltage is equal to the antilogarithm of input voltage.



The circuit is shown in Fig. The input  $V_i$ , for the antilog-amp is fed into the temperature compensating voltage divider  $R_2$  and  $R_{TC}$  and then to the base of  $Q_2$ . The output  $V_O$  of the antilog-amp is fed back to the inverting input of  $A_1$  through the resistor  $R_1$ . The base to emitter voltage of transistors  $Q_1$  and  $Q_2$  can be written as

$$V_{Q_1 \text{ B-E}} = kT/q \ln(V_O/R_1 I_S) \text{ and}$$

$$V_{Q_2 \text{ B-E}} = kT/q \ln(V_{ref}/R_1 I_S)$$

**Antilog amp diagram:**

 


Fig. Antilog amplifier

➤ Hence an increase of input by one volt causes the output to decrease by a decade. The 755 log/antilog amplifier IC chip is available as a functional module which may require some external components also to be connected to it.


**9. With a neat diagram explain the operation of Schmitt trigger. [CO2- H1-April/May 2016]**

**Regenerative comparator (Schmitt Trigger):**

➤ In a basic comparator a feedback is not used and the op-amp is used in open loop mode. As open loop gain of op-amp is large very small noise voltages also can cause triggering of comparator in applications of comparator as zero crossing detector. This may give a wrong indication of zero crossing due to zero crossing of noise voltage rather than zero crossing of input wanted signal.

➤ Such unwanted noise causes the output to jump between high and low states. The comparator circuit used to avoid such unwanted triggering is called as regenerative comparator or Schmitt trigger which uses a positive feedback.

 **1. Basic inverting Schmitt Trigger circuit:**



**Inverting schmitt trigger**

➤ Figure shows the basic Schmitt trigger circuit. As the input is applied to inverting terminal it is also called as inverting Schmitt Trigger circuit. The inverting mode produces opposite polarity output. This is feedback to the non-inverting input which is of same polarity as that of output. This ensures positive feedback.

➤ When  $V_{in}$  is slightly positive than  $V_{Ref}$ , the output gets driven into negative saturation at  $-V_{sat}$  level.

➤ When  $V_{in}$  becomes more negative than  $-V_{ref}$ , then output gets driven into positive saturation at  $+V_{sat}$  level.

- Thus output voltage is always at  $+V_{sat}$  or  $-V_{sat}$  but the voltage at which it changes its state now can be controlled by  $R_1$  and  $R_2$ . Thus  $V_{ref}$  can be obtained as per the requirement.
- Now  $R_1$  and  $R_2$  forms a potential divider and we write,
- The output voltage remains in a given state until the input voltage exceeds the threshold voltage level either positive or negative.
- The figure shows the graph of output voltage against input voltage. This is called as transfer characteristics of Schmitt trigger.


 


Fig. Transfer characteristics showing hysteresis

The graph indicates that once the output changes its state it remains there indefinitely until the input voltage crosses any of the threshold levels. This is called as hysteresis of Schmitt trigger. The hysteresis is also called as dead band or dead Zone.

 
If input applied is purely sinusoidal the input and output waveforms for inverting Schmitt trigger is shown below:



**Input and output waveforms of inverting schmitt trigger**

 **2.Non inverting Schmitt trigger:**


The figure shows the non inverting Schmitt trigger circuit. The input is applied to the noninverting input terminal of the op-amp.



 
**Noninverting schmitt trigger**

The output is positively saturated at  $+V_{sat}$ . This is the feedback to noninverting input through  $R_1$ . This is positive feedback.

At lower threshold the output changes its state from positive saturation  $+V_{sat}$  to negative saturation  $-V_{sat}$ . It remains in negative saturation till  $V_{in}$  increases beyond its upper threshold level. The transfer characteristics are shown below:



 **Transfer characteristics showing hysteresis**



Input and output waveforms

**Schmitt Trigger Applications:**

- Sine to square wave converter.
- It can be used to eliminate comparator chatter in signal shaping and in ON/OFF control.

It is a building block of relaxation oscillators.

**10. What is a precision rectifier? With circuit schematic explain the working principle of full wave rectifier. [CO2- L2-Nov/Dec 2015 & May/June 2016]**


The signal processing applications with very low voltage, current and power levels require rectifier circuits. The ordinary diodes cannot rectify voltages below the cut-in-voltage of the diode.

A circuit which can act as an ideal diode or precision signal – processing rectifier circuit for rectifying voltages which are below the level of cut-in voltage of the diode can be designed by placing the diode in the feedback loop of an op-amp.

**Half – wave Rectifier:****Operation:**


- (i) When  $V_i > 0V$ , the voltage at  $V_{OA}$  = negative  $D_1$  forward biased,  $D_2$  becomes reverse biased. Therefore  $V_o = 0$  when the input is positive.

 (ii) When  $V_i < 0$ , the voltage at  $V_{OA} = \text{positive}$   $D_2$  forward biased,  $D_1$  becomes reverse biased. Therefore  $V_o = V_{in}$  when the input is negative.




Non - Saturating half - wave precision rectifier circuit

 The **advantages** of half wave rectifier are it is a precision half wave rectifier and it is a non saturating one.




### Full wave Rectifier:

The Full wave Rectifier circuit commonly used an absolute value circuit is shown in figure.

 **Operation:**

(i) When  $V_i > 0V$ , op-amp  $A_1$  o/p is negative,  $D_1$  forward biased,  $D_2$  becomes reverse biased. Op-amp  $A_2$  input is negative, therefore (op-amp  $A_2$ )  $V_0 =$  positive.

(ii) When  $V_i < 0$ , op-amp  $A_1$  o/p is positive  $D_2$  forward biased,  $D_1$  becomes reverse biased. Therefore  $V_0 =$  positive.

 **11. Write short notes on : Clipper circuits. [CO2- L2-Nov/Dec 2016]****Clipper****Definition:**

The circuits which are used to clip off the certain portions of input voltage to get desired output are called as clipper or limiting circuits. As some part of input gets clipped off to produce output these circuits are commonly called clipping circuits.

**These circuits are classified as,**

1. Positive clipper circuit.
2. Negative clipper circuit.

The positive clipper circuits remove some positive part from the input to produce the output. The negative clipper circuits remove some negative part from the input to produce the output.

**Positive clipper circuit:**

 


Fig. Positive clipper circuit

A positive clipper circuit using op-amp is shown in figure:

The clipping level is determined by reference voltage  $V_{ref}$ . This reference voltage is obtained from positive supply voltage  $+V_{CC}$  or negative voltage  $-V_{EE}$ . In the circuit  $V_{ref}$  is determined by pot  $R_p$  e.g. 2V. In positive half cycle of input diode D conducts till  $V_{in} = V_{ref}$ . When  $V_{in}$  is less than  $V_{ref}$  the D becomes forward biased and op-amp acts as voltage follower. Hence output voltage  $V_o$  is same as  $V_{in}$ .


But for  $V_{in}$  greater than  $V_{ref}$  the diode D becomes reverse biased and becomes open. This opens the feedback loop and op-amp operates in open loop. This open loop operation drives op-amp output towards positive saturation  $+V_{CC}$ . Due to this output voltage  $V_o$  remains at  $V_{ref}$  and entire waveform above  $V_{ref}$  gets clipped off.

Thus the diode is on when  $V_{in} > V_{ref}$  and off for  $V_{in} < V_{ref}$ . The output follows input when diode is on and remains at  $V_{ref}$  when it is off. Thus op-amp alternates between closed loop and open loop operation and hence op-amp used must be high speed and compensated for unity gain.



The high speed op-amp like HA 2500, LM 310 can be used for such applications.

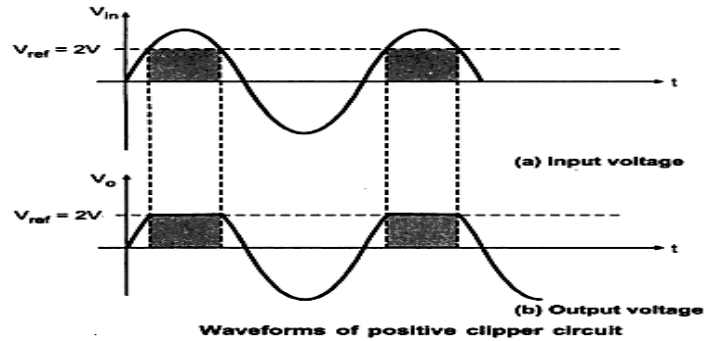The output and input waveforms are shown below:



In the same circuit if the pot  $R_p$  is used with  $-V_{EE}$  to generate negative  $V_{ref}$  instead of  $V_{CC}$  then the entire waveforms above  $-V_{ref}$  gets clipped off. Let  $V_{ref} = -2V$  in the same circuit, the output follows input only when  $V_{in} < -V_{ref}$  i.e.  $V_{in} < -2V$ . The waveforms with  $V_{ref} = -2V$  is shown below:


 


Fig: Waveforms with negative  $V_{ref}$

 
### Negative clipper circuit:

The negative clipper circuit can be obtained by reversing the connection of diode  $D$  and using pot  $R_p$  to generate negative voltage  $V_{ref}$ . This circuit is shown below:




 **Negative clipper circuit**

When  $V_{in} > -V_{ref}$  then diode D conducts and the output voltage follows the input voltage. But when  $V_{in} < -V_{ref}$  D is off and voltage below  $-V_{ref}$  gets clipped off. The circuit hence is called as negative clipper circuit. The waveforms are shown below:



**Waveforms of negative clipper circuit**

 

**Figure: Waveforms with positive  $V_{ref}$**

If for the same circuit reference voltage is generated using  $+V_{cc}$  i.e.  $+V_{ref}$  the diode D is on for  $V_{in} > V_{ref}$  and is off for  $V_{in} < V_{ref}$ . The corresponding waveforms are shown in figure.

**12.Explain in detail about clamper circuit with neat waveforms? [CO2-L2-Nov/Dec 2016]**

**Definition:**


The circuits which are used to add d.c. level as per the requirement to the a.c. output are called as clamper circuits. Sometimes it is necessary to add a d.c. level to the a.c. output signal. The circuits which are used to add d.c. level as per the requirement to the a.c. output are called as clamper circuits. These circuits are also called as d.c. restorer circuits. If the clamped d.c. level is positive the circuits are called as positive clamper circuits and if clamped level is negative the circuits are called as negative clamper circuits.

**Types:**

- (i) Positive clamper circuits
- (ii) Negative clamper circuits

 **Positive clamper circuits:**

The fig shows the positive clamper circuit using op-amp: When the input voltage is first time negative due to inverting mode of op-amp the op-amp is positive. This turns on the diode making it forward biased. Thus the capacitor charges to peak value of negative cycle of input with the polarities are shown in figure.



**Positive clamper circuit**

➤ The diode becomes reverse biased and stops conducting. It becomes open. Hence the output voltage is sum of the input voltage and the capacitor voltage mathematically it is given by,

$$V_{out} = V_{in} + V_p$$


➤ Thus d.c. level equal to  $V_p$  gets added in a.c. output signal. The final output waveform is sinusoidal but shifted positively through  $V_p$ .

➤ Hence the circuit is called as positive clamper and the waveform is called as positively clamped waveform. As during positive half cycle of input, Diode does not conduct the capacitor retains its voltage at  $V_p$  all time after the first negative peak of input.


➤ The waveforms are shown below: It can be observed that waveform swings from 0 to  $+2V_p$  i.e. peak to peak voltage of output waveform is  $2V_p$  which remains same as the input voltage. Thus the circuit shows that the total swing of output voltage remains same as the total swing of input voltage in clamper circuit.

➤ In the circuit given below the d.c. level added is equal to peak value of input used.

 Another circuit in which variable positive d.c. level can be added is shown below:



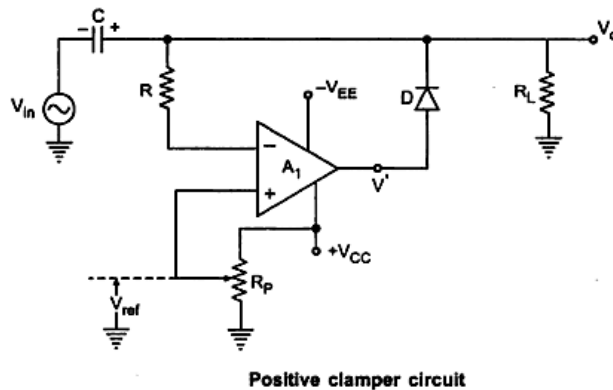The input voltage is applied to the inverting terminal of op-amp  $A_1$  while variable positive d.c. Voltage is applied to the noninverting input terminal of op-amp  $A_1$ . The circuit can be analysed using the superposition theorem considering only one input active at a time.



Let  $V_{ref}$  is acting along  $V_{in}$  is Zero. For positive  $V_{ref}$  the output voltage  $v$  is also positive. Due to this Diode  $D$  is forward biased. Hence the circuit acts as a voltage follower. Hence the net voltage  $V_o$  is same as positive  $V_{ref}$ .


Now let input at inverting terminal be purely sinusoidal i.e.  $V_{in} = V_m \sin \omega t$ . For negative half cycle of input  $V_o'$  will be positive and  $D$  will conduct. The capacitor  $C$  charges through Diode  $D$  to negative peak voltage  $V_m$ . During the positive half cycle of input  $D$  does not conduct and capacitor  $C$  retains its previous voltage of  $V_m$ .

This voltage  $V_m$  is in series with a.c. input voltage the output becomes  $V_{in}+V_m$ .

Hence the net output voltage due to the effect of both the inputs becomes

$$V_{in}+V_m+V_{ref}.$$

 The resistance R is used to protect op-amp against excessive discharge currents from Capacitor C when d.c. supply voltages are switched off. The waveforms are shown below:



As the circuit clamps the peak of input waveforms hence the circuit is also called as peak clamper circuit.


**Negative clamper circuit:** The figure shows the negative clamper circuit obtained by reversing the diode connections in positive clamper circuit.

When  $V_{in}$  is first positive going due to inverting mode of op-amp the voltage  $V_{OA}$  goes negative. Thus diode D becomes forward biased and capacitor charges to peak value with polarities as shown:


Hence beyond the positive peak the diode becomes reverse biased and becomes open.

Hence the output voltage  $V_o$  is sum of input and capacitor voltages.


$$V_o = V_{in} - V_p$$

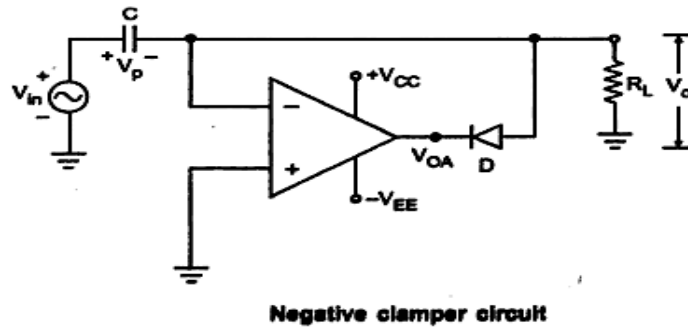

 
Hence a negative d.c. level of  $-V_p$  gets added to output hence the circuit is called as negative clamper circuit. The waveforms are shown below:



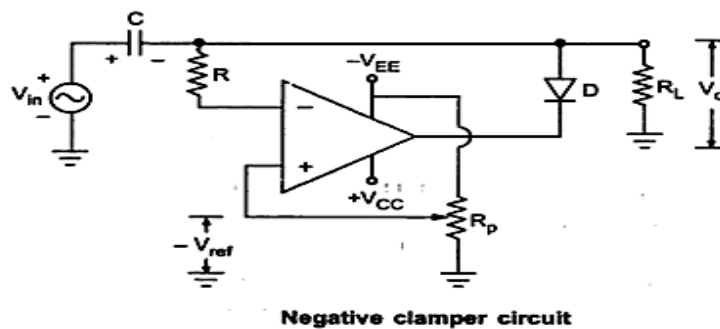Another circuit in which variable negative d.c. level can be added is shown below. In such circuit  $-V_{ref}$  is generated using the negative supply  $-V_{EE}$  of the op-amp and diode connections are reversed.



 
Hence negative clamper is obtained. The waveforms are shown below:






Due to opposite connection of diode D, the capacitor charges in reverse direction and hence negative clamper is obtained. The waveforms are shown above.

**13. Differentiate between low pass, high pass, band pass and band reject filter.**

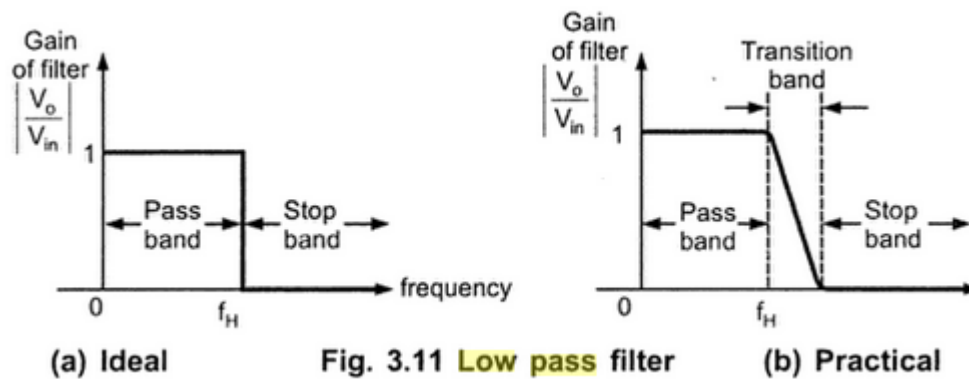**Sketch the frequency plot. [CO2-L2-Nov/Dec 2016]**





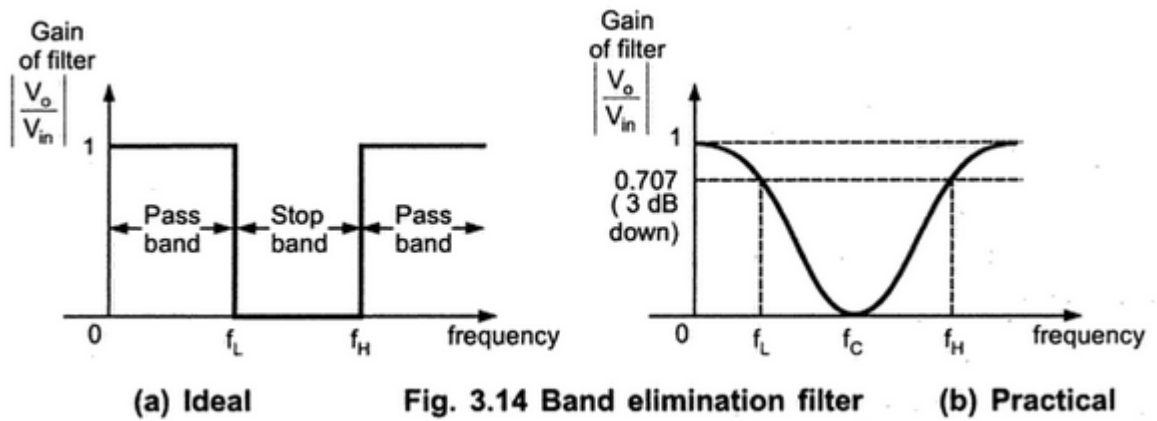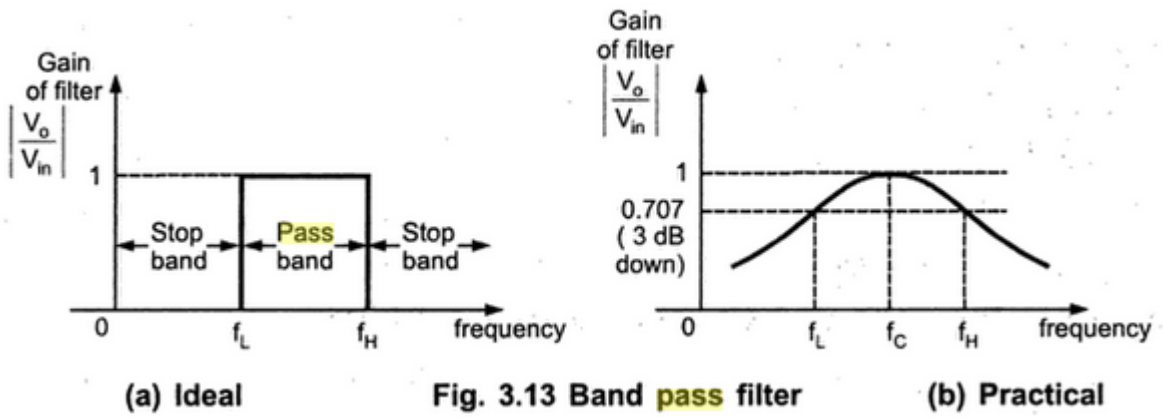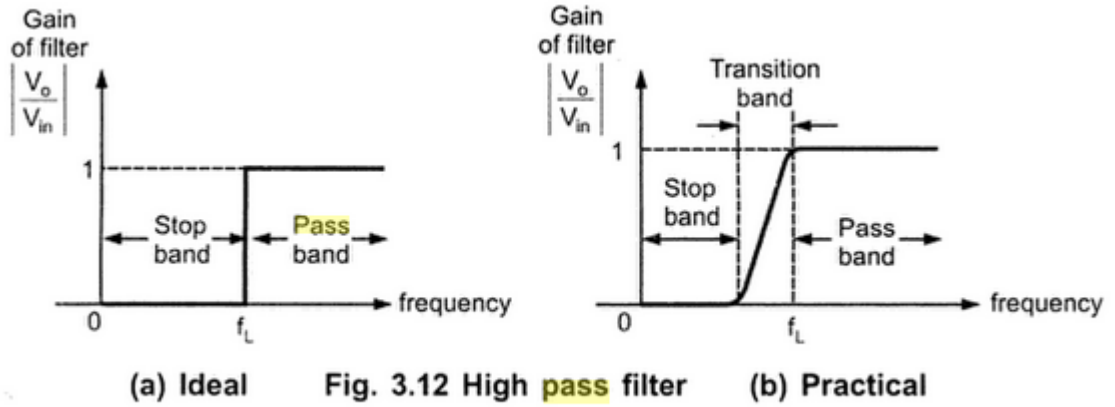

**14. Mention two advantages of active filter over passive filter. Also design a second order low pass filter using operational amplifier for the upper cut off frequency of 2 kHz. Assume the value of capacitor to be 0.1  $\mu$ F. [CO2-H3-Nov/Dec 2015]**

#### **Advantages of active filters**

The active filters have the following advantages over the passive filters :

1. All the elements alongwith op-amp can be used in the integrated form. Hence there is reduction in size and weight.
2. In large quantities, the cost of the integrated circuit can be much lower than its equivalent passive network.
3. Due to availability of modern ICs, variety of cheaper op-amps are available.
4. The op-amp gain can be easily controlled in the closed loop fashion hence active filter input signals are not attenuated.
5. Due to flexibility in gain and frequency adjustments, the active filters can be easily tuned.
6. The op-amp has high input impedance and low output impedance hence the active filters using op-amp do not cause loading of the source or load.
7. The inductors are absent in the active filters hence the modern active filters are more economical.
8. Active filters can be realized under number of class of functions such as Butterworth, Thomson, Chebyshev, etc.
9. The response is improved as compared to passive filters due to ready availability of high quality components.
10. The design procedure is simpler than that for the passive filters.

**15. Design a first order Low-pass filter for cut-off frequency of 2 KHz and pass-band gain of 2. [CO2-H3]**

**Solution :**

Given  $f_H = 2\text{kHz}$  and  $A = 2$

Let  $C = 0.01\mu\text{F}$

We know that  $f = 1 / 2\pi RC$

Therefore,  $R = 1 / 2\pi fc$

$= 7.95\text{K}\Omega$

Gain  $A = 1 + (R_f / R_i) = 2$


Therefore,  $R_f = R_i = 10\text{K}\Omega$ .

**16. Explain the application of operational amplifier as differentiator. [CO2-H3-  
Nov/Dec 2015]**

 **Differentiator**

An op-amp differentiator or a differentiating amplifier is a circuit configuration which produces output voltage amplitude that is proportional to the rate of change of the applied input voltage.

A differentiator with only RC network is called a passive differentiator, whereas a differentiator with active circuit components like transistors and operational amplifiers is called an active differentiator. Active differentiators have higher output voltage and much lower output resistance than simple RC differentiators.



### Fig. Op-amp differentiator

An op-amp differentiator is an inverting amplifier, which uses a capacitor in series with the input voltage. Differentiating circuits are usually designed to respond for triangular and rectangular input waveforms. For a sine wave input, the output of a differentiator is also a sine wave, which is out of phase by  $180^\circ$  with respect to the input (cosine wave).

Differentiators have frequency limitations while operating on sine wave inputs; the circuit attenuates all low frequency signal components and allows only high frequency components at the output. In other words, the circuit behaves like a high-pass filter.

### Unit -III

#### Analog Multiplier and PLL

##### Part A

**1. How do you convert a basic multiplier to a squaring and square root circuit? [CO3-L1]**

For Voltage Squarer: The input voltage  $V_i$  to be squared is simply connected to both the input terminals and hence we have,  $V_x = V_y = V_i$  and the output is  $V_o = KV_i^2$ .

For Square rooter: the divider circuit can be used to find the square root of a signal by connecting both the inputs of the multiplier to the output of the op-amp.

**2. What are the applications of PLL for AM detection? [CO3-L1]**

The PLL can be used as an AM detector for demodulating the amplitude modulated signals.

**3. Define : (a) Capture range and (b) Lock range of Phase Locked Loop (PLL) [CO3-L1]**

Capture range : The range of frequencies over which the PLL can acquire lock with an input signal is called the capture range. This parameter is expressed as percentage of  $f_o$ .

Lock-in Range : The range of frequencies over which the PLL can maintain lock with the incoming signal is called the lock-in range or tracking range. The lock-in range is expressed as a percentage of  $f_o$ , the VCO frequency.


**4. Mention two applications of analog multiplier. [CO3-L1]**

Voltage squarer , Frequency doubler

**5. What is four quadrant multiplier? [CO3-L1]**

The four-quadrant operation indicates that the output voltage is directly proportional to the product of the two input voltages regardless of the polarity of the inputs and such multipliers can be operated in all the four quadrants of operation.

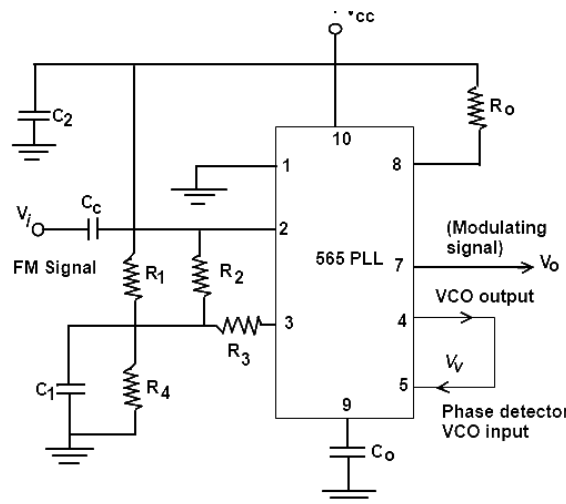**6. Draw the circuit diagram of a PLL circuit using as a FM detector. [CO3-L1]**




**7. Enlist any four applications of NE 565 PLL. [CO3-L3]**

- (i) AM detection
- (ii) FM detection
- (iii) FSK modulation /demodulation

(iv) Frequency multiplication

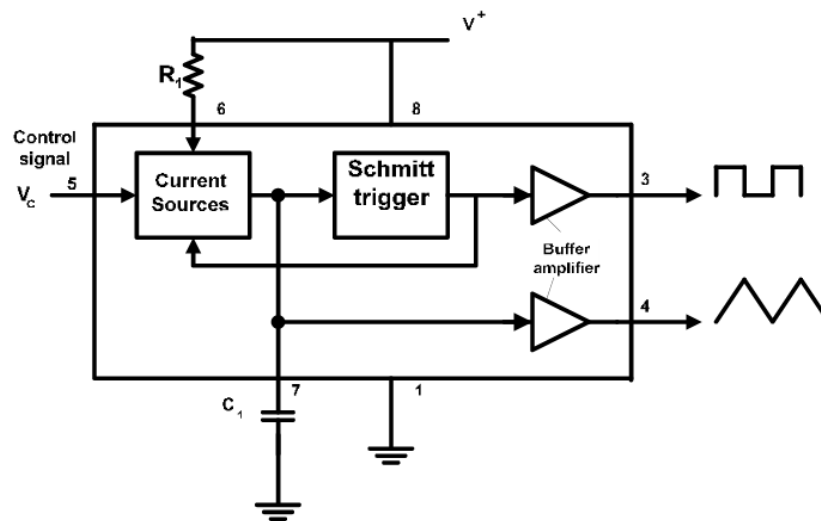8. Draw the block diagram of IC 566 VCO (Voltage Controlled Oscillator) [CO3-L1]



9. What is meant by frequency synthesizing? [CO3-L1]

A frequency synthesizer allows the designer to generate a variety of output frequencies as multiples of a single reference frequency. The frequency synthesizer produces a large number of precise frequencies, which are derived from a single reference source of frequency, a stable crystal controlled oscillator.

10. Define lock range of a PLL. [CO3-L1]

The range of frequencies over which the PLL can maintain lock with the incoming signal is called the lock-in range or tracking range. It is expressed as a percentage of  $f_o$ , the VCO frequency.

**11. A PLL frequency multiplier has an input frequency of “f” and a decade counter is included in the loop. What will be the frequency of the PLL output? [CO3-L3]**

$$f_o = 1 / 10\text{secs}$$

**12. Mention any two applications of PLL. [CO3-L1]**

Frequency translation, AM detection, FM Demodulation, FSK Demodulator.

**13. What is a two quadrant multiplier? [CO3-L1]**

A two quadrant multiplier functions properly if one input is held positive and the other is allowed to swing in both positive and negative.

**14 What are the advantages of variable transconductance technique? [CO3-L2]**

- i. Provides very good accuracy
- ii. Provides four quadrant operation
- iii. Reduced error atleast by 10 times

**15. VCO is also called V-f converter. Why? [CO3-L1]**

The VCO converts the applied input voltage to an output frequency. Hence, it is called voltage to frequency converter.

**16. What are the advantages of emitter coupled transistor pair? [CO3-L3]**

- i. Low drift because of its symmetrical IC construction.
- ii. Very high input resistance
- iii. High CMRR



**17. With a reference to a VCO, define voltage to frequency conversion factor  $K_v$ .**

**[CO3-L1]**


Voltage to frequency conversion factor  $K_v$  is defined as

$$K_v = \Delta f_0 / \Delta V_c$$

**18. What is VCO? [CO3-L1]**

The VCO is a free running multivibrator and operates at a set frequency called free running frequency. This frequency can be shifted to the either side by applying a dc control voltage. The frequency deviation is directly proportional to the dc control voltage and hence it is called Voltage Controlled Oscillator.

 **19. Draw the relation between the capture ranges and lock range in a PLL. [CO3-L1]**



**20. List the basic building blocks of a PLL? [CO3-L1]**

A phase locked loop consists to a phase detector, low pass filter, amplifier and a VCO in feedback loop.

**21. What are the important characteristics of a PLL? [CO3-L1]**

The important characteristics of a PLL are: lock-in range, capture range and pull-in-time.

**22. What is the need of LPF in a PLL? [CO3-L1]**

The LPF not only removes the high frequency components and noise, but also controls the dynamic characteristics of the PLL. The LPF controls the capture range and lock range of a PLL.

**23. Which is greater 'Capture range' or 'Lock-in range'? [CO3-L1]**

The lock-in range is usually greater than the capture range. The capture range depends upon the LPF characteristics.

**24. What is the range of modulation input voltage applied to a VCO? [CO3-L1]**

The modulating input voltage is usually varied from  $0.75 V_{cc}$  to  $V_{cc}$  which can produce a frequency variation of about 10 to 1.


**25. Mention few monolithic PLL ICs? [CO3-L1]**

Signetics SE/NE 560 series – 560, 561, 562, 564, 565 and 567 are monolithic PLLs.

**26. Mention few applications of analog multiplier? [CO3-L1]**

Frequency doubling, Phase angle detection, Squaring, Multiplication, Division

 **27. Sketch the schematic symbol of multiplier. [CO3-L1]**



**28. What is transconductance multiplier? [CO3-L1]**

Log-amps require the input and reference voltages to be of the same polarity. This restricts log-antilog amplifiers to one quadrant operation. A technique that provides four quadrant multiplication is trans-conductance multiplier.

**29. What are the types of phase detector? [CO3-L1]**

Analog phase detector and Digital Phase detector

**30. What are the performance parameters of a multiplier? [CO3-L1]**

Accuracy, Linearity, Bandwidth, Feed through voltage, Scale factor

**31. Define scale factor of multiplier? [CO3-L1]**

Scale factor is the constant (k) relating the output voltage and the product of two input voltages.

$$K = V_o / V_1 V_2$$


**32. Define Pull-in time. [CO3-L1]**

The total time taken by the PLL to establish lock is called pull-in time. It depends on the initial phase and frequency difference between the two signal levels as well as on the overall loop gain and loop filter characteristics.

**33. What are the three stages through which PLL operates? [CO3-L3]**


- i. Free running
- ii. Capture
- iii. Locked/tracking

 34. Draw the sketches for (i) One quadrant multiplier (ii) Two quadrant multiplier and (iii) Four quadrant multiplier. [CO3-L3]



Analog multiplier (a) Symbol; (b) to (d) multiplier quadrants of operation

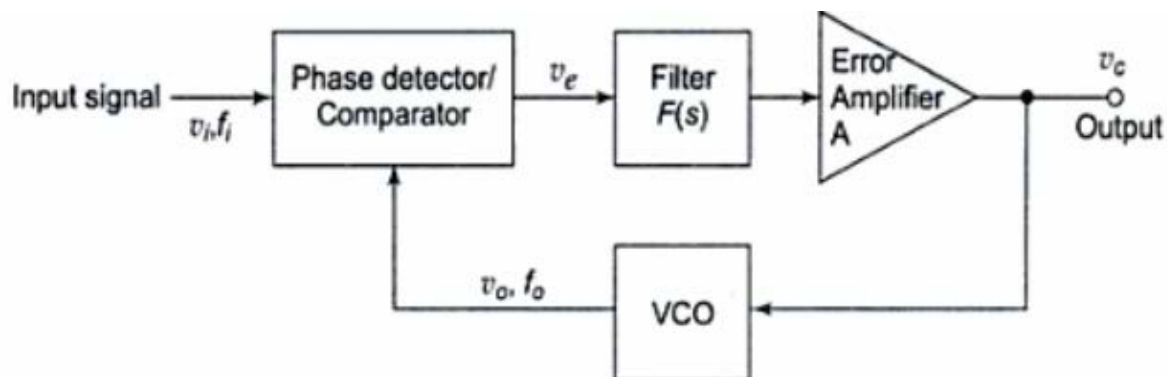35. Draw the basic block diagram of a PLL. [CO3-L1]



### Part B


1. State the limitations of emitter coupled transistor pair. [CO3-L1]

The first limitation is that  $V_2$  is offset by  $V_{BE(on)}$ . The second is that  $V_2$  must always be positive which results in only a two-quadrant multiplier operation. The third limitation is that, the  $\tanh(x)$  is approximated as  $x$ . The first two limitations are overcome in the Gilbert cell.

2. Discuss the principle of operation of NE 565 PLL circuit. [CO3-H1-May/June 2016]

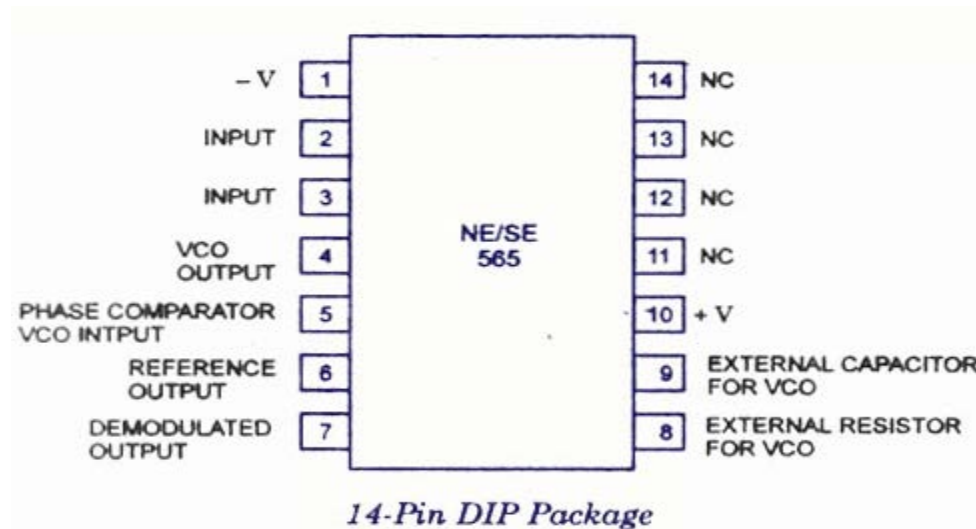
### Pin Configuration of PLL IC 565:

The pin details of PLL IC 565 is shown in the figure.


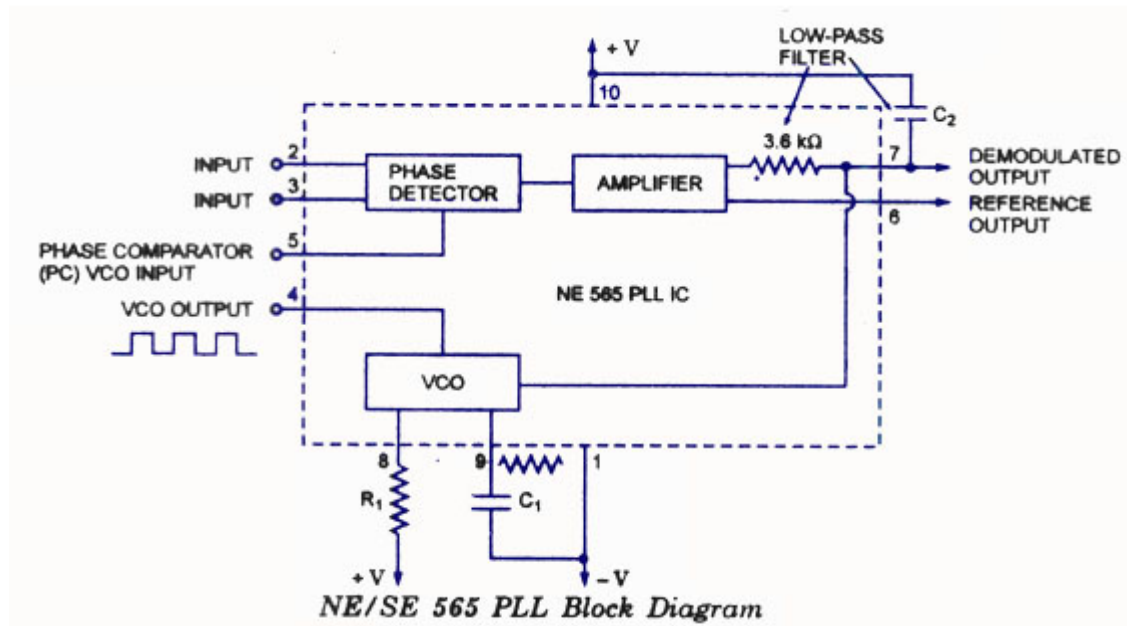
### Basic Block Diagram Representation of IC 565:

The signetics NE/SE 560 series is monolithic phase locked loops. The SE/NE 560, 561, 562, 564, 565 & 567 differ mainly in operating frequency range, power supply requirements & frequency & bandwidth adjustment ranges.



- The important electrical characteristics of the 565 PLL are,
  - Operating frequency range: 0.001Hz to 500 KHz.
  - Operating voltage range:  $\pm 6$  to  $\pm 12$ v
  - Input level required for tracking: 10mv rms min to 3 Vpp max
  - Input impedance: 10 K ohms typically.
  - Output sink current: 1mA
  - Output source current: 10 mA

The center frequency of the PLL is determined by the free running frequency of the VCO,

which is given by 
$$f_{OUT} = \frac{1.2}{4R_1C_1} \text{ Hz} \text{-----(1)}$$

where  $R_1$  &  $C_1$  are an external resistor & a capacitor connected to pins 8 & 9.

- The VCO free-running frequency  $f_{OUT}$  is adjusted externally with  $R_1$  &  $C_1$  to be at the center of the input frequency range.
- $C_1$  can be any value,  $R_1$  must have a value between 2 k ohms and 20 K ohms.

- Capacitor  $C_2$  connected between 7 & +V.
- The filter capacitor  $C_2$  should be large enough to eliminate variations in the demodulated output voltage in order to stabilize the VCO frequency.
- The lock range  $f_L$  & capture range  $f_c$  of PLL is given by,


$$\text{The lock range } f_L = \pm \frac{8 f_{out}}{V} \text{ Hz} \text{ -----(2)}$$

Where  $f_{OUT}$  = free running frequency of VCO (Hz)

$$V = (+V) - (-V) \text{ volts}$$

Capture range  $f_c$  of PLL is


$$\left[ \frac{f_L}{2\pi(3.6)(10^3)(C_2)} \right]$$

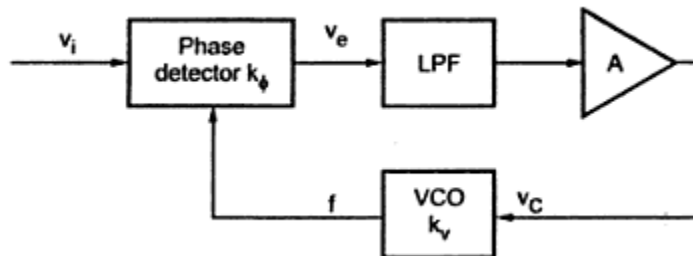

**Fig. PLL block diagram to determine capture range**
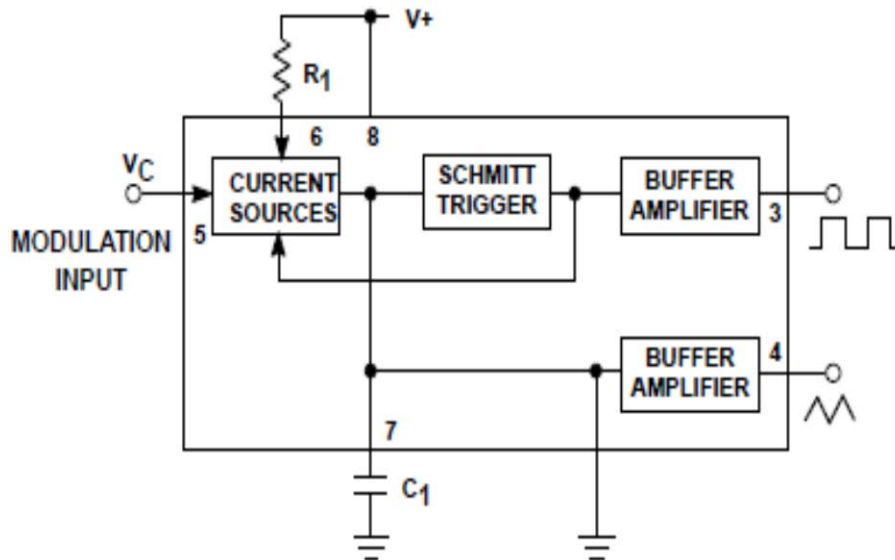
### 3.. Explain the application of VCO for FM generation. [CO3-L2]

A common type of VCO available in IC form is Signetics NE/SE566. The pin configuration and basic block diagram of 566 VCO are shown in figures below.



Referring to the circuit in the above figure, the capacitor  $c_1$  is linearly charged or discharged by a constant current source/sink. The amount of current can be controlled by changing the voltage  $v_c$  applied at the modulating input (pin 5) or by changing the timing resistor  $R_1$  external to the IC chip.

The voltage at pin 6 is held at the same voltage as pin 5. Thus, if the modulating voltage at pin 5 is increased, the voltage at pin 6 also increases, resulting in less voltage across  $R_1$  and thereby decreasing the charging current.

The voltage across the capacitor  $C_1$  is applied to the inverting input terminal of Schmitt trigger via buffer amplifier. The output voltage swing of the Schmitt trigger is designed to  $V_{cc}$  and  $0.5 V_{cc}$ .

If  $R_a = R_b$  in the positive feedback loop, the voltage at the non-inverting input terminal of Schmitt trigger swings from  $0.5 V_{cc}$  to  $0.25 V_{cc}$ . When the voltage on the capacitor  $c_1$  exceeds  $0.5 V_{cc}$  during charging, the output of the Schmitt trigger goes LOW ( $0.5 V_{cc}$ ). The capacitor now discharges and when it is at  $0.25 V_{cc}$ , the output of Schmitt trigger goes HIGH ( $V_{cc}$ ).



Since the source and sink currents are equal, capacitor charges and discharges for the same amount of time. This gives a triangular voltage waveform across  $C_1$  which is also available at pin 4. The square wave output of the Schmitt trigger is inverted by buffer amplifier at pin 3. The output waveforms are shown near the pins 4 and 3.

**Calculation of the output frequency of the VCO:** The total voltage on the capacitor changes from  $0.25V_{cc}$  to  $0.5V_{cc}$ . Thus  $\Delta V = 0.25 V_{cc}$ . The capacitor charges with a constant current source.

$$\frac{\Delta v}{\Delta t} = \frac{i}{C_T}$$

$$\frac{0.25V_{cc}}{\Delta t} = \frac{i}{C_T}$$


$$\Delta t = \frac{0.25V_{cc} C_T}{i} \dots\dots\dots(1)$$

The time period  $T$  of the triangular waveform  $= 2 \Delta t$ . The frequency of oscillation  $f_o$  is

$$f_o = \frac{1}{T} = \frac{1}{2\Delta t} = \frac{i}{0.5V_{cc}C_T}$$

$$i = \frac{V_{cc} - v_c}{R_T}$$

Therefore,  $f_o = \frac{2(V_{cc} - v_c)}{R_T C_T V_{cc}} \dots\dots\dots(2)$

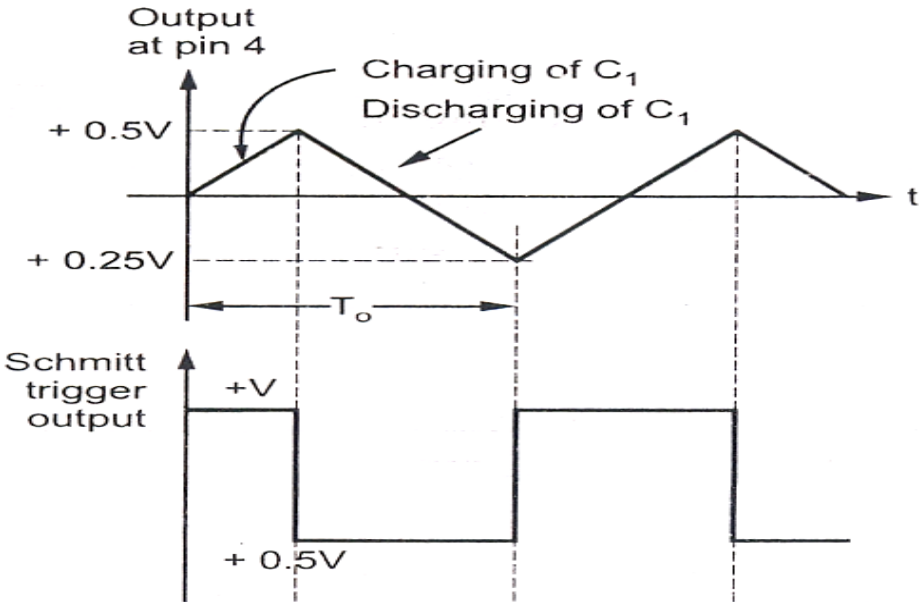


 


Fig. Waveforms for VCO

The output frequency of the VCO can be changed either by (i)  $R_T$ , (ii)  $C_T$  or (iii) the voltage  $v_c$  at the modulating input terminal pin 5. The voltage  $v_c$  can be varied by connecting a  $R_1R_2$  circuit as shown in the figure below.

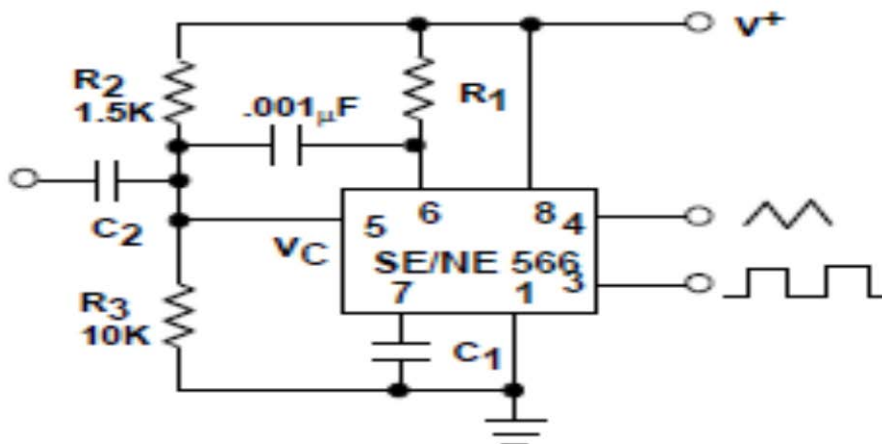The components  $R_1$  and  $c_1$  are first selected so that VCO output frequency lies in the centre of the operating frequency range. Now the modulating input voltage is usually varied from  $0.75 V_{cc}$  to  $V_{cc}$  which can produce a frequency variation of about 10 to 1.



4. Draw the block diagram of VCO and explain operation. Also derive the frequency of oscillator.

Voltage Controlled Oscillator

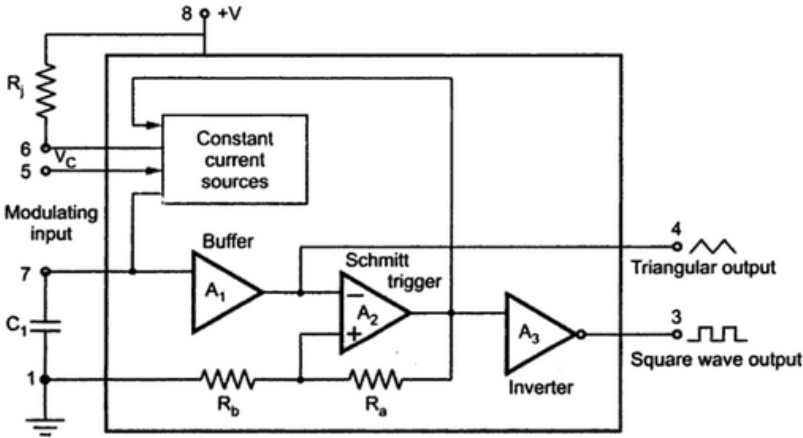


Fig. Block diagram of VCO

5. Brief the application of PLL IC for frequency multiplication. [CO3-L3- Nov/Dec 2016]

PLL as Frequency Multiplier.

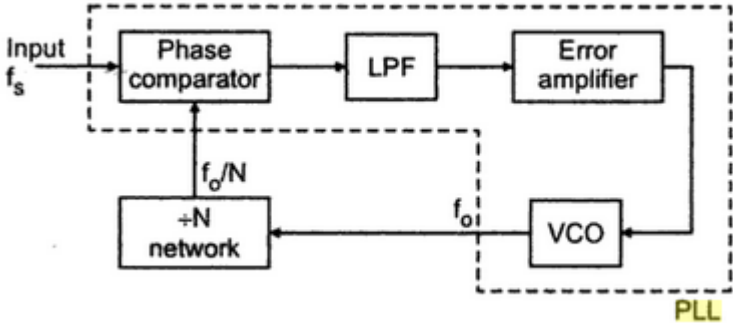


Fig. PLL as frequency multiplier

For the working of Frequency multiplier circuit the frequency divider is inserted between the VCO and phase comparator. Since the output of the divider is locked into the input

frequency  $f_{IN}$ , the VCO is actually running at a multiple of the input frequency. The desired amount of multiplication can be obtained by selecting a proper divide-by-N network, where N is an integer. For example, to obtain the output frequency  $f_{OUT} = 5f_{IN}$ , a divide-by-N = 5 network is needed.

**6. Explain the application of Phase Locked Loop as CO3-L3-Nov/Dec 2015]**

**(i) Frequency synthesizer**

**(ii) AM demodulator and**

**(iii) FM demodulator**

**(iv) Frequency Shift Keying (FSK) Demodulator**

➤ The output from a PLL system can be obtained either as the voltage signal  $v_c(t)$  corresponding to the error voltage in the feedback loop, or as a frequency signal at VCO output terminal. The voltage output is used in frequency discriminator applications whereas the frequency output is used in signal conditioning, frequency synthesis or clock recovery applications.

Consider the case of voltage output. When PLL is locked to an input frequency, the error voltage  $v_c(t)$  is proportional to  $(f_s - f_o)$ . If the input frequency is varied as in the case of FM signal,  $v_c$  will also vary in order to maintain the lock. Thus the voltage output serves as a frequency discriminator which converts the input frequency changes to voltage changes.

In the case of frequency output, if the input signal is comprised of many frequency components corrupted with noise and other disturbances, the PLL can be made to lock, selectively on one particular frequency component at the input. The output of VCO would then regenerate that particular frequency (because of LPF which gives output for beat frequency) and attenuate heavily other frequencies. VCO output thus can be used for regenerating or reconditioning a desired frequency signal (which is weak and buried in noise) out of many undesirable frequency signals.


➤ Some of the typical applications of PLL are discussed below.

**(i) Frequency Multiplier:**

➤ Fig. 4.63 shows the block diagram for a frequency multiplier using PLL 565. Here, a divide by N network is inserted between the VCO output (pin 4) and the phase comparator input (pin 5).

➤ Since the output of the divider is locked to the input frequency  $f_i$ , the VCO is actually running at a multiple of the input frequency. Therefore, in the locked state, the VCO output frequency  $f_o$  is given by,

$$f_o = Nf_i \quad (1)$$

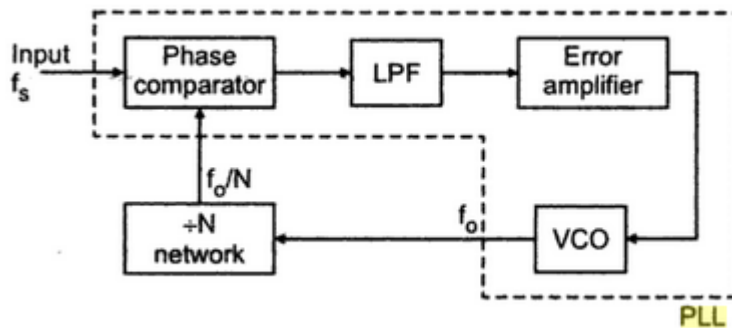


➤ By selecting proper divider by N network, we can obtain desired multiplication. For example, to obtain output frequency  $f_o = 6f_i$ , a divide by N should be equal to 6.

**(ii) Frequency Synthesizer:**

➤ The PLL can be used as the basis for frequency synthesizer that can produce a precise series of frequencies that are derived from a stable crystal controlled oscillator. Fig. 4.65 shows the block diagram of frequency synthesizer.

➤ It is similar to frequency multiplier circuit except that divided by M network is added at the input of phase lock loop. The frequency of the crystal-controlled oscillator is divided by an integer factor M by divider network to produce a frequency  $f_{osc}/M$ , where  $f_{osc}$  is the frequency of the crystal controlled oscillator.

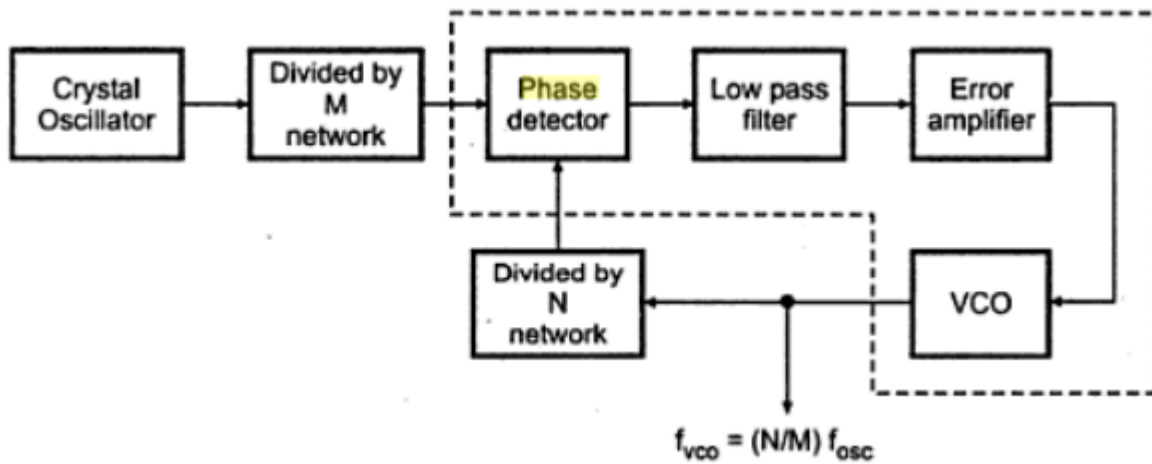
The VCO frequency  $f_{VCO}$  is similarly divided by factor  $N$  by divider network to give frequency equal to  $f_{VCO}/N$ . When the PLL is locked in on the divided-down oscillator frequency, we will have  $f_{osc}/M = f_{VCO}/N$  so that  $f_{VCO} = (N/M) f_{osc}$



**PLL as Frequency synthesizer**

By adjusting divider counts to desired values large number of frequencies can be produced, all derived from the crystal controlled oscillator.

**(iii) FM Demodulator:**

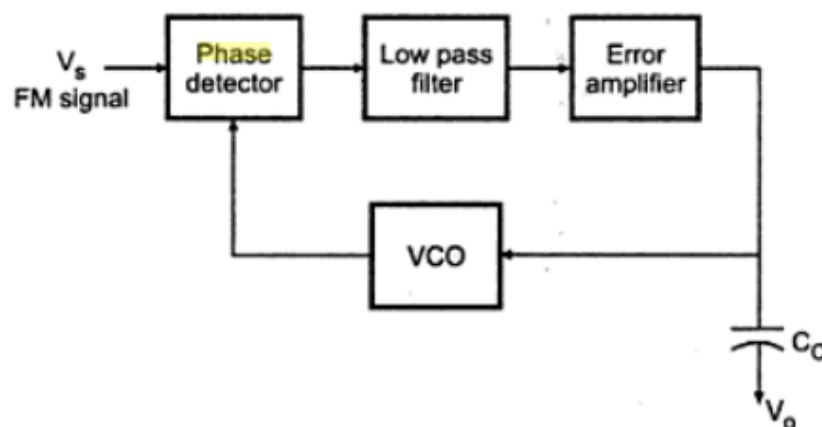

**Fig. PLL as FM Demodulator**

The PLL can be very easily used as an FM detector or demodulator. Fig. 4.66 shows the block diagram of FM detector. When the PLL is locked in on the FM signal, the VCO frequency follows the instantaneous frequency of the FM signal, and the error voltage or VCO control voltage is proportional to the deviation of the input frequency from the centre frequency.

Therefore, the a-c component of error voltage or control voltage of VCO will represent a true replica of the modulating voltage that is applied to the FM carrier at the transmitter. The faithful reproduction of modulating voltage depends on the linearity between the instantaneous frequency deviation and the control voltage of VCO. It is also important to note that the FM frequency deviation and the modulating frequency should remain in the locking range of PLL to get the faithful replica of the modulating signal.

If the product of the modulation frequency  $f_m$  and the frequency deviation exceeds the  $(\Delta f_c)^2$ , the VCO will not be able to follow the instantaneous frequency variations of the FM signal.


#### **(iv) Frequency Shift Keying (FSK) Demodulator:**

In digital data communication, binary data is transmitted by means of a carrier frequency. It uses two different carrier frequencies for logic 1 and logic 0 states of binary data signal. This type of data transmission is called frequency shift keying (FSK).

In this data transmission, on the receiving end, two carrier frequencies are converted into 1 and 0 to get the original binary data. This process is called as FSK demodulation. A PLL can be used as a FSK demodulator, as shown in the Fig. 4.67.

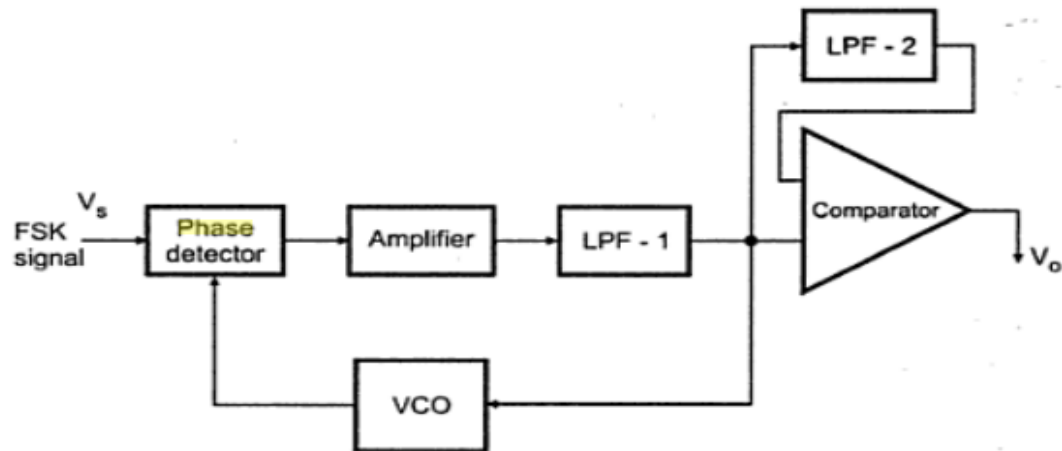It is similar to the PLL demodulator for analog FM signals except for the addition of a comparator to produce a reconstructed digital output signal.





Let us consider that there are two frequencies, one frequency ( $f_1$ ) is represented as "0" and other frequency ( $f_2$ ) is represented as "1". If the PLL remain is locked into the FSK signal at both  $f_1$  and  $f_2$ , the VCO control voltage which is also supplied to the comparator will be given as

$$V_{c1} = (f_1 - f_0) / K_v \text{ and } V_{c2} = (f_2 - f_0) / K_v \text{ respectively.}$$

where  $K_v$  is the voltage to frequency transfer coefficient of the VCO.

The difference between the two control voltage levels will be  $\Delta V_c = (f_2 - f_1) / K_v$

The reference voltage for the comparator is derived from the additional low pass filter and it is adjusted midway between  $V_{c1}$  and  $V_{c2}$ . Therefore, for  $V_{c1}$  and  $V_{c2}$ , comparator gives output '0' and '1', respectively.

### (v)AM detection:

 


Fig. 4.68 PLL used as AM demodulator

The PLL is locked to the carrier frequency of the incoming AM signal. Once locked the output frequency of VCO is same as the carrier frequency, but it is in unmodulated form. The modulated signal with 90° phase shift and the unmodulated carrier from output of PLL are fed to the multiplier. Since VCO output is always 90° out of phase with the incoming AM signal under the locked condition, both the signals applied to the multiplier are in same phase. Therefore, the output of the multiplier contains both the sum and the difference signals. The low pass filter connected at the output of the multiplier rejects high frequency components gives demodulated output. As PLL follows the input frequencies with high accuracy, a PLL AM detector exhibits a high degree of selectivity and noise immunity which is not possible with conventional peak detector type AM modulators.

**(vi) Frequency Translation:** Frequency translation means shifting the frequency of an oscillator by a small factor.

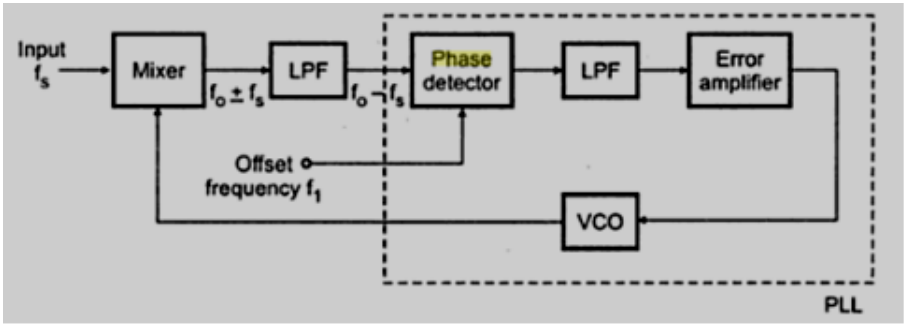


Fig . Block schematic for frequency translator using PLL

It consists of mixer, low pass filter and the PLL. The input frequency  $f_s$  which has to be shifted is applied to the mixer. Another input to the mixer is the output voltage of VCO,  $f_o$ . Therefore, the output of mixer contains the sum and difference signal ( $f_o \pm f_s$ ). The low pass filter connected at the output of mixer rejects the ( $f_o+f_s$ ) signal and gives only ( $f_o-f_s$ ) signal at the output. The ( $f_o-f_s$ ) signal is applied to the phase detector. Another input for phase detector is the offset frequency  $f_1$ . In the locked mode, the VCO output frequency is adjusted to make two input frequencies of phase detector equal. This gives  $(f_o-f_s) = f_1$  and  $f_o = f_s + f_1$ . By adjusting offset frequency  $f_1$  we can shift the frequency of the oscillator to the desired value.

**Unit IV****Analog to Digital And Digital to Analog Converters****Part A**

- 1. What would be produced by a DAC, whose output range is 0 to 10V and whose binary number is 10111100 (for a 8 bit DAC)? [ CO4-L1]**

$$\begin{aligned}V_0 &= 10V(1 \times 1/2 + 0 \times 1/2^2 + 1 \times 1/2^3 + 1 \times 1/2^4 + 1 \times 1/2^5 + 1 \times 1/2^6 + 0 \times 1/2^7 + 0 \times 1/2^8) \\ &= 10V(1/2 + 1/8 + 1/16 + 1/32 + 1/64) \\ &= 7.34 \text{ V}\end{aligned}$$

- 2. What is over sampling? [ CO4-L1]**

Oversampling is a process in which additional “oversampling factor-1” zeros are inserted in to the digital data.

- 3. Determine the number of comparators and resistors required for 8 bit flash type ADC. [ CO4-L3]**

The number of comparators required for 8 bit flash type ADC is  $2^{n-1}$  ( n is the number of bits ), hence we need  $2^{8-1}$  comparators.

i.e  $2^7 - 1 = 255$  comparators.

- 4. Mention two advantages of R-2R ladder type Digital to Analog converter when compared to weighted resistor type Digital to Analog converter. [ CO4-L1]**

- (i) More accurate selection and design of resistors R and 2R are possible
- (ii) The binary word length can be increased by adding required number of R-2R sections.


5. A 12 bit D/A converter has resolution of 20 mV/LSB. Find the full scale output voltage.[ CO4-L2]

$$\text{Resolution} = \frac{V_{OFS}}{2^n - 1}$$

$$20 = \frac{V_{OFS}}{2^{12} - 1}$$

Therefore,  $V_{OFS} = 5.1V$

 6. Draw the binary ladder network of DAC. If the value of the smaller resistance is 10k. What is the value of the other resistance? [CO4-L1]



7. What are the advantages of inverted R-2R (current type) ladder D/A converter over R-2R (voltage type) D/A converter. [ CO4-L1]

The most important advantage of the current mode or inverted ladder type of D/A converter is that the stray capacitance do not affect the speed of response of the circuit due to the constant ladder node voltages.

Speed performance is improved.

### 8. What is the need for electronic switches in D/A converter? [ CO4-L1]


The Switches which connects the digital binary input to the nodes of a D/A converter is an electronic switch. Although switches can be made of using diodes, Bipolar junction Transistors, Field Effect transistors or MOSFETs, there are four main configurations used as switches for DACs.

They are

- i) Switches using overdriven Emitter Followers.
- ii) Switches using MOS Transistor- Totem pole MOSFET Switch and CMOS Inverter Switch.
- iii) CMOS switch for Multiplying type DACs .
- iv) CMOS Transmission gate switches.

These configurations are used to ensure the high speed switching operations for different types of DACs.
 
### 9. Draw a sample and hold circuit. [ CO4-L1]



### 10. State the principle of single slope A/D converter. [ CO4-L1]

The single slope A/D converter compares the unknown analog input voltage with a reference voltage that begins at 0V and increases linearly with time.

**11. Mention any two applications of a D/A converter. [ CO4-L1]**

- i. Microprocessor interfacing
- ii. CRT graphics representation
- iii. Programmable power supplies
- iv. Digitally controlled gain circuits.

**12. For an n-bit flash type A/D converter, how many comparators are required? State the disadvantage of that type of converter. [CO4-L1]**

The number of comparators required is  $2^n - 1$ .

Disadvantage: The number of comparators required almost doubles for each added bit. The larger the value of n, the more complex is the priority encoder.

**13. What output voltage would be produced by a D/A converter whose output range is 0 to 10V and whose input binary number is 0110 for a 4 bit DAC. [CO4-L3]**

$$V_o = 10V (0 \times \frac{1}{2} + 1 \times \frac{1}{2^2} + 1 \times \frac{1}{2^3} + 0 \times \frac{1}{2^4})$$

$$= 10 ( \frac{1}{4} + \frac{1}{8} ) = 3.75 V$$

**14. What is the main drawback of dual slope ADC? [CO4-L2]**

The dual slope ADC has *long conversion time*. This is the main drawback of dual slope ADC.

**15. Define settling time of D/A converter. [CO4-L1]**

Settling time represents the time it takes for the output to settle within a specified band  $\pm(1/2)$  LSB of its final value

**16. What is meant by resolution of a DAC? [CO4-L2]**

Smallest change in voltage which may be produced at the output (or input) of the converter.

Resolution (in volts)  $( V_{FS} / 2^n - 1 ) = 1$  LSB increment

**17. Which is the fastest ADC? State the reason? [CO4-L2]**

Parallel comparator (Flash) A/D converter is the fastest ADC because the conversion takes place simultaneously rather than sequentially.

**18. Give the advantages of integrating type ADC. [CO4-L2]**

- (i) The integrating type of ADCs do not need a Sample/Hold circuit at the input.
- (ii) It is possible to transmit frequency even in noisy environment or in an isolated form.

**19. Define accuracy of a D/A CONVERTER.[CO4-L2]**

Absolute accuracy: It is the maximum deviation between the actual converter output and the ideal converter output.

Relative accuracy: It is the maximum deviation after gain and offset errors have been removed.

**20. Compare and contrast Binary ladder and R-2R ladder type DAC. [CO4-H1]**

Binary weighted resistor DAC	R-2R DAC
(i) Requires a wide range of resistor values. (ii) Due to higher values of resistor required for the LSB, the use of weighted resistor DAC in monolithic form restricted to 8-bits.	(i) Requires only two values to resistor. (ii) No such restriction as only two resistor values are used whatever may be the number of inputs.



**21. Define resolution time and conversion time of DAC. [CO4-L1]**

Resolution time: The resolution of a data converter is the smallest change in voltage which may be produced at the output or input of the converter.

Conversion time: It is defined as the total time required to convert a digital signal to analog signal.

**22. What is a sample and hold circuit? [CO4-L1]**

It samples an input signal and holds on to its last sampled value until the input is sampled again.

**23. What are the components of a sample and hold circuit? [CO4-L1]**

- (i) n-Channel E-MOSFET                      (ii) Control Voltage                      (iii) Capacitor

**24. What is sample period and hold period? [CO4-L1]**

Time period  $T_s$  during which the voltage across the capacitor is equal to the input voltage is called Sample period. Time period  $T_H$  during which the voltage across the capacitor is held constant is Hold Period.

**25. What are the applications of sample and hold circuit?[CO4-L1]**

- (i) Digital interfacing  
(ii) Analog to digital conversion  
(iii) Pulse code modulation systems

**26. What are the important specifications of converters? [CO4-L2]**

*Resolution:* The resolution of a converter is the smallest change in voltage which may be produced at the output (or input) of the converter.

*Linearity:* It gives us how close the converter output is to its ideal transfer characteristics.

*Accuracy :* Actual accuracy and Relative accuracy.

**Actual Accuracy:** It is the maximum deviation between the actual converter output and the ideal converter output.

**Relative Accuracy:** It is the maximum deviation after gain and offset errors have been removed.

**Monotonicity:** For a DAC, it is the one whose analog output increases for an increase in digital input.

**Settling time:** It represents the time it takes for the output to settle within a specified band.

### **Part-B**

#### **1. With neat block diagram, explain analog to digital converter & digital to analog converter.**

○ Most of the real-world physical quantities such as voltage, current, temperature, pressure and time etc. are available in analog form. Even though an analog signal represents a real physical parameter with accuracy, it is difficult to process, store or transmit the analog signal without introducing considerable error because of the superimposition of noise as in the case of amplitude modulation.

○ Therefore, for processing, transmission and storage purposes, it is often convenient to express this variable in digital form. It gives better accuracy and reduces noise. The operation of any digital communication system is based upon analog to digital (A/D) and digital to analog (D/A) conversion.

○ Figure highlights a typical application within which A/D and D/A conversion is used. The analog signal obtained from the transducer is band limited by antialiasing filter. The signal is then sampled at a frequency rate more than twice the maximum frequency of the band limited signal.

○ The sampled signal has to be held constant while conversion is taking place in A/D converter. This requires that ADC should be preceded by a sample and hold (S/H) circuit. The

ADC output is a sequence in binary digit. The micro-computer or digital signal processor performs the numerical calculations of the desired control algorithm.

○ The D/A converter is to convert digital signal into analog and hence the function of DAC is exactly opposite to that of ADC. The D/A converter is usually operated at the same frequency as the ADC. The output of a D/A converter is commonly a staircase. This staircase-like digital output is passed through a smoothing filter to reduce the effect of quantization noise.

○ The scheme given in Fig. 10.1 is used either in full or in part in applications such as digital audio recording and playback, computer, music and video synthesis, pulse code modulation transmission, data acquisition, digital multimeter, direct digital control, digital signal processing, microprocessor based instrumentation.

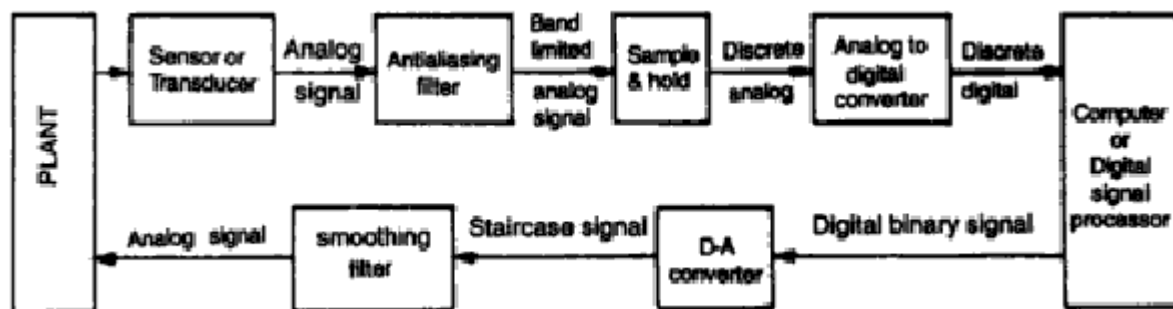


Fig. Circuit showing application of A/D and D/A converter

Both ADC and DAC are also known as data converters and are available in IC form. It may be mentioned here that for slowly varying signal, sometimes sample and hold circuit may be avoided without considerable error. The A-D conversion usually makes use of a D-A converter so we shall first discuss DAC followed by ADC.

**2. Define basic DAC techniques. What are the limitations in weighted resistor type D/A converters and explain how this problem can be solved in R-2R ladder D/A converters and inverted R-2R ladder technique and also derive the necessary equations. [CO4-H1-May - 2011) (Dec - 2011) ( May - 2012) ( May – 2014, May 2015)**

**Basic DAC:**

The schematic of a DAC is shown in Fig. The input is an n-bit binary word D and is combined with a reference voltage  $V_R$  to give an analog output signal. The output of a DAC can be either a voltage or current. For its voltage output DAC, the D/A converter is mathematically described as

$$V_o = K V_{FS} (d_1 2^{-1} + d_2 2^{-2} + \dots + d_n 2^{-n})$$

Where  $V_o$  — output voltage

$V_{FS}$  = full scale output voltage

$K$  = scaling factor usually adjusted to unity

$d_1 d_2 \dots d_n$  = n-bit binary fractional word with the decimal point located at the left

$d_1$  = most significant bit (MSB) with a weight of  $V_{FS}/2$

$d_n$  - least significant bit (LSB) with a weight of  $V_{FS}/2^n$

 


Fig: Schematic of a DAC

### Weighted resistor DAC: ( May - 2014)

- One of the simplest circuits shown in Fig. uses a summing amplifier with a binary weighted resistor network. It has n-electronic switches  $d_1, d_2, \dots, d_n$  controlled by binary input word. These switches are single pole double throw (SPDT) type.
- If the binary input to a particular switch is 1, the resistance is connected to the reference voltage ( $-V_R$ ). And if the input bit is 0, the switch connects the resistor to the ground. From Fig. 10.3(a), the output current for an ideal op-amp can be written as
- Comparing Eq (10.1) with Eq (10.2) it can be seen that if  $R_f = R$  then  $K = 1$  and  $V_{FS} = V_R$ .


The circuit shown in Fig.(a) uses a negative reference voltage. The analog output voltage is therefore positive staircase as shown in Fig. (b) for a 3-bit weighted resistor DAC.

**It may be noted that**

- (1) Although the op-amp in Fig. (a) is connected in inverting mode, it can also be connected in non-inverting mode.
- (2) The op-amp is simply working as a current to voltage converter.
- (3) The polarity of the reference voltage is chosen in accordance with the type of the switch used. For example, for TTL compatible switched, the reference voltage should be + 5V and the output will be negative.
- (4) The accuracy and stability of a DAC depends upon the accuracy of the resistors and the tracking of each other with temperature.

**Disadvantages:**

One of the disadvantages of binary weighted type DAC is the wide range of resistor values required. It may be observed that for better resolution, the input binary word length has to be increased. Thus, as the number of bit increases, the range of resistance value increases.

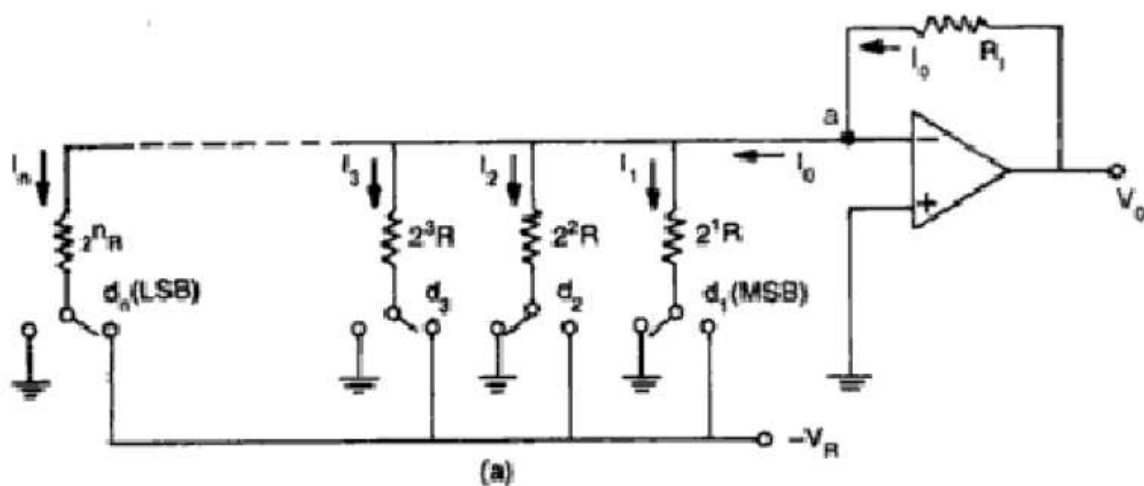

**Fig. (a) A simple weighted resistor DAC**


 


Fig (b) Transfer characteristics of a 3 bit DAC

 **R-2R Ladder circuit: (voltage mode R-2R)**

- Wide range of resistors are required in binary weighted resistor type DAC. This can be avoided by using R-2R ladder type DAC where only two values of resistor (R & 2R) are required.
- It is well suited for integrated circuit realization.
- The typical value of R ranges from 2.6 KΩ to 10 KΩ.
- For simplicity, consider a 3-bit DAC as shown in Fig (a), where the switch position  $d_1, d_2, d_3$  corresponds to the binary word 100. The circuit can be simplified to the equivalent form of Fig. Then, voltage at node C can be easily calculated by the set procedure of network analysis as



Fig(a) R-2R ladder DAC , Fig (b) Equivalent circuit of (a) , Fig (c) Equivalent circuit of (b)

The switch position corresponding to the binary word 001 in 3 bit DAC is shown in Fig, 10.6 (a). The circuit can be simplified to the equivalent form of Fig. 10.6 (b). The voltages at the nodes (A, B, C) formed by resistor branches are easily calculated in a similar fashion and the output voltage becomes

**Inverted R-2R Ladder: (Current mode R-2R)**

- In weighted resistor type DAC And R-2R ladder type DAC, current flowing in the resistors changes as the input data changes. More power dissipation causes heating, which in turn, creates non-linearity in DAC.
- This is a serious problem and can be avoided completely in Inverted R-2R ladder type DAC. A 3-bit Inverted R-2R ladder type DAC is shown in Fig. 10.7 (a) where the position of MSB end LSB is interchanged.
- Here each input binary word connects the corresponding switch either to ground or to the inverting input terminal of the op- amp which is also at virtual ground, Since both the terminals of switches are at ground potential, current flowing in the reactances is constant and independent of switch position, i.e. independent of input binary word.
- In Fig, 10.7 (a), when switch  $d_i$  is at logical 0 i.e., to the left, the current through  $2R$  resistor flows to the ground and when the switch  $d_i$  is at logical '1' ie., to the right, the current through  $2R$  sinks to the virtual ground. The circuit has the important property that the currents divides equally at each of the nodes. This is because the equivalent resistance to the right or to the left of any node is exactly  $2R$ . The division of the current is shown, in fig.10.7 (b).
- Consider a reference current of  $2\text{ mA}$ . Just to the right of node  $A$ . Similarly to the right of node  $B$ , the equivalent resistor is  $2R$ . Thus  $1\text{ mA}$  of current further divides to value  $0.5\text{ mA}$  at node  $B$ . Similarly, current divides -equally at node  $C$  to  $0.25\text{ mA}$ . The equal division of current in successive nodes remains the same in the 'inverted  $R$ - $2R$  ladder irrespective of the input binary word. Thus the Currents remain constant in each branch of the ladder.



 


Fig (a) Inverted R-2R ladder DAC

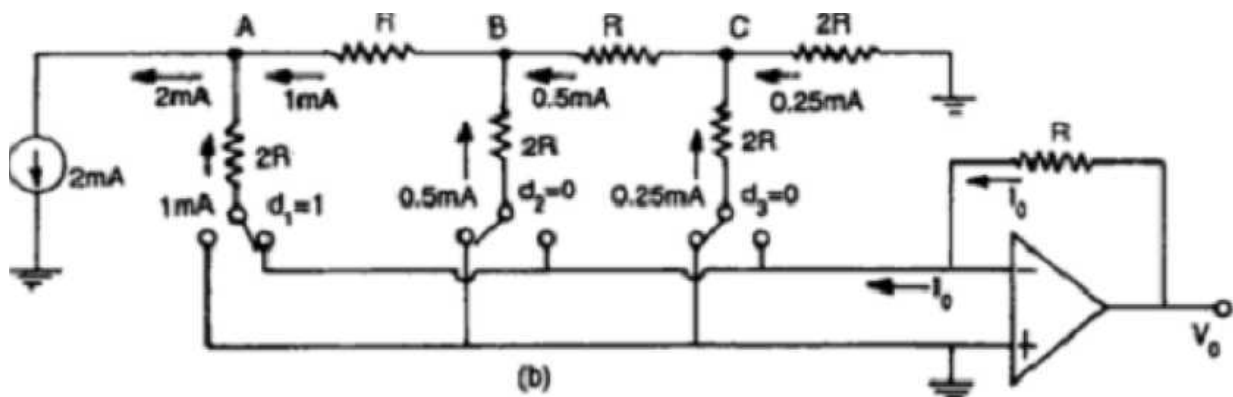


Fig (b) Inverted R-2R ladder DAC showing division of current for digital input word 001

**3. Define sample and hold circuit. With neat diagram explain sample and hold circuit and also give the advantages and applications. [CO4- H1- (May - 2010) ( Dec - 2010) (Dec - 2011) ]**

**Sample & hold circuit:**

o A sample and hold circuit samples an input signal and holds on to its Last sampled value until the input is sampled again. This type of circuit is very useful in digital interfacing and analog to digital and pulse code modulation systems.

- One of the simplest practical sample and hold circuit configuration is shown in Fig. 4.17 (a). The n-channel E-MOSFET works as a switch and is controlled by the control voltage  $v_c$  and the capacitor  $C$  stores the charge.
- The analog signal  $v_i$  to be sampled is applied to the drain of E-MOSFET and the control voltage  $v_c$  is applied to its gate. When  $v_c$  is positive, the E-MOSFET turns on and the capacitor  $C$  charges to the instantaneous value of input  $v_i$  with a time constant  $[R_0 + r_{DS(ON)}]C$ . Here  $R_0$  is the output resistance of the MOSFET when ON.
- Thus the input voltage  $v_i$  appears across the capacitor  $C$  and then at the output through the voltage follower  $A_2$ .
- During the time when control voltage  $v_c$  is zero, the E-MOSFET is off. The capacitor  $C$  is now facing the high input impedance of the voltage follower  $A_2$  and hence cannot discharge.
- The capacitor holds the voltage across it. The time period  $T_s$  the time during which voltage across the capacitor is equal to input voltage called **sample period**.
- The time period  $T_H$  during which the voltage across the capacitor is held constant is called **hold period**. The frequency of the control voltage should be kept higher than the input so as to retrieve the input waveform. A low leakage capacitor such as polystyrene, Mylar or Teflon should be used to retain the storage charge.

 


Fig. Sample and Hold Circuit

 


Fig. Input and Output waveforms

### **Advantages of Sample and Hold Circuits**

1. The primary use of the sample and hold circuit to hold the sampled analog input voltage constant during conversion time of A/D converter.
2. In case of multichannel ADCs, synchronization can be achieved by sampling signals from all channels at the same time.
3. It also reduces the crosstalk in the multiplexer.

### **Applications of Sample and Hold Circuits**

The applications of such sample and hold circuit are :

- Digital interfacing.
- Analog to digital converter circuits.
- Pulse modulation systems.
- In storage of outputs of a multiplexer between updates in data distribution systems.
- In reset-stabilised op-amps.

- In analog demultiplexers.


#### 4. Write ADC/DAC specifications. (or) Explain resolution, linearity, monotonicity, stability and settling time. [CO4-H2- Dec – 2012]

##### DAC /ADC specifications:

Both D/A and A/D converters are available with wide range of specifications. The various important specifications of converters generally specified by the manufacturers are analyzed.

**(1) Resolution:** The resolution of a converter is the smallest change in voltage which may be produced at the output (or input) of the converter. For example, an 8-bit D/A converter has  $2^8 - 1 = 255$  equal intervals. Hence the smallest change in output voltage is  $(1/255)$  of the full scale output range. In short, the resolution is the value of the LSB

 **(2) Linearity:** The linearity of an A/D or D/A converter is an important measure of its accuracy and tells us how close the output is to its ideal transfer characteristics. In an ideal DAC, equal increment in the digital input should produce equal increment in the analog output and the transfer curve should be linear.



**(3) Monotonicity:** A monotonic DAC is the one whose analog output increases for an increase in digital input. Figure. represents the transfer curve for a non-monotonic DAC, since the output decreases when input code changes from 001 to 010. A monotonic characteristic is essential in control applications, otherwise oscillations can result.

 


Fig. 10.18 A non-monotonic 3-bit DAC

**(4) Settling time:** The most important dynamic parameter is the settling time. It represents the time it takes for the output to settle within a specified band  $\pm (1/2)$  LSB of its final value following a code change at the input (usually a full scale change). It depends upon the switching time of the logic circuitry due to internal parasitic capacitances and inductances. Settling time ranges from 100 ns to 10  $\mu$ s depending on word length and type of circuit used.

**(5) Stability:** The performance of converter changes with temperature, age and power supply variations. So all the relevant parameters, such as offset, *gain*, linearity error and monotonicity must be specified over the full temperature and power supply ranges.

**5. Explain any two analog to digital converter(or) With neat circuit diagram. explain flash type and successive approximation type ADC. [CO4- H2 -(May - 2010) ( Dec - 2010) ( May – 2012, May 2015,16) ( Dec - 2013) (Nov/Dec 2016)]**

### DIRECT TYPE ADCs

#### 1. The parallel comparator/Flash

This is the simplest possible A/D Converter. It is at the same time the fastest and most expensive technique. Fig shows a 3-bit A/D converter.

The circuit consists of a resistive divider network, 8 op-amp comparators and a 8-line to 3-line priority encoder. The comparator and its truth table is shown in fig. A small amount of hysteresis is built into the comparator to resolve any problems that might occur if both inputs

were of equal voltage as shown in the truth table. Coming back to Fig. 10.10 (a), at each node of the resistive divider, a comparison voltage is available.

Since all the resistors are of equal value, the voltage levels available at the nodes are equally divided between the reference voltage  $V_R$  and the ground. The purpose of the circuit is to compare the analog input voltage  $V_{in}$  with each of the node voltages. The truth table for the flash type A/D converter is shown in fig. 10,10 (c).

### **Advantage:**

The circuit has the advantage of high speed as the conversion takes place simultaneously rather than sequentially. Typical conversion time is 100 ns or less.

Conversion time is limited only by the speed of the comparator and of the priority encoder. By using an Advanced Micro Devices AMD 686A comparator and a T1147 priority encoder, conversion delays of the order of 20 ns can be obtained.

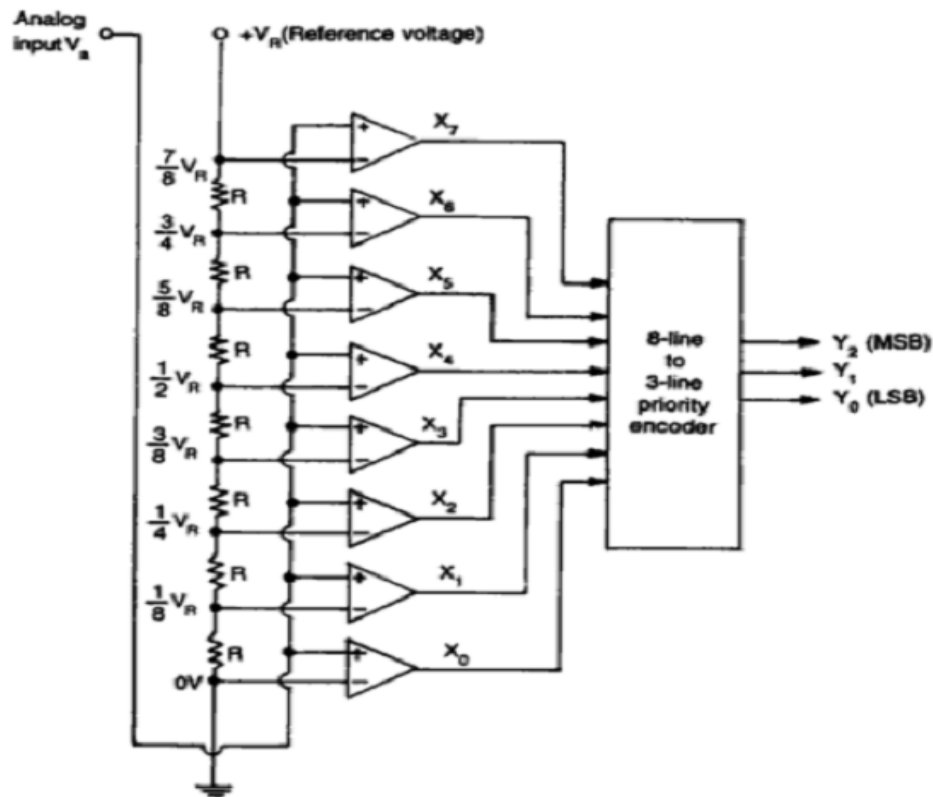


Fig. Flash type comparator

 


Fig. Comparator and its truth table

Input voltage $V_a$	$X_7$	$X_6$	$X_5$	$X_4$	$X_3$	$X_2$	$X_1$	$X_0$	$Y_2$	$Y_1$	$Y_0$
0 to $V_R/8$	0	0	0	0	0	0	0	1	0	0	0
$V_R/8$ to $V_R/4$	0	0	0	0	0	0	1	1	0	0	1
$V_R/4$ to $3 V_R/8$	0	0	0	0	0	1	1	1	0	1	0
$3 V_R/8$ to $V_R/2$	0	0	0	0	1	1	1	1	0	1	1
$V_R/2$ to $5 V_R/8$	0	0	0	1	1	1	1	1	1	0	0
$5 V_R/8$ to $3 V_R/4$	0	0	1	1	1	1	1	1	1	0	1
$3 V_R/4$ to $7 V_R/8$	0	1	1	1	1	1	1	1	1	1	0
$7 V_R/8$ to $V_R$	1	1	1	1	1	1	1	1	1	1	1

Fig. Truth table for flash type ADC


### Disadvantage

The number of comparators- approximately doubles for each added *bit*. Also the larger the value of  $n$ , the more complex is the priority encoder.


### 2. Successive approximation technique.

In this technique the basic idea is to adjust the DACs input code such that its output is within  $\pm \frac{1}{2}$  LSB of the analog input  $v_1$  to be A/D converted. the code that achieves this represents the desired ADC output.

The successive approximation method uses very efficient code searching strategy called binary search. It completes searching process for  $n$ -bit conversion in just  $n$  clock periods. It consists of a DAC, a comparator and a successive approximation register(SAR).

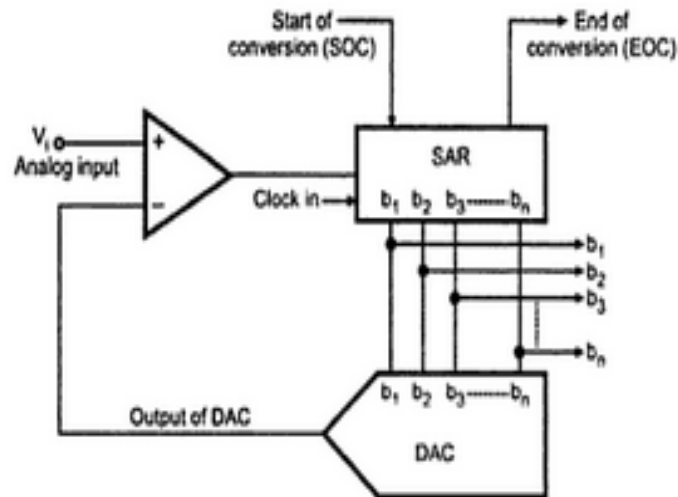

**Fig. 4.18 Block diagram of successive approximation A/D converter**

 

The searching code process in successive approximation method is similar to weighing an unknown material with a balance scale and a set of standard weights. Let us assume that we have 1 kg, 2 kg and 4 kg weights (SAR) plus a balance scale (comparator and DAC). Now we will see the successive approximation analogy for 3-bit ADC.

The analog voltage  $V_{in}$  is applied at one input of comparator. On receiving start of conversion signal (SOC) successive approximation register sets 3-bit binary code  $100_2$  ( $b_2=1$ ) as an input of DAC. This is similar process of placing the unknown weight on one platform of the balance and 4 kg weight on the other. The DAC converts the digital word 100 and applies its equivalent analog output at the second input of the comparator. The Comparator then



compares two voltages just like comparing unknown weight with 4 kg weight with the help of balance scale. If the input voltage is greater than the analog output of DAC, successive approximation register keeps  $b_2 = 1$  and makes  $b_1 = 1$  (addition of 2kg weight to have total 6 kg weight) otherwise it resets  $b_2 = 0$  and makes  $b_1 = 1$  (replacing 2 kg weight). The same process is repeated for  $b_1$  and  $b_0$ . the status of  $b_0, b_1$  and  $b_2$  bits gives the digital equivalent of the analog input.

The time for one analog to digital conversion must depend on both the clock's period  $T$  and number of bits  $n$ . It is given as,

$$T_C = T(n+1)$$

Where  $T_C$  = conversion time

$T$  = clock period

$N$  = number of bits

The dark lines in the figure shows setting and resetting actions of bits for input voltage 5.2v, on the basis of comparison. It can be seen from the Figure that one clock pulse is required for the successive approximation register to compare each bit. However an additional clock pulse is usually required to reset the register prior to performing a conversion.

**6. Explain any two indirect type ADC(or) With neat circuit diagram and wave form of output, explain the working of Dual slope A/D converter. [CO4-H1- (May - 2013) ( Dec - 2013) ( May – 2014, May 2015)]**

### 1. Dual Slope ADC

- Dual slope conversion is an indirect method for A/D conversion where an analog voltage and a reference voltage are converted into time periods by an integrator, and then measured by a counter. The speed of this conversion is slow but the accuracy is high. Fig. 3.142 shows a typical dual slope converter circuit.
- It consists of integrator (ramp generator), comparator, binary counter, output latch and reference voltage. The ramp generator input is switched between the analog input voltage  $V_i$

and a negative reference voltage,  $-V_{REF}$ . The analog switch is controlled by the MSB of the counter. When the MSB is a logic 0, the voltage being measured is connected to the ramp generator input. When MSB is logic 1, the negative reference voltage is connected to the ramp generator.

 
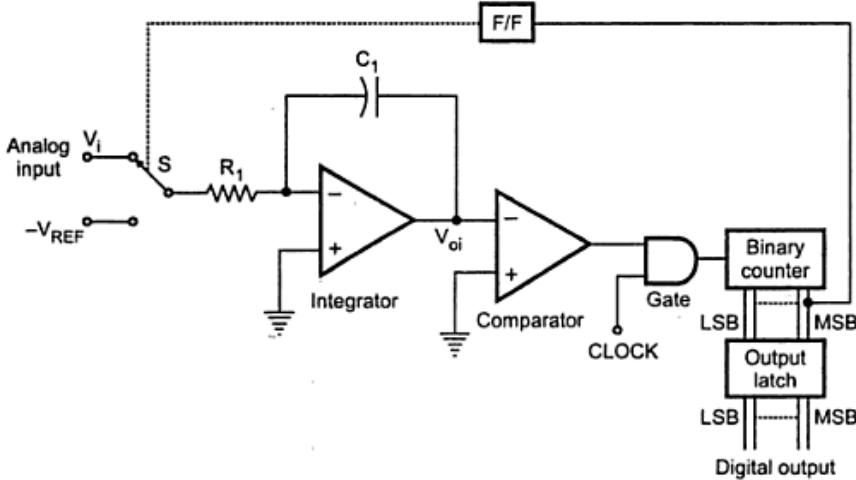


Fig. Integrator output voltage

At time  $t = 0$ , analog switch S is connected to the analog input voltage  $V_i$ , so that the analog input voltage integration begins. The output voltage of the integrator can be given as,

$$V_{oi} = \frac{-1}{R_1 C_1} \int_0^t V_i dt$$

$$= \frac{-V_i t}{R_1 C_1}$$

- where  $R_1 C_1$  is the integrator time
- The integrator output ramp down to a voltage constant and  $V_i$  is assumed constant over the integration time period. At the end of  $2^N$  clock periods MSB of the counter goes high. As a result the output of the flip-flop goes high, which causes analog switch S to be switched from  $V_i$  to  $-V_R$ . At this very same time the binary counter which has gone through its entire count sequence is reset.
- The negative input voltage ( $-V_R$ ) connected to the input of integrator causes the integrator output to ramp positive. When integrator output reaches zero, the comparator output voltage goes low, which disables the clock AND gate. This stops the clock pulses reaching the counter, so that the counter will be stopped at a count corresponding to the number of clock pulses in time  $t_2$ .
- $V$  and get back upto 0. Therefore, the charge voltage is equal to discharge voltage and we can write,

$$\frac{V_i t_1}{R_1 C_1} = \frac{V_R t_2}{R_1 C_1}$$

$$V_i t_1 = V_R t_2$$

$$t_2 = \frac{V_i t_1}{V_R}$$

The above equation shows that  $t_2$  is directly proportional only to the  $V_i$ . since  $V_R$  and  $t_1$  are constants. The binary digital output of the counter gives corresponding digital value for time period  $t_2$  and hence it is also directly proportional to input signal  $V_i$ . The actual conversion of analog voltage  $V_{in}$  into a digital count occurs during  $t_2$ . The control circuit connects the clock to the counter at the beginning of  $t_2$ . The clock is disconnected at the end of  $t_2$ . Thus the counter

contents is digital output. Hence we can write,

$$\text{digital output} = \left( \frac{\text{counts}}{\text{second}} \right) t_2$$

But from equation (5) we can write,

$$\text{digital output} = \left( \frac{\text{counts}}{\text{second}} \right) t_1 \left( \frac{V_i}{V_R} \right)$$

The counter output can then be connected to an appropriate digital display.

### **Advantages**

1. It is highly accurate.
2. Its cost is low.
3. It is immune to temperature caused variations in  $R_1$  and  $C_1$ .

### **Disadvantage**

The only disadvantage of this ADC is its speed which is low.

**2.Voltage to Time Converter ADC: (May - 2013) (or)With functional block diagram explain A/D converter using voltage to time converter with input and output waveforms.(Nov/Dec 2016)**

➤ The voltage to time conversion can be easily obtained by using voltage to frequency converter. Infact as the time is reciprocal of the frequency, the frequency output of voltage to frequency converter can be easily converted to time using a counter, monostable multivibrator and a latch. The block diagram of voltage to time converter is shown in the Fig.

A negative going pulse is used to trigger the monostable multivibrator. The same pulse is used to reset the counter. The input voltage is applied to the voltage to frequency converter. It produces the output pulses whose frequency is linearly proportional to the input.

When the trigger is applied to the monostable multivibrator its output goes high for the particular time period. At the same time the counter starts counting the pulses. After the time period of monostable multivibrator, its output goes low.

This output is applied to the latch which is negative edge triggered. Hence the counter output gets latched. The number of pulses which occur during the specific time period are counted and the latched output is then displayed by the decade counting. .

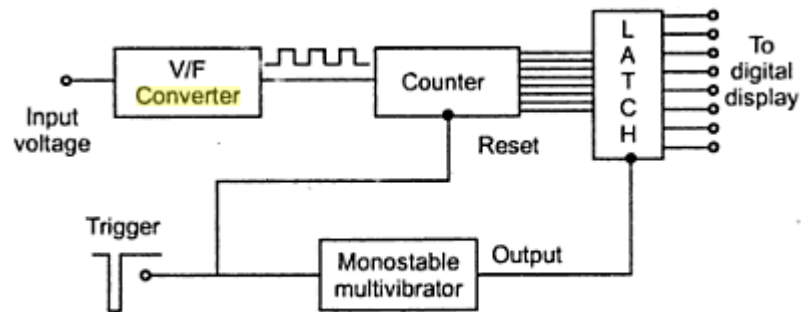


Fig. Voltage to Time converter

### 7.Explain Over sampling A/D converter. [CO4-L3-May - 2011)

In conventional A/D converters (the so-called Nyquist rate category) the input signal is sampled at a rate that is only twice that of the band of the input signal itself. The digital output, generated at the same rate, following to the sampling theorem, retains all the informative contents of the input signal which represents it. However, in order to avoid aliasing, the input signal must be band-limited by an anti-aliasing filter before sampling. Such analog filters suffer from limitations such as noise, distortion, group delay, and passband ripple; unless great care is taken, it is difficult for downstream A/D converters to achieve resolution beyond 18-bits. In many applications, brick-wall analog anti-aliasing filters and SAR A/D converters have been replaced by over sampling A/D converters with digital filters.

A/D converter where the input signal is sampled much faster than the Nyquist rate, is called an over sampling A/D converter. The signal bandwidth of the input signal is denoted by  $f_b$  and the Nyquist rate, which is the minimum sampling frequency required to avoid aliasing, equals

$$f_N = 2f_b$$

The over sampling ratio is defined as the ratio between the sampling frequency and the Nyquist rate. In other words, it indicates how much faster the input signal is sampled than minimally required by the Nyquist theorem,

$$OSR = \frac{f_s}{f_N} = \frac{f_s}{2f_b}$$

The principle of using over sampling is that by sampling the signal many times, errors due to noise and coarse quantization are averaged out. Through the use of loop-filter and feedback, the noise is shaped to high frequencies, which can be easily removed by digital filters.

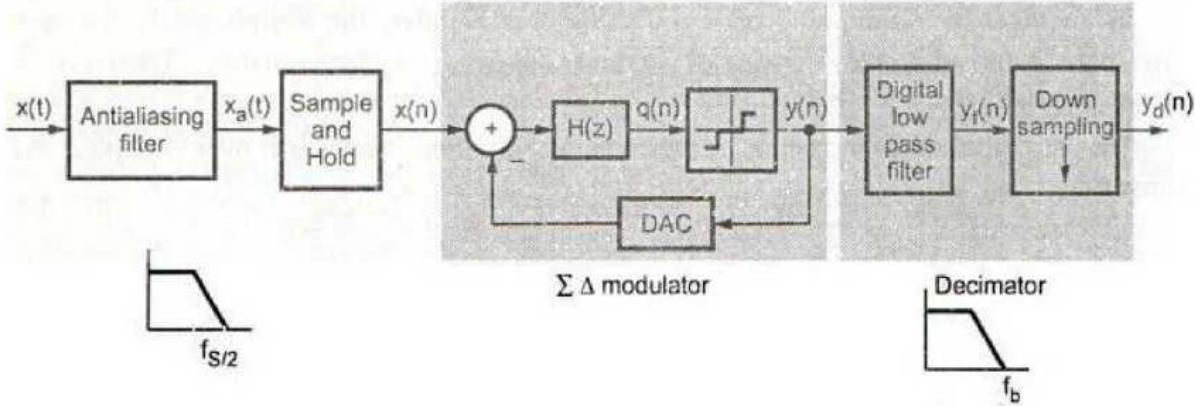


Fig. Block diagram of oversampled ADC

**Anti-aliasing filter (AAF):** It eliminates spectral components above half the sampling frequency from the input signal so that the modulator input signal is band-limited and the subsequent sampling operation does not alias input signals from higher frequencies into the band of interest.

**LA Modulator :** It performs the actual A/D conversion by means of sampling and quantizing the band-limited input signal as well as by filtering the quantization error from the internal quantizer out of the in-band. The internal feedback DAC is commonly implemented with the

same low resolution as the internal quantizer and thus does not introduce an additional quantization error.

**Decimation filter** : After quantization, a digital low pass filter uses decimation both to reduce the sampling frequency to a nominal rate and prevent aliasing at the new, lower sampling frequency. Quantized data words are output at a lower frequency (for example, 48 or 96 kHz). The decimation low pass filter removes frequency components beyond the Nyquist frequency of the output sampling frequency to prevent aliasing when the output of the digital filter is resampled (under-sampled) at the system's sampling frequency.

The decimator typically consists of two different blocks. First, a digital low pass filter is used to remove all the frequency components above — to avoid signal degradation due to aliasing in the down sampling block that follows the digital filter. This digital filter also removes all the quantization noise which does not fall inside the signal band. The digital filter operates in the digital domain and its output contains N-bits words.

The next block in the decimation filter down-samples the output of the digital filter. Down-sampling by a ratio of OSR can be done by simply keeping a sample and remove the next OSR-1 samples. Since the sampling rate of signal is changed, aliasing can occur. However, the decimation process does not result in loss of information since the digital filter removes all the components that could alias in the signal band.

### **8\_With necessary circuit diagram ,explain single slope ADC . [CO4-L3- May – 2014]**

#### **Single slope ADC:**

It consists of a ramp generator and BCD or binary counters. The Fig. 3.140 shows the single slope ADC

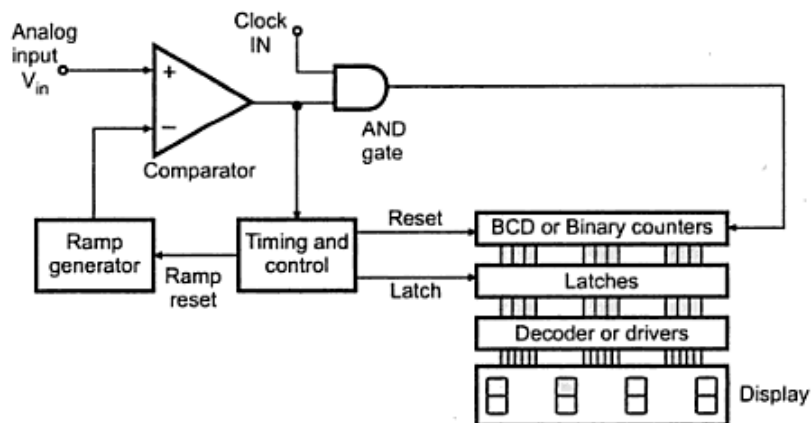


Fig. 3.140 Single slope ADC

At the start, the reset signal is provided to the ramp generator and the counters. Thus counters are resetted to 0's. The analog input voltage  $V_{in}$  is applied to the positive terminal of the comparator. As this is more positive than the negative input, the comparator output goes high. The output of ramp generator is applied to the negative terminal of the comparator. The high output of the comparator enables the AND gate which allows clock to reach to the counters and also this high output starts the ramp.

The ramp voltage goes positive until it exceeds the input voltage. When it exceeds  $V_{in}$ , comparator output goes low. This disables AND gate which in turn stops the clock to the counters. The control circuitry provides the latch signal which is used to latch the counter data. The reset signal resets the counters to 0's and also resets the ramp generator. The latched data is then displayed using decoder and a display device.

The main limitations of this circuit are,

Its resolution is less. Hence for applications which require resolution of 9 part in 20,000 or more, this ADC is not stable.

Variations in ramp generator due to time, temperature or input voltage sensitivity also cause a lot of problems



### 9.Explain switches for D/A converters.[CO4-L3-May 2016]

JFET can be used as an analog switch. For this, the gate-source voltage  $V_{GS}$  is restricted to two values : 0 V or a large negative voltage. The negative voltage must be equal to or more than  $V_{GS(OFF)}$  When  $V_{GS}$  is zero, the JFET operates in the ohmic region and JFET acts as a closed switch. When  $V_{GS}$  is more negative than  $V_{GS(OFF)}$ , the JFET is cut off and the switch is open.

#### 1.Shunt Switch

Fig. 8.5 shows JFET used as a shunt switch. The JFET is turned on and off by  $V_{GS}$ . When  $V_{GS} = 0$  V, JFET acts as a closed switch and  $R_{DS}$  is much less than  $R_D$ . Due to the voltage divider action  $V_{out}$  is very small, approximately equal to 0 V. When  $V_{GS}$  is more negative than  $V_{GS(OFF)}$ , the JFET acts as an open switch. Due to this  $V_{out}$  is equal to  $V_{in}$



 


Fig. 8.5 (a) Shunt switch

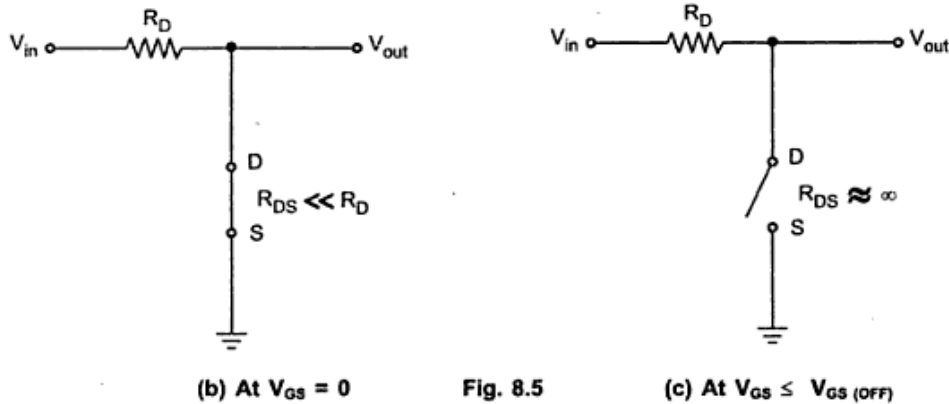

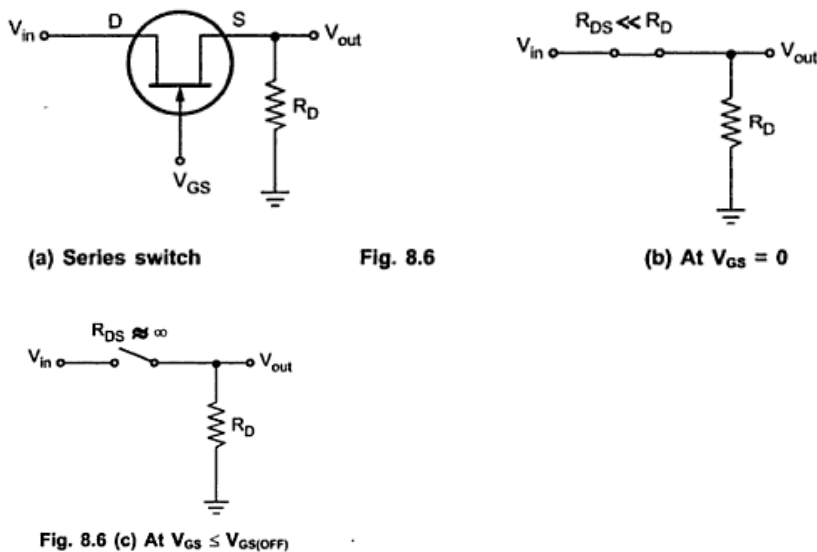Series Switch Fig. 8.6 shows JFET used as a series switch. When  $V_{GS} = 0$  V, the switch is closed and  $V_{out}$  equals  $V_{in}$ . When  $V_{GS}$  is equal to or more negative than  $V_{GS(off)}$ , the JFET is open and  $V_{out}$  is approximately zero.



**10.State the significance of using high speed sample and hold circuits.Explain its working principle.[CO4-L3-May 2016]**

 
 


Fig. 4.17 (b) Input and output waveforms

A sample and hold circuit samples an input signal and holds on to its last sampled value until the input is sampled again. This type of circuit is very useful in digital interfacing and analog to digital and pulse code modulation systems. One of the simplest practical sample and hold circuit configuration is shown in Fig. The n-channel E-MOSFET works as a switch and is controlled by the control voltage  $u$ , and the capacitor  $C$  stores the charge. The analog signal  $s$ , to be sampled is applied to the drain of E-MOSFET and the control voltage  $u$ , is applied to its gate. When  $u$ , is positive, the E-MOSFET turns on and the capacitor  $C$  charges to the instantaneous value of input  $e_i$  with a time constant  $[(R_o + r_{ds(on)})C]$ . Here  $R_o$ , is the output resistance of the voltage follower  $A$ , and  $r_{ds(on)}$  is the resistance of the MOSFET .

During the time when control voltage  $u$ , is zero, the EMOSFET is off. The capacitor  $C$  is now facing the high input impedance of the voltage follower  $A_2$  and hence cannot discharge. The capacitor holds the voltage across it. The time period  $T_s$ , the time during which voltage across the capacitor is equal to input voltage is called sample period. The time period  $T_H$  of  $u$ , during which the voltage across the capacitor is held constant is called hold period. The frequency of the control voltage should be kept higher than (at least twice) the input so as to retrieve the input from output waveform. A low leakage capacitor such as Polystyrene, Mylar, or Teflon should be used to retain the stored charge.

## Unit -V

### Waveform Generators and Special Function ICs


#### Part A

**1. State the two conditions for oscillations. [CO5-L1-April /May 2015]**

The two basic conditions for oscillations are :

- (i) The magnitude of the loop gain  $A_v\beta$  must be unity
- (ii) The total phase-shift of the loop gain  $A_v\beta$  must be equal to  $0^\circ$  or  $360^\circ$

 **2. Draw the functional block diagram of 723 regulator. [CO5-L1- April/May 2015]**



**3. What is the purpose of connecting a capacitor at the input and output side of an IC voltage regulator? [CO5-L3- Nov/Dec 2015]**

Two capacitors  $C_1$  and  $C_2$  are connected on the input and output sides. The output capacitor  $C_2$  helps in isolating the effect of transients that may appear on

the regulated supply line. C2 is a high quality tantalum capacitor with capacitance of around 1.0 $\mu$ F connected close to the regulator using short connecting leads in order to improve the stability of the output.

4. A Hartley oscillator has  $L_1 = 10$  mH,  $L_2 = 5$  mH and  $C = 200$  pF. Calculate the frequency of oscillation. [CO5-L3 –May/June 2016]

Here  $M=0$  then,  $L_T=L_1+L_2=15$ mH

$$f = \frac{1}{2\pi\sqrt{15 * 10^{-3} * 200 * 10^{-12}}}$$

$$f = \frac{1}{2\pi\sqrt{15 * 200 * 10^{-9}}}$$

$$f = \frac{1}{2\pi\sqrt{3000 * 10^{-9}}}$$


$$f = \frac{1}{2\pi\sqrt{3 * 10^{-6}}}$$

$$f = \frac{1}{2\pi\sqrt{3 * 10^{-6}}} = 92.59\text{HZ.}$$

5. What is an isolation amplifier? Mention its applications. [CO5-L1-May/June 2016]

An isolation amplifier is an amplifier in which, there is no physical contact between the input and output sections. These amplifiers are used in applications requiring very large common-mode voltage difference between the input and output sections. They find use in medical instrumentation applications, where the patient must be isolated and protected from leakage currents.

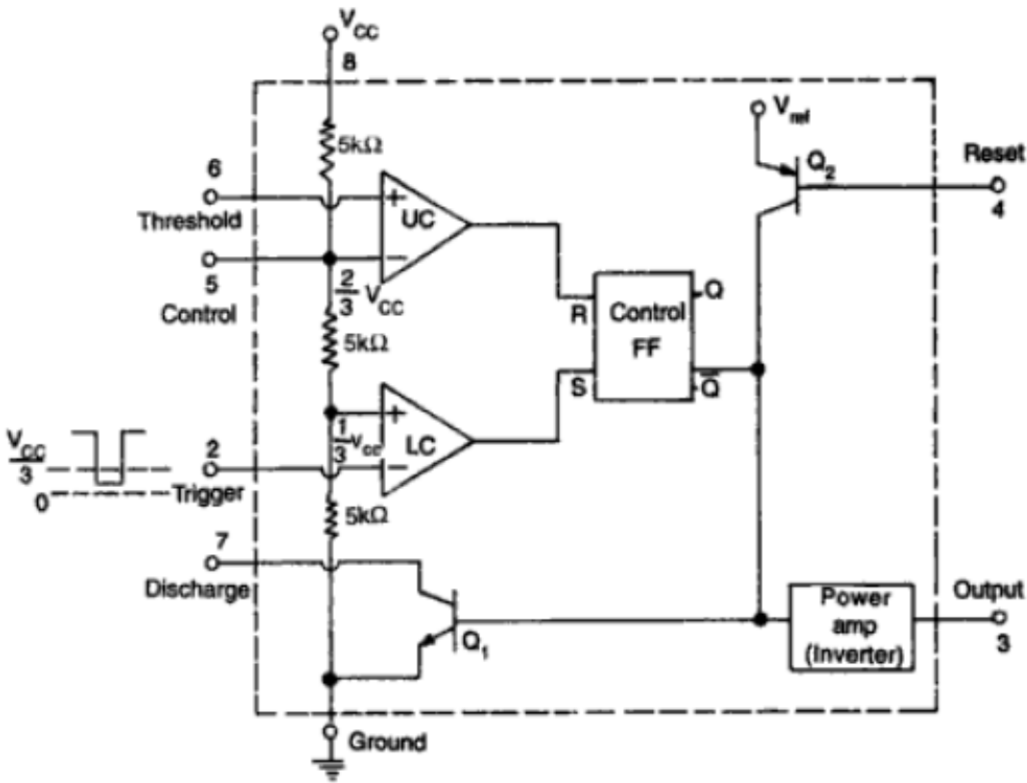6. Draw the block schematic of IC 555 timer. [CO5-L1-Nov/Dec 2016]



7. What is the function of a voltage regulator? Name few IC voltage regulators. [CO5-L2-Nov/Dec 2016]

The voltage regulators are classified into two types.

Linear voltage regulators	Switching regulators
1. Series voltage regulator	1. Transformer based type
2. Shunt voltage regulator	2. Buck switched type
	3. Boost switched type

**8. State the applications of 555 Timer IC. [CO5-L3]**

- Missing pulse detector (Monostable mode)
- Linear ramp generator (Monostable mode)
- Frequency divider (Monostable mode)
- FSK generator (Astable mode)
- Pulse position modulator (Astable mode)

**9. Define line regulation with respect to a voltage regulator. [CO5-L1]**

It is defined as the percentage change in the output voltage for a change in the input voltage. It is usually expressed in millivolts or as a percentage of the output voltage.

**10. Give the formula for period of oscillations in an op-amp astable circuit. [CO5-L2]**

The period of the output waveform is determined by the RC time constant of the two timing components and the feedback ratio established by the R1, R2 voltage divider network which sets the reference voltage level. If the positive and negative values of the amplifiers saturation voltage have the same magnitude, then  $t_1 = t_2$  and the expression to give the period of oscillation becomes:

$$\beta = \frac{R_2}{R_1 + R_2}$$

$$T = 2RC \ln\left(\frac{1+\beta}{1-\beta}\right)$$

Then we can see from the above equation that the frequency of oscillation for an Op-amp Multivibrator circuit not only depends upon the RC time constant but also upon the feedback fraction.



**11. Define duty cycle of a periodic pulse wave form. [CO5-L2]**

The pulse wave has only two possible states: on or off. The most often used pulse wave is the square wave, which spends exactly the same amount of time in the "on" position as it does in the "off" position.

The amount of time a pulse wave spends in the "on" position is called its **duty cycle**. A pulse wave which spends a quarter of the time on, then three quarters off before repeating, is said to have a 25% duty cycle.

**12. What are the limitations of IC 723 general purpose regulator? [CO5-L1]**

No built in thermal protection

It has no short circuit current limits.

**13. What is power amplifier? [CO5-L1]**

A power amplifier is an electronic device that receives an electrical signal and reprocesses it to amplify, or increase, its power. The boost in power is achieved by significantly increasing the input signal's voltage. A power amplifier is used to power an output source, such as a stereo speaker, a relay or a motor. One of the most common functions for a power amplifier is in audio applications.

**14. What are the limitations of three terminal regulators? [CO5-L1]**

No short circuit protection

Output voltage (positive or negative) is fixed.

**15. What is a switched capacitor filter? [CO5-L1]**

A switched capacitor filter is a three terminal element, which consists of capacitors, periodic switches and operational amplifiers and whose open circuit voltage transfer function represents filtering characteristics. The operation of the

filter is based on the ability of on-chip capacitors and MOS switches to stimulate resistors. It does not require external reactive components, capacitors or inductors.

**16. Define the duty in astable multivibrator using IC555. [CO5-L1]**

$$\text{Duty cycle } d = (T_c / T) \times 100$$

Where T is the total time period and T<sub>c</sub> is the charging period.

**17. What are the advantages of switched capacitor filter over active filters?**

**[CO5-L1]**

Low system cost

Low external component count

High accuracy


Good temperature stability

**18. What is Opto-coupler? Mention its applications. [CO5-L1]**

The opto-coupler circuit is a combined package of a photo-emitting device and a photo-sensing device. The basic opto coupler consists of a LED and a photo diode.

Application : This can be used as a coupler between any two stages for better electrical isolation. Capable of wide band signal transmission.

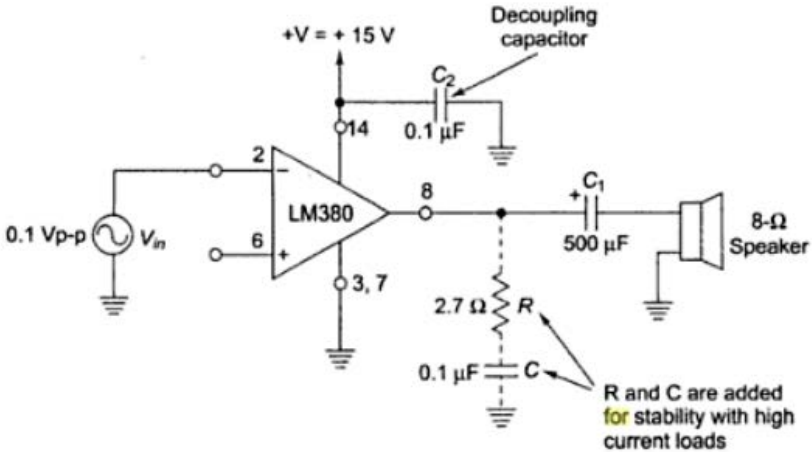
19. Draw the internal circuit for audio power amplifier. [CO5-L1]



20. What are the three different wave form generated by ICL8038?[CO5-L1]

Sine wave, Square wave and Triangular waveform

 21. Sketch the monostable multivibrator circuit diagram using IC555. [CO5-L2]



**22. What is meant by thermal shutdown applied to voltage regulator? [CO5-L1]**

Thermal shutdown means that the chip will automatically turn itself off if the internal temperature exceeds typically  $175^{\circ}\text{C}$

**23. What are the modes of operation of a timer? [CO5-L1]**

Astable mode and Bistable mode are the two operating modes of a timer.

**24. What are the advantages of 723 Voltage regulator? [CO5-L1]**

The 723 is a general purpose voltage regulator that overcomes the limitations of three terminal fixed voltage regulators. It is a low current device that can be employed for load current upto 10A or more by using external components. It can give adjustable output voltage in a wide range. It provides short circuit protection and current foldback using external components.

**25. What are the applications of LM 380? [CO5-L1]**

LM 380 is an audio power amplifier which is used for applications such as audio power amplifier, high gain audio amplifier, intercom system and bridge amplifier.

**26. Mention the advantage of foldback current limiting. [CO5-L1]**

Protecting the load from the over-current protection and protecting the regulator itself.

**27. Mention the advantages of switched capacitor circuits. [CO5-1]**

- i. The compatibility with CMOS process technology
- ii. Good accuracy of time constants and (iii) High linearity with voltage

**28. List all the special application IC's and its Functions**

<b>IC</b>	<b>Function</b>
SE555 / NE555	Timer
NE/SE 566	Voltage Controlled Oscillator
SE/NE560	Phase Locked Loop
LM560	Phase Locked Loop
SE/NE 5018	8-bit DAC
MC1408	8-bit DAC
ICL 8038	Function generator
LM137/LM337	Adjustable Negative Voltage regulators
IC 723	General Purpose Voltage Regulator
78xx/ 79xx	General Purpose Voltage Regulator
MC3420 /3250	Monolithic Switching Regulator
$\mu$ A 78S40	Monolithic Switching Regulator
LM 380	Audio Power amplifier
LM 733	Video amplifier
IC ISO 100	Isolation amplifier
AD293 ,AD294	Isolation amplifier

### Part B

#### 1. Explain the functional block diagram of IC 555 Timer.[CO5 – H1-May/June 2016)

The 555 is a monolithic timing circuit that can produce accurate & highly stable time delays or oscillation.


➤ The timer basically operates in one of two modes: either

1. Monostable (one - shot) multivibrator or
2. Astable (free running) multivibrator

➤ **The important features of the 555 timer are these:**

1. It operates on +5v to +18 v supply voltages
2. It has an adjustable duty cycle
3. Timing is from microseconds to hours
4. It has a current o/p

#### **PIN CONFIGURATION OF 555 TIMER:**

 

#### **Pin description:**

##### **Pin 1: Ground:**

All voltages are measured with respect to this terminal.

**Pin 2: Trigger:**

The o/p of the timer depends on the amplitude of the external trigger pulse applied to this pin.

**Pin 3: Output:**

➤ There are 2 ways a load can be connected to the o/p terminal either between pin3 & ground or between pin 3 & supply voltage

(Between Pin 3 & Ground → ON load )

(Between Pin 3 & + V<sub>cc</sub> → OFF load )

➤ When the input is low:

The load current flows through the load connected between Pin 3 & +V<sub>cc</sub> in to the output terminal & is called the sink current.

➤ When the output is high:

The current through the load connected between Pin 3 & +V<sub>cc</sub> (i.e. ON load) is zero. However the output terminal supplies current to the normally OFF load. This current is called the source current.

**Pin 4: Reset:**

The 555 timer can be reset (disabled) by applying a negative pulse to this pin. When the reset function is not in use, the reset terminal should be connected to +V<sub>cc</sub> to avoid any false triggering.

**Pin 5: Control voltage:**

An external voltage applied to this terminal changes the threshold as well as trigger voltage. In other words by connecting a potentiometer between this pin & GND, the pulse width of the output waveform can be varied. When not used, the control pin should be bypassed to ground with 0.01μF capacitor to prevent any noise problems.

**Pin 6: Threshold:**

This is the non inverting input terminal of upper comparator which monitors the voltage across the external capacitor.

**Pin 7: Discharge:**

This pin is connected internally to the collector of transistor  $Q_1$ .

When the output is high  $Q_1$  is OFF.

When the output is low  $Q_1$  is (saturated) ON.

**Pin 8: +Vcc:**

The supply voltage of +5V to +18V is applied to this pin with respect to ground.

**Block Diagram of 555 Timer IC:**

From the above figure, three 5k internal resistors act as voltage divider providing bias voltage of  $2/3 V_{cc}$  to the upper comparator &  $1/3 V_{cc}$  to the lower comparator. It is possible to vary time electronically by applying a modulation voltage to the control voltage input terminal (5).

**i) In the Stable state:**

The output of the control  $\overline{FF}$  is high. This means that the output is low because of power amplifier which is basically an inverter.  $Q = 1$ ; Output = 0


**(ii) At the Negative going trigger pulse:**

The trigger passes through  $(V_{cc}/3)$  the output of the lower comparator goes high & sets the FF.  $Q = 1$ ;  $Q = 0$

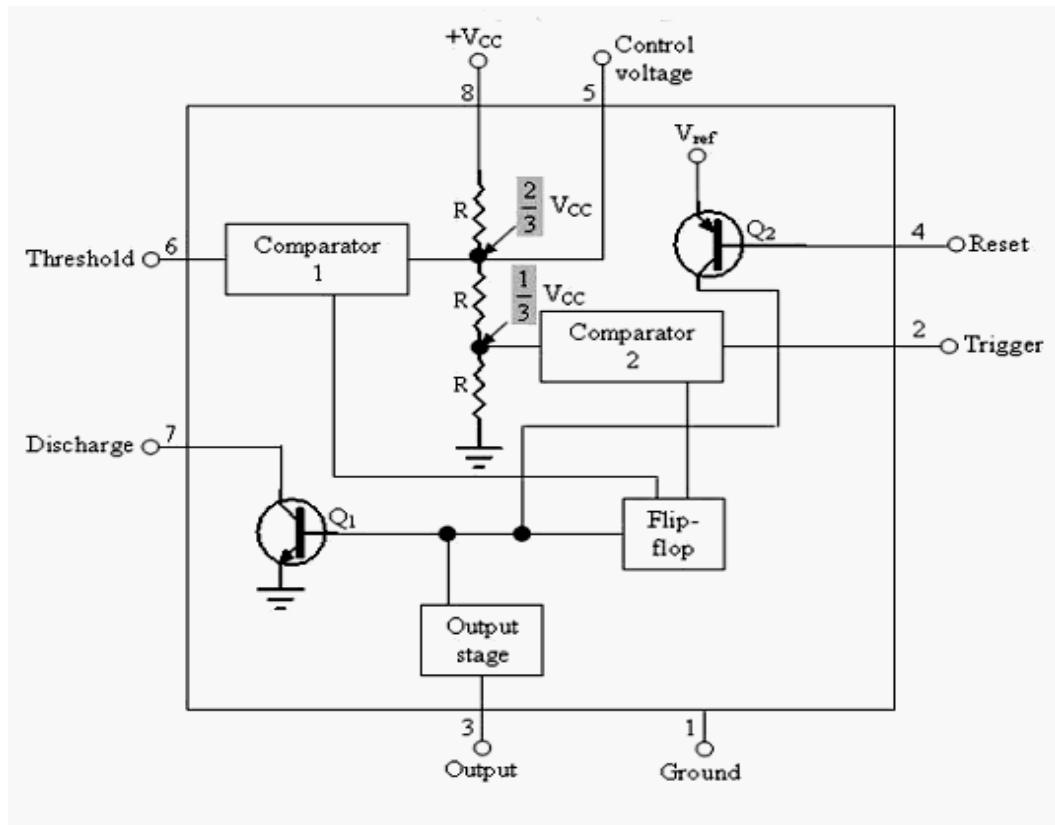**(iii) At the Positive going trigger pulse:** It passes through  $2/3V_{cc}$ , the output of the upper comparator goes high and resets the FF.  $Q = 0$ ;  $Q = 1$

The reset input (pin 4) provides a mechanism to reset the FF in a manner which overrides the effect of any instruction coming to FF from lower comparator





2. Draw the functional diagram and applications of Monostable multivibrator using IC 555 timer (May-2010),(Nov-2010),(May-2011),(Dec-2011),(Dec-2010)

### Monostable Multivibrator using IC 555:

The IC 555 timer can be operated as a monostable multivibrator by connecting an external resistor and a capacitor as shown in the Fig.

The circuit has only one stable state. When trigger is applied, it produces a pulse at the output and returns back to its stable state.

- The duration of the pulse depends on the values of R and C. As it has only one stable state, it is called one shot multivibrator.

**Operation:** The flip-flop is initially set i.e. Q is high. This drives the transistor  $Q_d$  in saturation. The capacitor discharges completely and voltage across it is nearly zero. The output at pin 3 is low.

- When a trigger input, a low going pulse is applied, then circuit state remains unchanged till trigger voltage is greater than  $1/3 V_{cc}$ . When it becomes less than  $1/3 V_{cc}$ , then comparator 2 output goes high.
- This resets the flip-flop so Q goes low and  $\bar{Q}$  goes high. Low Q makes the transistor  $Q_d$  off. Hence capacitor starts charging through resistance R. as shown by dark arrows in the Fig.
- The voltage across capacitor increases exponentially. This voltage is nothing but the threshold voltage at pin 6. When this voltage becomes more than  $2/3 V_{cc}$ , then comparator 1 output goes high.
- This sets the flip-flop i.e. Q becomes high and  $\bar{Q}$  low. This high Q drives the transistor  $Q_d$  in saturation. Thus capacitor C quickly discharges through  $Q_d$  as shown by dotted arrows in the Fig. So it can be noted that  $V_{out}$  at pin 3 is low at start, when trigger is less than  $1/3 V_{cc}$  it becomes high and when threshold is greater than  $2/3 V_{cc}$ . again becomes low, till next trigger pulse occurs. So a rectangular wave is produced at the output.


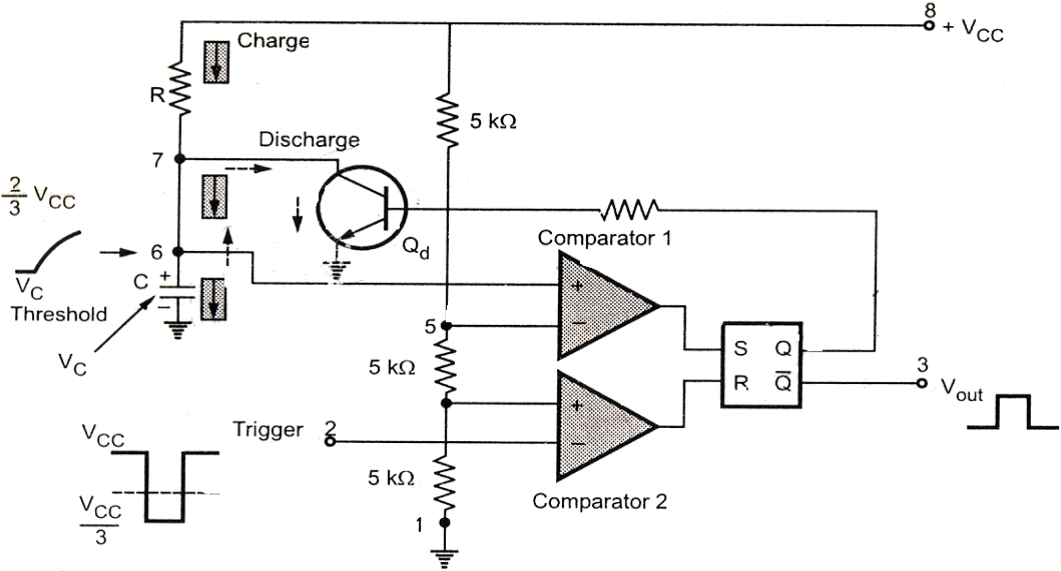


Fig. Monostable operation of 555

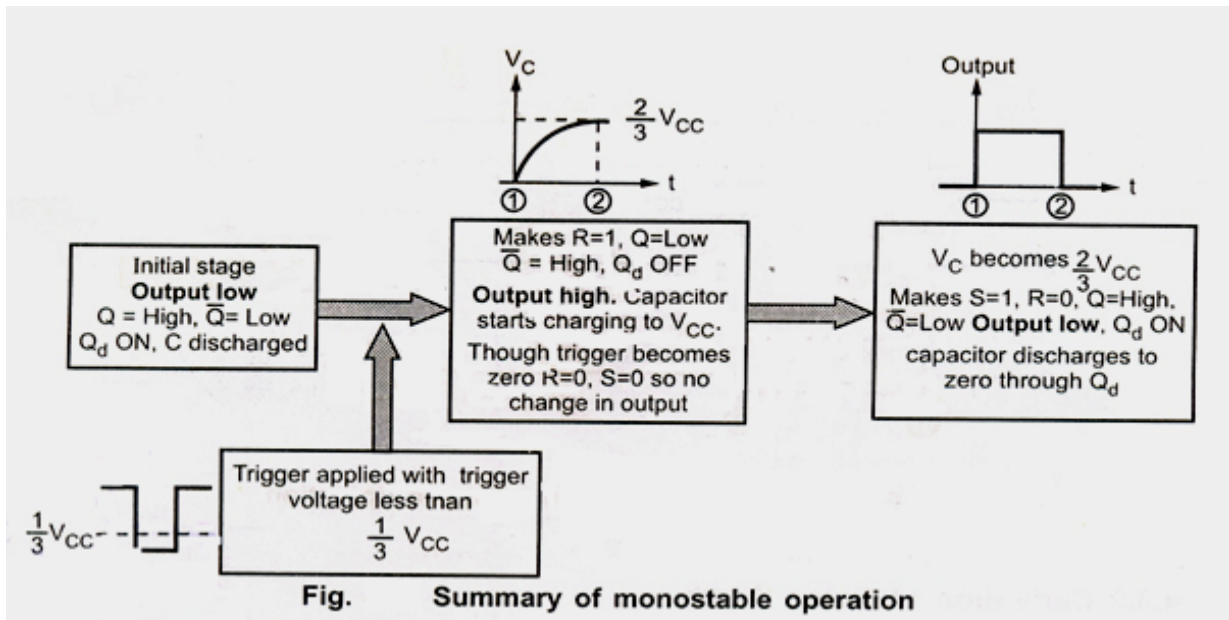**Summary of monostable operation:**

- The pulse width of this rectangular pulse is controlled by the charging time of capacitor. This depends on the time constant RC. Thus RC controls the pulse width. The waveforms are shown in the Fig.



### Calculation of Time period (or) Pulse Width:

- The voltage across the capacitor is given by

$$v_c = V_{cc}(1 - e^{-t/RC})$$

$$\text{At } t=T, v_c = (2/3)V_{cc}$$

$$\text{Therefore, } (2/3)V_{cc} = V_{cc}(1 - e^{-T/RC})$$

$$(2/3)V_{cc} = V_{cc} - V_{cc} e^{-T/RC}$$

$$(2/3)V_{cc} - V_{cc} = -V_{cc} e^{-T/RC}$$

$$-1/3 = e^{-T/RC}$$

Taking ln on both sides,

$$\ln(-1/3) = \ln e^{-T/RC}$$

$$-T/RC = \ln(3)$$

$$-T/RC = -1.09$$

$$\mathbf{T = 1.1RC \text{ (seconds)}}$$

## **Applications of Monostable Multivibrator**

### **Frequency Divider:**


We know that, in monostable multivibrator, application of trigger pulse gives a positive going pulse on the output. The same monostable circuit can be used as a frequency divider if the timing interval is adjusted to be longer than the period of the input signal, as shown in the Fig.

The Fig.shows monostable multivibrator as a divider-by-2 circuit. Here, timing interval 't' is kept slightly larger than the time period T of the trigger input signal.

The monostable multivibrator will be triggered by the first negative going edge of the trigger input, which will make output to go in its high state. The output will remain high. For the period equal to 'timing interval'.


As timing interval is greater than time period of the trigger input, output will still be high when the second negative going pulse occurs. The monostable will, however, be re-triggered on the third negative-going pulse.

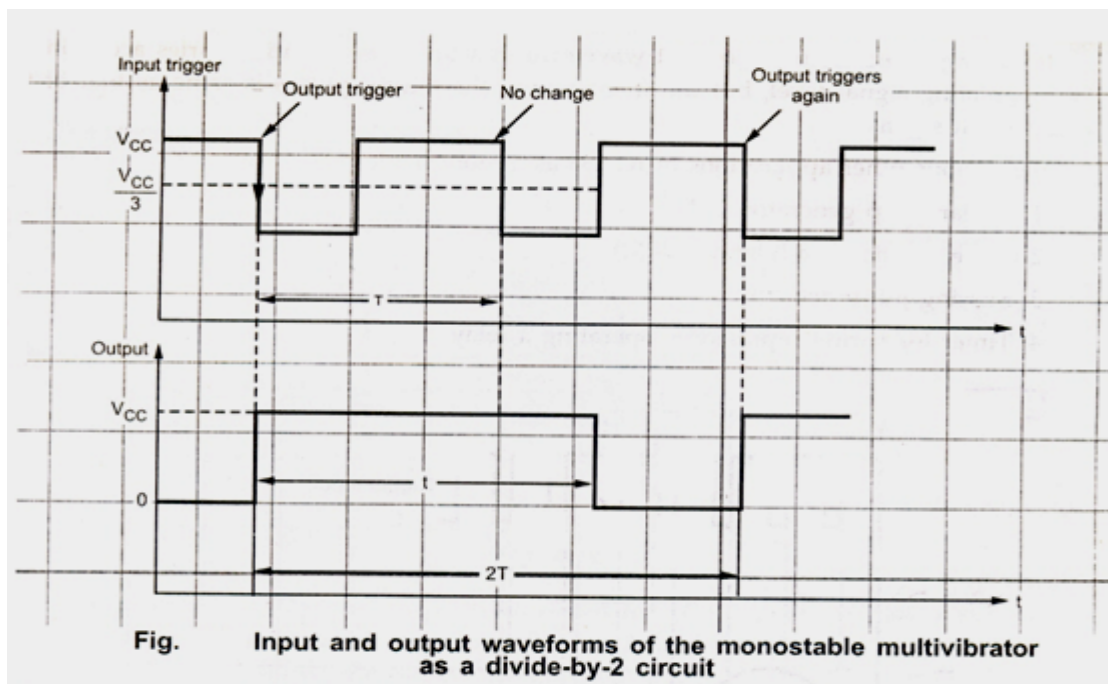Therefore, monostable triggers on every other pulse of the trigger input, so there is only one output for every two input pulses, thus trigger signal is, divided by 2. In this way, by adjusting the timing interval, the monostable circuit can be made integral fractions of the frequency of the input trigger signal.


 
### Pulse Width Modulation:

- Fig. shows pulse width modulator. It is basically a monostable multivibrator with a modulating input signal applied at the control voltage input (pin 5). Internally, the control voltage is adjusted to the  $\frac{2}{3} V_{CC}$ .
- Externally applied modulating signal changes the control voltage, and hence the threshold voltage level of the upper comparator (comparator 1). As a result, time period required to charge the capacitor up to threshold voltage levels changes giving pulse width modulated signals at the output.
- It may be noted from the output waveform that the pulse duration varies according to the modulating signal level, but the frequency of the output pulses is same as that of the trigger input signal.



### Other Applications of monostable multivibrator:

The various other applications of IC 555 as a monostable mode are,

1. Linear ramp generator
2. Pulse position modulation (PPM)
3. Missing pulse detector

**3. Draw the functional diagram of Astable multivibrator using IC 555 timer and explain astable mode of operation using 555 timer IC? (OR) With a neat circuit diagram and internal functional diagram explain the working of 555 timers in astable mode. (16)**  
**[CO5-H1-(May - 2010) (May-2010),(May-2011),(Dec-2011),(Nov-2012)]**

**Astable Multivibrator using IC 555:**

### OPERATION:

- The figure shows IC 555 connected as an astable multivibrator. The threshold input is connected to the trigger input. Two external resistances  $R_A, R_B$  and a capacitor  $C$  is used in the circuit.
- The circuit has no stable state.
- The circuit changes its state alternately. Hence the operation is also called free running non sinusoidal oscillator.
- When the flip-flop is set,  $Q$  is high which drives the transistor  $Q_d$  in saturation and the capacitor gets discharged. Now the capacitor voltage is nothing but the trigger voltage. So while discharging, when it becomes less than  $1/3 V_{CC}$  comparator 2 output goes high.
- This resets the flip-flop hence  $Q$  goes low and  $\bar{Q}$  goes high. The low  $Q$  makes the transistor off. Thus capacitor starts charging through the resistances  $R_A, R_B$  and  $V_{CC}$ . The charging path is shown by thick arrows in the Fig. As total resistance in the charging path is  $(R_A + R_B)$ , the charging time constant is  $(R_A + R_B) C$ .
- The capacitor voltage is also a threshold voltage. While charging, capacitor voltage increases i.e. the threshold voltage increases. When it exceeds  $2/3 V_{CC}$ , then the comparator 1 output goes high which sets the flip-flop. The flip-flop output  $Q$  becomes high and output at pin 3 i.e.  $\bar{Q}$  becomes low.
- High  $Q$  drives transistor  $Q_d$  in saturation and capacitor starts discharging through resistance  $R_B C$  and transistor  $Q_d$ . This path is shown by dotted arrows in the Fig. Thus the discharging time constant is  $R_B C$ .



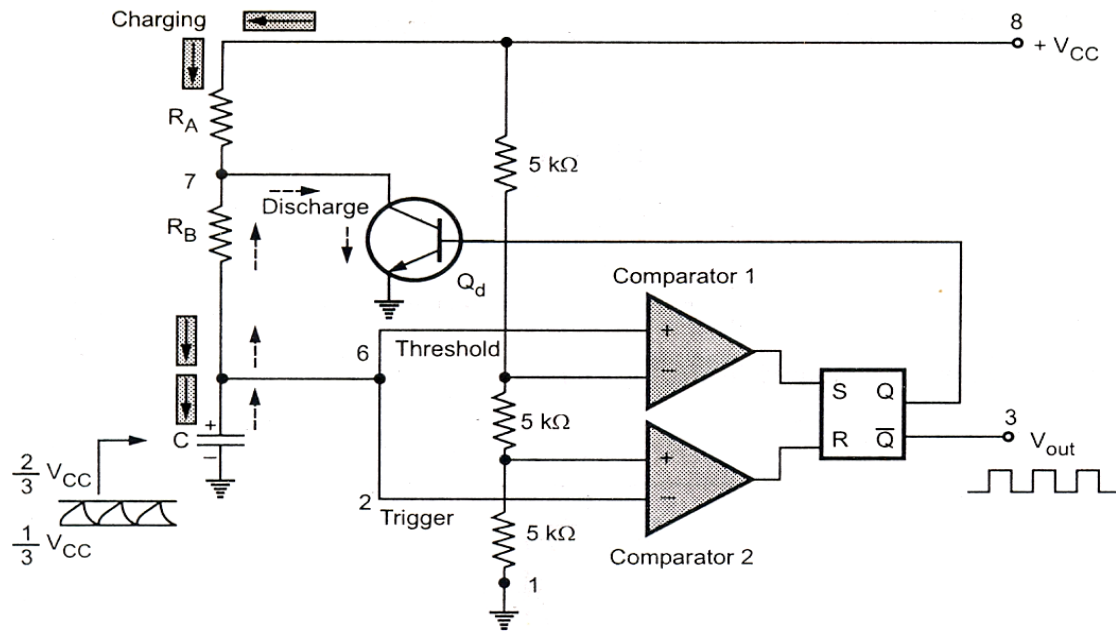


Fig. Astable operation of 555

- When capacitor voltage becomes less than  $\frac{1}{3} V_{CC}$  comparator 2 output goes high, resetting the flip-flop. This cycle repeats. Thus when capacitor is charging, output is high while when it is discharging the output is low. The output is a rectangular wave. The capacitor voltage is exponentially rising and falling. The waveforms are shown in the Fig.

### Calculation of T:

The capacitor voltage for a low pass RC circuit subjected to a step input of  $V_{CC}$  is

$$v_C = V_{CC}(1 - e^{-t/RC})$$

The time  $t_1$  taken by the circuit to charge from 0 to  $(\frac{2}{3})V_{CC}$  is,

$$(\frac{2}{3})V_{CC} = V_{CC}(1 - e^{-t_1/RC})$$

$$(\frac{2}{3})V_{CC} - V_{CC} = -V_{CC} e^{-t_1/RC}$$

$$-\frac{1}{3} V_{CC} = -V_{CC} e^{-t_1/RC}$$

$$\frac{1}{3} = e^{-t_1/RC}$$

Taking ln on both sides

$$\ln(1/3) = \ln(e^{-t_1/RC})$$

After simplifying we get,

$$t_1 = 1.09 RC$$

The time  $t_2$  to charge from 0 to  $(1/3)V_{CC}$

$$(1/3)V_{CC} = V_{CC}(1 - e^{-t_2/RC})$$

$$t_2 = 0.405RC$$

So the time to charge from  $(1/3)V_{CC}$  to  $(2/3)V_{CC}$  is,

$$(1/3)V_{CC} = V_{CC}(1 - e^{-t_2/RC})$$

$$t_{HIGH} = t_1 - t_2$$

$$t_{HIGH} = 1.09RC - 0.405RC = 0.69RC$$

So, for the given circuit,

$$t_{HIGH} = 0.69(R_A + R_B)C$$

The output is low while the capacitor discharges from  $(2/3)V_{CC}$  to  $(1/3)V_{CC}$  and the voltage across the capacitor is given by

$$(1/3)V_{CC} = (2/3)V_{CC}e^{-t/RC}$$

$$\text{Solving we get, } t = 0.69 RC$$

$$\text{So, for the given circuit, } t_{LOW} = 0.69 R_B C$$

Notice that  $R_A$  and  $R_B$  are in the charging path, but only  $R_B$  is in the discharging path. Therefore, total time

$$T = t_{HIGH} + t_{LOW}$$

$$T = 0.69(R_A + R_B)C + 0.69 R_B C$$

$$= 0.69R_A C + 0.69R_B C + 0.69 R_B C$$



$$T = 0.69(R_A + 2R_B)C$$

$$\text{So, } f = 1/T = 1.45 / [(R_A + 2R_B)C]$$
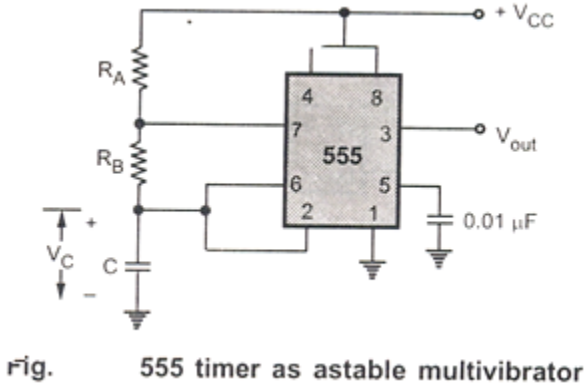 
### **Duty Cycle:**

The high output remains for longer period than low output.

The ratio of high output period and low output period is given by a mathematical parameter called Duty cycle. It is defined as the ratio of ON time.i.e. high output to the total time of one cycle.




#### 4. Explain Applications of astable multivibrator. [CO5- L3]

##### Astable Multivibrator Applications:
 
##### (a) Square wave oscillator:(Schmitt Trigger)

➤ With out reducing  $R_A = 0$  ohm, the astable multivibrator can be used to produce square wave output. Simply by connecting diode D across Resistor  $R_B$ . The capacitor C charges through  $R_A$  & diode D to approximately  $2/3 V_{cc}$  & discharges through  $R_B$  &  $Q_1$  until the capacitor voltage equals approximately  $1/3 V_{cc}$ , then the cycle repeats.

➤ To obtain a square wave output,  $R_A$  must be a combination of a fixed resistor & potentiometer so that the potentiometer can be adjusted for the exact square wave.



##### (b) Free – running Ramp generator:

- The astable multivibrator can be used as a free – running ramp generator when resistor  $R_A$  &  $R_B$  are replaced by a current mirror.
- The current mirror starts charging capacitor C toward  $V_{cc}$  at a constant rate.


- When voltage across **C equals to  $2/3 V_{cc}$** , upper comparator turns transistor  $Q_1$  ON & C rapidly discharges through transistor  $Q_1$ .
- When voltage across **C equals to  $1/3 V_{cc}$** , lower comparator switches transistor OFF & then capacitor C starts charging up again..
- Thus the charge – discharge cycle keeps repeating.
- The discharging time of the capacitor is relatively negligible compared to its charging time.
- The time period of the ramp waveform is equal to the charging time & is approximately is given by,

$$T = V_{cc}C/3I_C \dots\dots\dots (1)$$

$$I_C = (V_{cc} - V_{BE})/R = \text{constant current}$$

Therefore the free – running frequency of ramp generator is

$$f_0 = 3I_C/ V_{cc} C$$

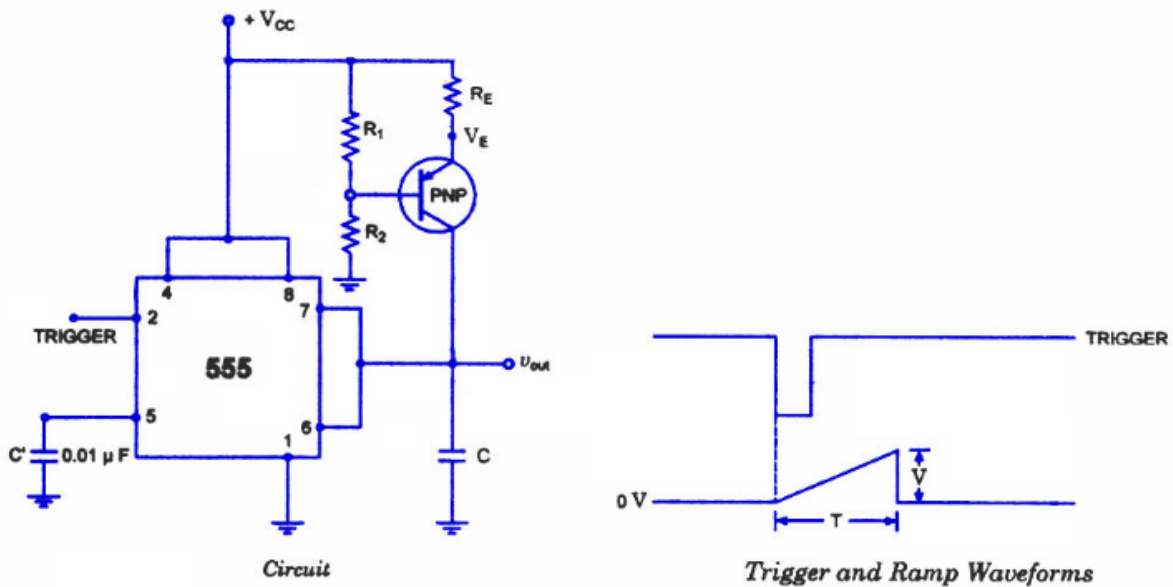

*Ramp Generator Using The Timer 555*

**5. Draw the circuit using op-amp to generate triangular wave. Explain its operation.[CO5 – L3-May – 2011]**


**TRIANGULAR WAVE GENERATOR**

Figure 7.10(a) shows the circuit of a triangular wave generator. It consists of two op-amps and several passive components. The op-amp  $A_1$  forms a non-inverting comparator with hysteresis, which is a Schmitt Trigger. The op-amp  $A_2$  forms an integrator which integrates the output obtained from the Schmitt trigger. The op-amp  $A_1$  is a two level comparator whose outputs are determined by  $\pm V_{sat}$ . The square-wave output from  $A_1$  is applied to the (-)ve input terminal of the op-amp  $A_2$ . The output of  $A_2$  is a triangular wave, and it is fed back as an input to the comparator  $A_1$  through a voltage divider network formed by  $R_2$  and  $R_3$ .

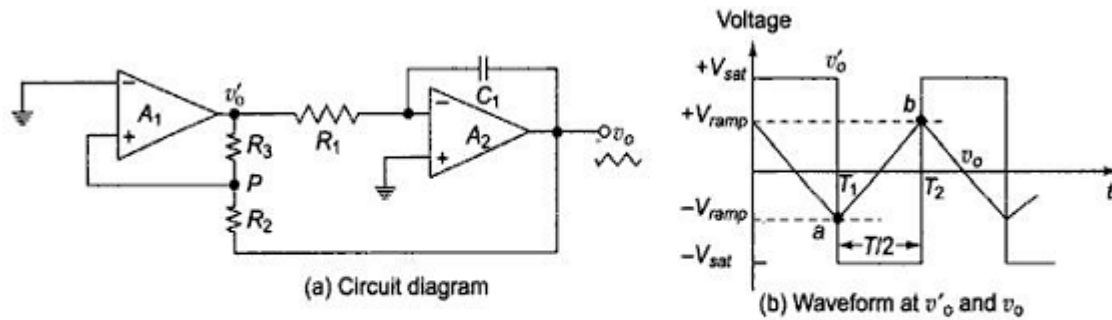**Loop Analysis :**

Let us consider that the output  $v'_0$  of comparator  $A_1$  is  $+V_{sat}$  initially. The integrator integrates  $+V_{sat}$  and produces a negative going ramp at its output as shown in Fig. 7.10 (b). Hence, the voltages at the two ends of the voltage divider formed by  $R_2 - R_3$  are  $+V_{sat}$  at the output of  $A_3$  and  $V_{sat}$  at the output of  $A_2$ . At the instant  $t = T_1$ , when the negative going ramp reaches a value of  $V_{ramp}$ , represented as point a in Fig.7.10 (b), the effective value at the point P becomes slightly less than 0V. This switches the op-amp  $A_1$  to its negative saturation level  $-V_{sat}$ .

With the output of  $A_1$  at  $V_{sat}$  the op-amp  $A_2$  starts integrating and increases its output in the positive direction. At the instant  $t = T_2$  shown as point b in Fig.7.10 (b) the voltage at P becomes just more than 0V. This switches the output of op-amp  $A_1$  from  $-V_{sat}$  to  $+V_{sat}$ . This cycle repeats itself, and generates a triangular waveform. The frequency of the waveform is determined by the RC value of the integrator formed by op-amp  $A_2$  and the saturation voltage levels  $\pm V_{sat}$  of comparator op-amp  $A_1$ .



Triangular waveform generator (a) Circuit diagram and (b) Waveforms at  $v'_o$  and  $v_o$

6. Draw the circuit using op-amp to generate sawtooth wave. Explain its operation. [CO5-L3-May 2016]


### SAWTOOTH WAVE GENERATOR

The saw tooth wave refers to a waveform with its rise time being many times longer than the corresponding fall time or fall time very longer as compared to the rise time. Triangular wave generator can be modified to produce a saw tooth waveform.

The saw tooth wave generator circuit is shown in Fig. 7.12(a). The op-amp  $A_1$  functions as a ramp generator and the op-amp  $A_2$  function as a comparator. The input reference signal  $V_i$  of value less than zero is connected to the inverting input of the op-amp. Since  $V_i$  is negative, the output of op-amp  $A_1$  can only ramp up. The rate of raise is given by

$$V_{OR}/t = V_i/R_iC$$

The ramp voltage  $V_{OR}$  is monitored by the comparator  $A_2$ . The output  $V_{OR}$  is connected to the non-inverting terminal of op-amp  $A_2$ , and a reference voltage set by a potentiometer  $V_{ref}$  is connected to the inverting input of comparator. When the capacitor  $C$  charges, and when the voltage is  $V_{OR}$  below  $V_{ref}$  the output of comparator is negative. Then the transistors  $Q_1$  and  $Q_2$  do not conduct. The diodes  $D_1$  and  $D_2$  protect the transistors from excessive reverse bias voltages.

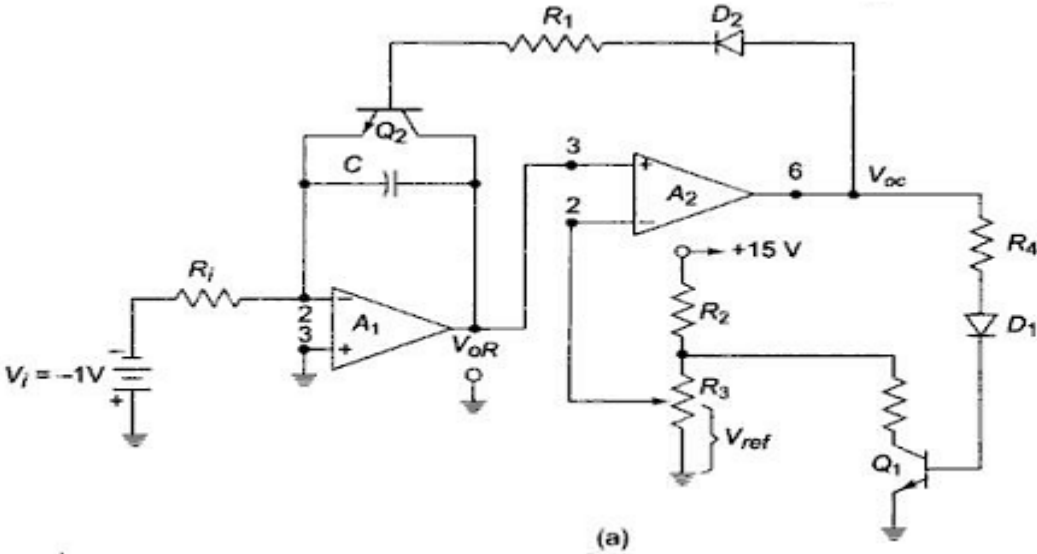

When  $V_{OR}$  rises and just exceeds  $V_{ref}$ , the output  $V_{OC}$  of comparator goes to positive saturation. This action forward biases the transistor  $Q_2$  into saturation. The saturated transistor then acts as a switch across the capacitor  $C$ , which charges quickly making the output  $V_{oc}$  come down essentially to 0V.

The positive saturation  $V_{oc}$ , of  $A_2$  also makes the transistor  $Q_1$  ON, and the  $V_{ref}$  or negative input of op-amp  $A_2$  drops to 0V. As the capacitor  $C$  discharges rapidly making  $V_{OR}$  zero volts, it drops below  $V_{ref}$ . This causes the comparator output to become negatively saturated. This action switches the transistor (22 OFF, and  $C$  begins charging linearly, and the cycle repeats.

The sawtooth output waveform is shown in fig. Fig shows the sawtooth waveform designing method. The circuit can also be operated as a current-controlled sawtooth waveform generator by applying an external control current sink  $I_s$  at the (-) input terminal of op-amp  $A_1$  is shown in fig. Then,

$$f = I_s / CV_{ref}$$




Here, the op-amp A1 can preferably be a FET input op-amp with low bias current and good slew rate.

**7. Describe in detail the working principle of IC 8038 function generator.[CO5- L2-Dec – 2011]**

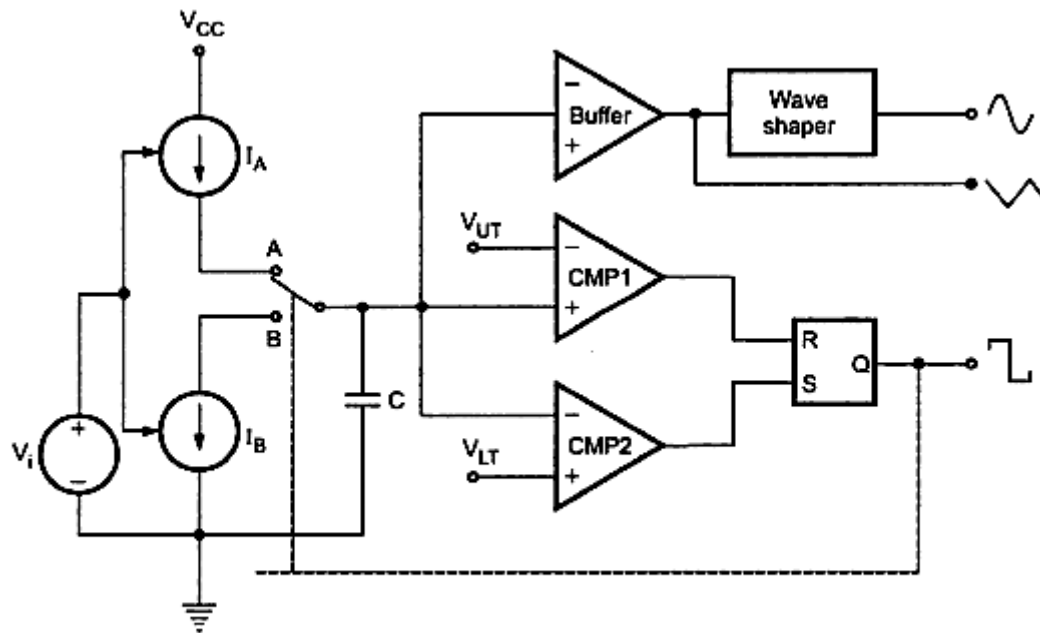**ICL8038 FUNCTION GENERATOR**

Function Generator ICL 8038 Function generators are designed to provide the basic waveforms such as square wave, triangular wave and sine wave. They are also called as waveform generators. The monolithic function generators provide these basic waveforms with a minimum number of external components reducing complexity, but increasing the reliability of the circuit. They find application in communication, telemetry, electronic music, and testing and calibration in the laboratory. In function generators, VCO (voltage controlled oscillator) generates the triangular and square waves. The triangular wave is passed through the on chip wave shaper to generate a sine wave. The sawtooth and pulse waveforms are generated by

configuring the oscillator for a highly asymmetric duty cycle.



**Simplified block diagram of ICL 8038 function generator**

**8. Explain in detail about features and internal structure of IC 723 with block diagram? [CO5 – L2-May 2016]**


**General purpose linear IC723 regulator.**

The three terminal regulators discussed earlier have the following limitations: 1. Not short circuit protection 2. Output voltage (positive or negative) is fixed. These limitations have been overcome in the 723 general purpose regulator, which can be adjusted over a wide range of both positive or negative regulated voltage. This IC is inherently low current device, but can be boosted to provide 5 amps or more current by connecting external components. The limitation of 723 is that it has no in-built thermal protection. It also has no short circuit current limits.

Figure shows the functional block diagram of a 723 regulator IC. It has two separate sections. The series diode, a constant current source and reference amplifier produce a fixed voltage of about 7 volts at the terminal V. The constant current source forces the generator to operate at a

fixed point so that the device outputs a fixed voltage. The other section of the IC consists of an error amplifier, a series pass transistor  $Q_1$ , and a current limit transistor  $Q_2$ . The error amplifier compares a sample of the output voltage applied at the INV input terminal to the reference voltage  $V_{ref}$  applied at the NI input terminal.
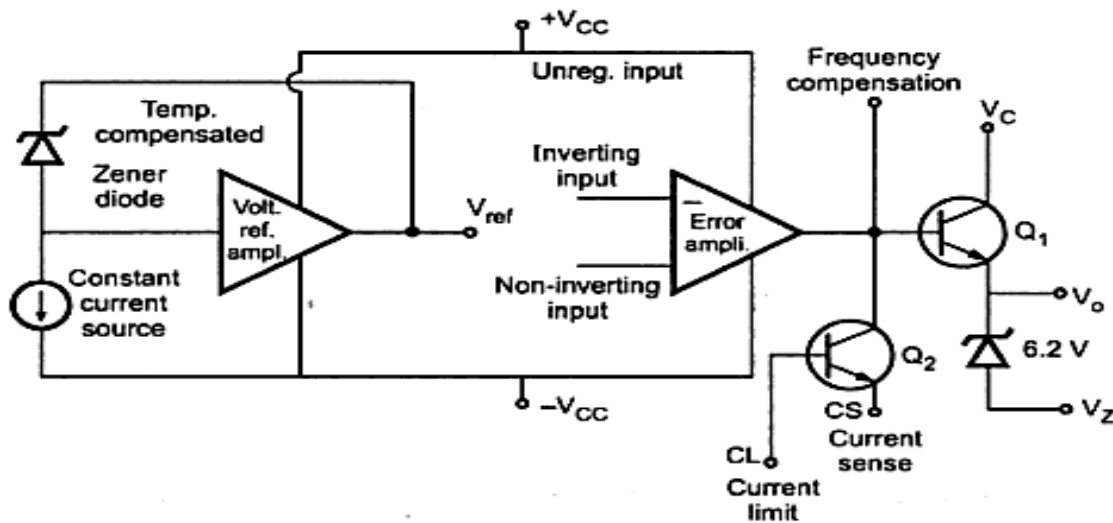
### Functional block diagram IC 723 regulator:



Output voltage is compared with this temperature compensated reference potential of the order of 7 volts. For this,  $V_{rd}$  is connected to the non-inverting input of the error amplifier. This error amplifier is high gain differential amplifier. Its inverting input is connected to the either whole regulated output voltage or part of that from outside. For later case a potential divider of two scaling resistors is used. Scaling resistors help in getting multiplied reference voltage or scaled up reference voltage. Error amplifier controls the series pass transistor  $Q_1$ , which acts as variable resistor. The series pass transistor is a small power transistor having about 800 mW dissipation. The unregulated power supply source ( $< 36V$  d.c.) is connected to collector of series pass transistor.

Transistor  $Q_2$  acts as current limiter in case of short circuit condition. It senses drop across  $I_{cc}$  placed in series with regulated output voltage externally. The frequency compensation terminal controls the frequency response of the error amplifier. The required roll-off is obtained by

connecting a small capacitor of 100 pF between frequency compensation and inverting input terminals.

### **Important Features of IC 723**

- 1) It works as voltage regulator at output voltage ranging from 2 to 37 volts at currents upto 150 mA.
- 2) It can be used at load currents greater than 150 mA with use of suitable NPN or PNP external pass transistors.
- 3) Input and output short-circuit protection is provided.
- 4) It has good line and load regulation (0.03%)
- 5) Wide variety of applications of series, shunt, switching and floating regulator.
- 6) Low temperature drift and high ripple rejection.
- 7) Low standby current drain.
- 8) Small size, lower cost
- 9) Relative ease with which power supply can be designed.
- 10) Provides a choice of supply voltage.

### **9. State the limitations of linear voltage regulators. [CO5- L2]**

Linear regulated power supplies have following limitations :


- 1) The required input step down transformer is bulky and expensive.
- 2) Due to low line frequency (50 Hz), large values of filter capacitors are required.
- 3) The efficiency is very low.
- 4) Input must be greater than the output voltage.
- 5) As large is the difference between input and output voltage, more is the power dissipation in the series pass transistor.
- 6) For higher input voltages, efficiency decreases.
- 7) The need for dual supply, is not economical and feasible to achieve with the help of linear regulators. The switching regulators overcome all these limitations.

**10.Explain the working of step-down switching regulator.[CO5 – L2 -May – 2011]****BUCKING SWITCHING REGULATOR**

Figure 8.28 shows the basic diagram of a step-down or bucking switching regulator circuit. The input voltage  $V_i$  is a dc voltage. A pulse train is applied efficiently to the base of the control transistor Q1, and the transistor acts as a switch, alternating between its cut-off and saturation regions. When the transistor is ON, the diode D gets reverse biased. When the transistor is OFF, it becomes forward biased providing a continuous path for the inductive current. The LC filter functions as a smoothing circuit for the input variations that provides a steady dc output voltage.

When the transistor Q1 is turned ON and OFF for equal time durations, i.e. when duty cycle  $D$  of the pulse train is 50%, the dc output voltage  $V_o$  is given by  $V_o = (t_{ON}/T)V_i = 0.5V_i$ . Note that the voltage drop across transistor and diodes are neglected. A typical switching frequency for the transistor is several kHz.

The reference voltage  $V_{ref}$  is obtained from the unregulated input voltage with the use of a Zener diode. The error circuit compares the regulated output voltage with the  $V_{ref}$  voltage. The output of the error circuit operates the pulse width modulator. The pulse width modulator generates pulses at a fixed frequency. The width of the pulses is dependent on the control voltage from the error circuit. When the dc output voltage falls below the reference voltage, the error signal is generated in the error circuit. This causes the width of the pulses to increase, thus increasing the output voltage. If the output voltage is more than the reference voltage, the error signal reduces the pulse width which results in reducing the output voltage. Thus the constant output voltage is maintained.

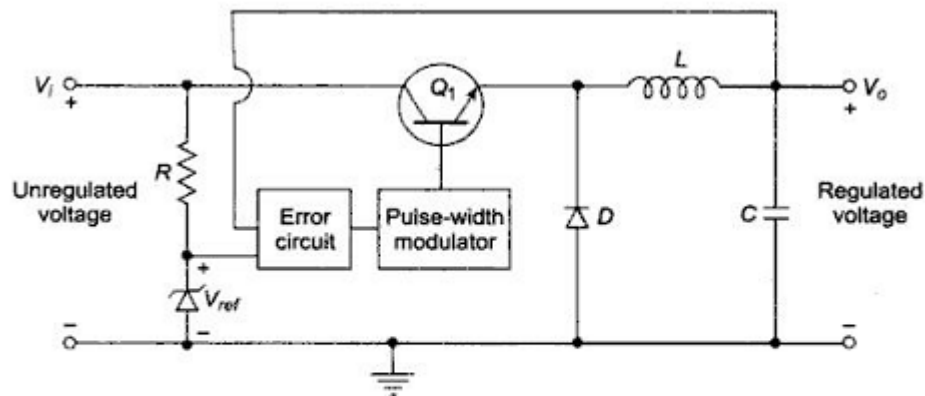

Basic diagram of a step-down (Bucking) switching regulator circuit

**11. With suitable diagram, explain the working of a switched capacitor filter. Also explain how resistor can be realized using switched capacitor filter. [CO5- L3 -May – 2011]**

### SWITCHED CAPACITOR FILTER

Active RC filters using ICs have advantages of not using inductors and of offering easy implementation of various high performance low-pass, high-pass, band-pass and band-elimination filters. The resistor values needed for these filters are generally much too large for fabrication on a monolithic IC chip. Integrated (diffused) resistors have poor temperature and linearity characteristics. Large value resistors ( $\geq 10 \text{ k}\Omega$ ) take up an excessive amount of chip area. This is the major reason that active filters have not previously been fully integrated in MOS technology. The switched capacitor filter offers an attractive alternative to the conventional RC active filter.

A switched capacitor filter shown in Fig. is a three terminal element which consists of capacitors, periodic switches and operational amplifiers and whose open circuit voltage transfer function represents filtering characteristics. It is not possible to manufacture passive elements of an RC active filter with suitable values and quality in the same technology as the op-amps. For the range of frequencies within which the op-amp operates satisfactorily, it is not possible in MOS technology to implement RC products of sufficient magnitude and accuracy.

On the other hand, in the case of switched capacitor filter, the RC products are set by capacitor ratios and the switch period. In MOS technology, the accuracy and the values of these quantities are suitable for the implementation of selective filters. The large resistor values required for active filters are easily simulated by the combination of small value capacitors (say 10 PF) and MOS switching transistors. The equivalent resistor value so obtained is high enough such that the filter capacitance value should be small enough to be easily incorporated on a monolithic IC chip.


 


Fig. 7.19 Switched capacitor filter schematic

 

**12. With a neat functional diagram explain the operation of LM 380 power amplifier.[CO5- L3 –May/June2016]**

LM 380 is a popular power audio amplifier produced by national semiconductor. It is capable of delivering 2.5 W minimum to 8 $\Omega$  load. Hence it is very much ideal for consumer applications.

**Features of LM380:**

- Internally fixed gain of 50 (34dB)
- Output is automatically self centering to one half of the supply voltage.
- Output is short circuit proof with internal thermal limiting.
- Input stage allows the input to be ground referenced or ac coupled.
- Wide supply voltage range (5 to 22V).
- High peak current capability.
- High impedance.
- Low total harmonic distortion
- Bandwidth of 100KHz at  $P_{out} = 2W$  &  $R_L = 8\Omega$

**Pin diagram of LM380:**

The figure shows the pin diagram of LM380 power audio amplifier. A copper lead frame is used with the center three pins on either side (3,4,5,10,11,12) of DIP package comprises a heat sink.




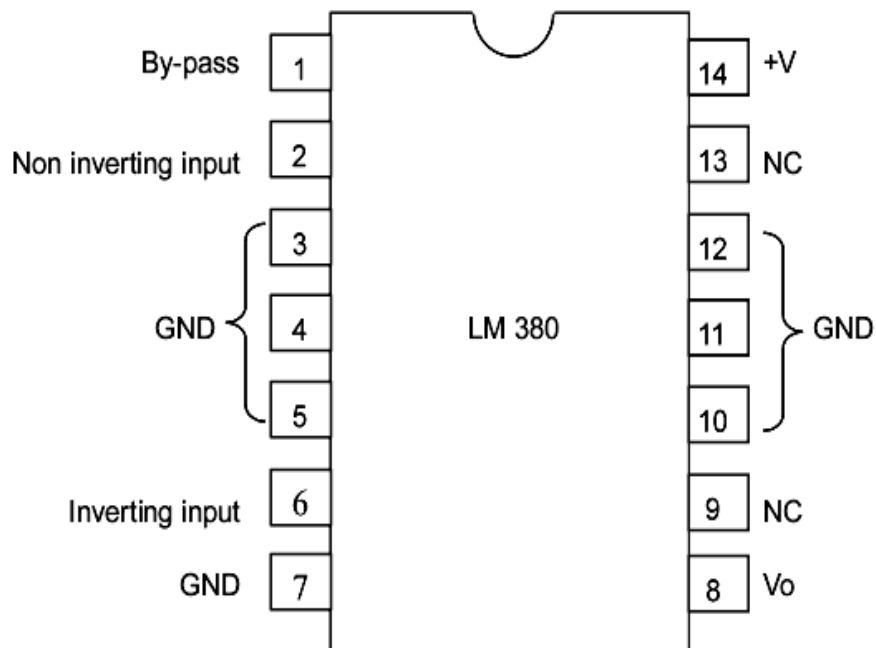


Fig: Pin diagram

 Symbolically LM 380 audio amplifier is represented as shown in the Fig.



Symbolic representation of LM 380

### (i) PNP Emitter follower:

- The input stage is emitter follower composed of PNP transistors Q1 & Q2 which drives the PNP Q3-Q4 differential pair.


- The choice of PNP input transistors Q1 & Q2 allows the input to be referenced to ground i.e., the input can be direct coupled to either the inverting & non-inverting terminals of the amplifier.

**(ii) Differential Amplifier:**

- The current in the PNP differential pair Q3-Q4 is established by Q7, R3 & +V.
- The current mirror formed by transistor Q7, Q8 & associated resistors then establishes the collector current of Q9.
- Transistor Q5 & Q6 constitute of collector loads for the PNP differential pair.
- The output of the differential amplifier is taken at the junction of Q4 & Q6 transistors & is applied as an input to the common emitter voltage gain.

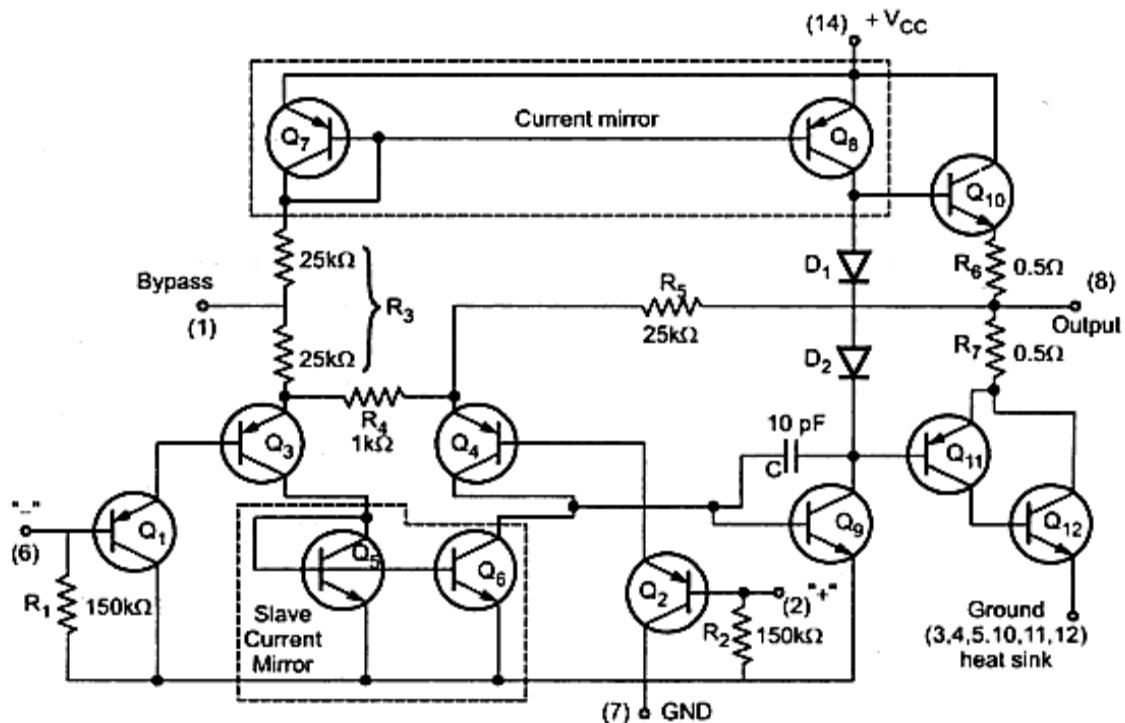**(iii) Common Emitter:**

- Common Emitter amplifier stage is formed by transistor Q9 with D1, D2 & Q8 as a current source load.
- The capacitor C between the base & collector of Q9 provides internal compensation & helps to establish the upper cutoff frequency of 100 KHz.
- Since Q7 & Q8 form a current mirror, the current through D1 & D2 is approximately the same as the current through R3.
- D1 & D2 are temperature compensating diodes for transistors Q10 & Q11 in that D1 & D2 have the same characteristics as the base-emitter junctions of Q11. Therefore the current through Q10 & (Q11-Q12) is approximately equal to the current through diodes D1 & D2.



Internal circuit diagram of LM 380

**(iv) (Output stage) - Emitter follower:**

Emitter follower formed by NPN transistor Q10 & Q11. The combination of PNP transistor Q11 & NPN transistor Q12 has the power capability of an NPN transistors but the characteristics of a PNP transistor.

- The negative dc feedback applied through R5 balances the differential amplifier so that the dc output voltage is stabilized at  $+V/2$ ;
- To decouple the input stage from the supply voltage  $+V$ , by pass capacitor in order of micro farad should be connected between the by pass terminal (pin 1) & ground (pin 7).
- The overall internal gain of the amplifier is fixed at 50. However gain can be increased by using positive feedback.

**13.A 555 timer is configured in astable mode with  $R_A = 2 \text{ kohm}$   $R_B = 6 \text{ kohm}$  and  $C = 0.1 \mu\text{F}$ . Determine the frequency of oscillation. [CO5 –H3 –May/June 2016]**

$$T = 0.69(R_A + 2R_B)C$$

So,

$$f = 1/T = 1.45 / [(R_A + 2R_B)C]$$

$$f = 1.45 / [(2\text{k} + 12\text{k})0.1\mu]$$

$$f = 1.035 \text{ Kohm.}$$